


Computer Architecture
EECS 361
Lecture 8: Designing a Single Cycle Datapath

Outline of Today's Lecture


- **Introduction**
- **Where are we with respect to the BIG picture?**
- **Questions and Administrative Matters**
- **The Steps of Designing a Processor**
- **Datapath and timing for Reg-Reg Operations**
- **Datapath for Logical Operations with Immediate**
- **Datapath for Load and Store Operations**
- **Datapath for Branch and Jump Operations**

The Big Picture: Where are We Now?

 ◦ The Five Classic Components of a Computer



 
◦ Today's Topic: Design a Single Cycle Processor



The Big Picture: The Performance Perspective

◦ Performance of a machine is determined by:

 - Instruction count
- Clock cycle time
- Clock cycles per instruction



◦ Processor design (datapath and control) will determine:

- Clock cycle time
- Clock cycles per instruction

◦ Today:


- Single cycle processor:
 - Advantage: One clock cycle per instruction
 - Disadvantage: long cycle time

How to Design a Processor: step-by-step

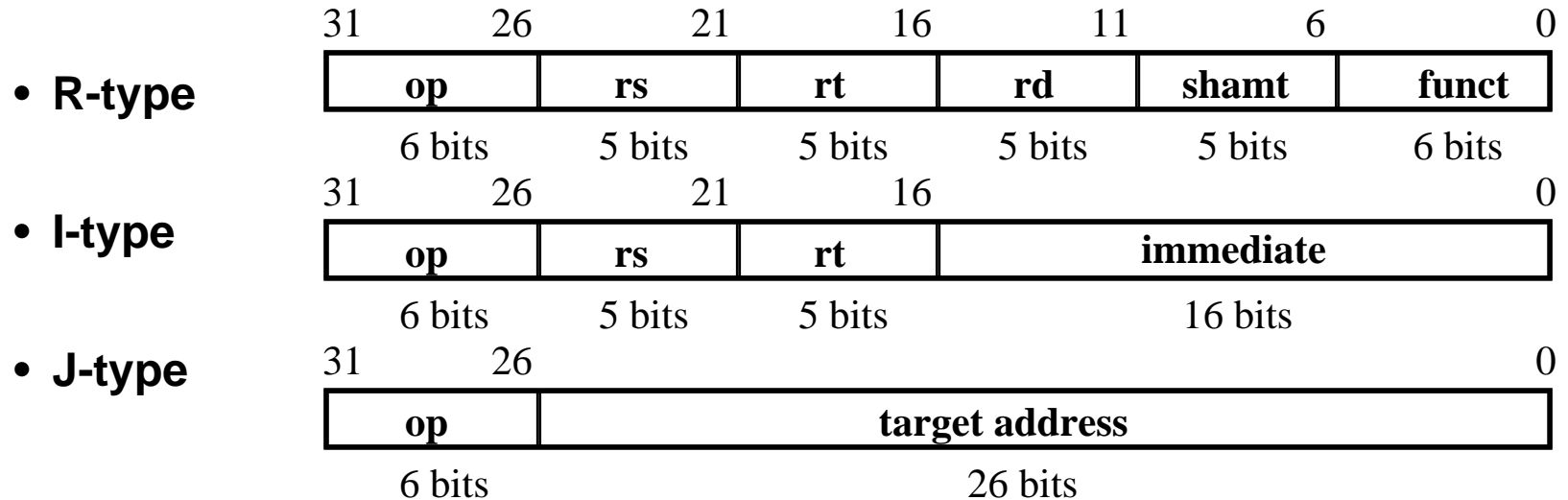- 1. Analyze instruction set => datapath requirements
 - the meaning of each instruction is given by the *register transfers*
 - datapath must include storage element for ISA registers
 - possibly more
 - datapath must support each register transfer
- 2. Select set of datapath components and establish clocking methodology
- 3. Assemble datapath meeting the requirements
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- 5. Assemble the control logic

The MIPS Instruction Formats

- All MIPS instructions are 32 bits long. The three instruction formats:




- The different fields are:
 - **op**: operation of the instruction
 - **rs, rt, rd**: the source and destination register specifiers
 - **shamt**: shift amount
 - **funct**: selects the variant of the operation in the “op” field
 - **address / immediate**: address offset or immediate value
 - **target address**: target address of the jump instruction

Step 1a: The MIPS-lite Subset for today


◦ ADD and SUB

 - **addU rd, rs, rt**
- **subU rd, rs, rt**




◦ OR Immediate:

- **ori rt, rs, imm16**

 


◦ LOAD and STORE Word

 - **lw rt, rs, imm16**
- **sw rt, rs, imm16**



◦ BRANCH:

- **beq rs, rt, imm16**

 

Step 1: Requirements of the Instruction Set


- **Memory**
 - **instruction & data**
- **Registers (32 x 32)**
 - **read RS**
 - **read RT**
 - **Write RT or RD**
- **PC**
- **Extender**
- **Add and Sub register or extended immediate**
- **Add 4 or extended immediate to PC**

Step 2: Components of the Datapath


- **Combinational Elements**
- **Storage Elements**
 - **Clocking methodology**

Combinational Logic Elements (Basic Building Blocks)


◦ Adder

 

◦ MUX

 


◦ ALU

 

Storage Element: Register (Basic Building Block)

◦ Register

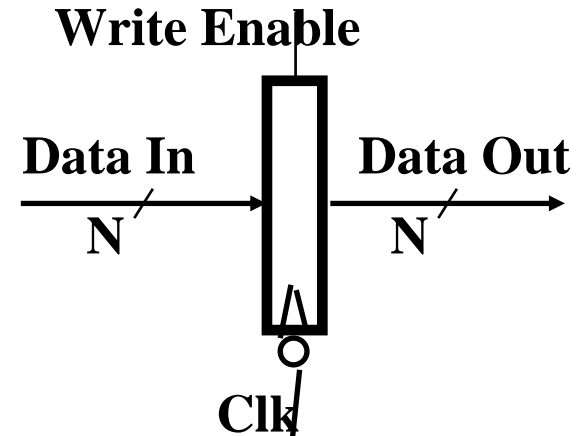
- **Similar to the D Flip Flop except**
 - **N-bit input and output**
 - **Write Enable input**
- **Write Enable:**
 - **negated (0): Data Out will not change**
 - **asserted (1): Data Out will become Data In**



Storage Element: Register File

- Register File consists of 32 registers:

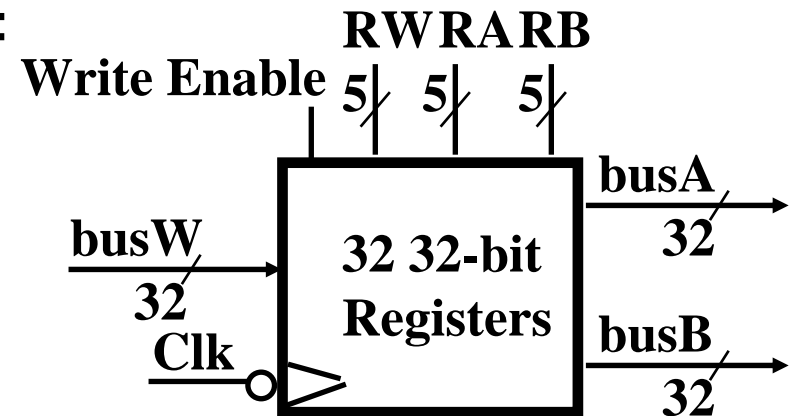- Two 32-bit output busses:
busA and busB
- One 32-bit input bus: busW



- Register is selected by:

- RA (number) selects the register to put on busA (data)
- RB (number) selects the register to put on busB (data)
- RW (number) selects the register to be written via busW (data) when Write Enable is 1

- Clock input (CLK)

- The CLK input is a factor ONLY during write operation
- During read operation, behaves as a combinational logic block:
 - RA or RB valid => busA or busB valid after “access time.”

Storage Element: Idealized Memory

- **Memory (idealized)**


- One input bus: Data In
- One output bus: Data Out

- **Memory word is selected by:**


- Address selects the word to put on Data Out
- Write Enable = 1: address selects the memory word to be written via the Data In bus

- **Clock input (CLK)**

 - The CLK input is a factor **ONLY** during write operation
- During read operation, behaves as a combinational logic block:
 - Address valid => Data Out valid after “access time.”



Clocking Methodology

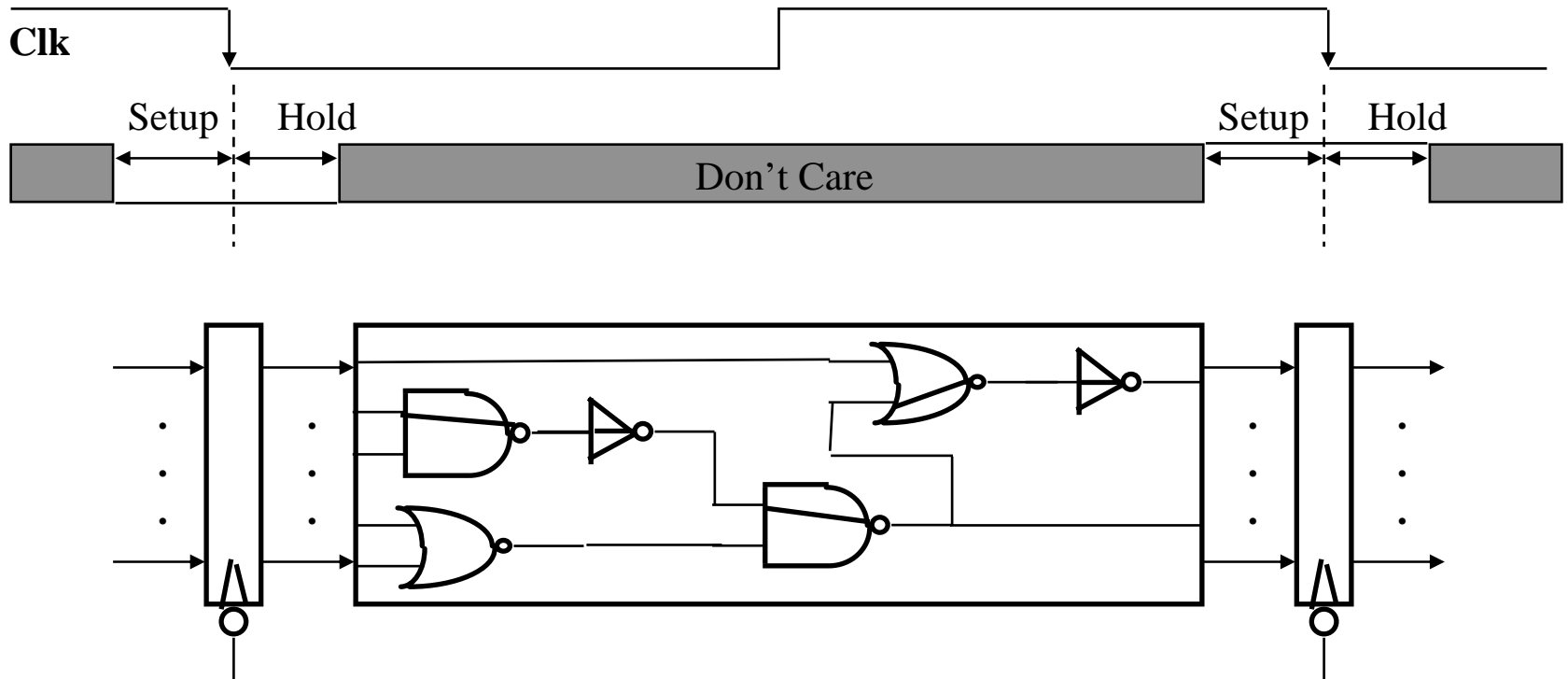

- All storage elements are clocked by the same clock edge
- **Cycle Time = CLK-to-Q + Longest Delay Path + Setup + Clock Skew**

Questions and Administrative Matters


Step 3

- **Register Transfer Requirements**
→ **Datapath Assembly**
- **Instruction Fetch**
- **Read Operands and Execute Operation**


3a: Overview of the Instruction Fetch Unit

◦ The common RTL operations

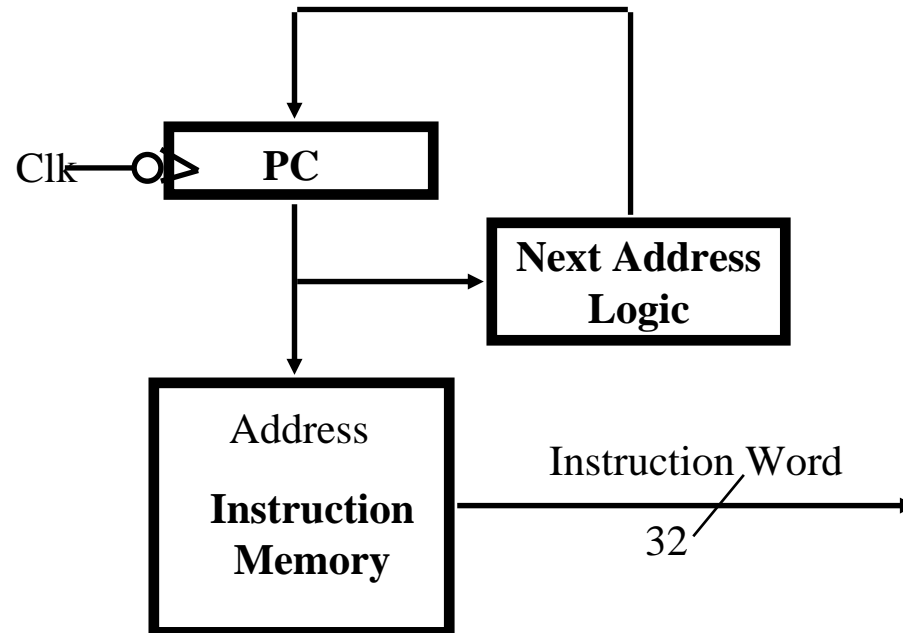- Fetch the Instruction: $\text{mem}[\text{PC}]$
- Update the program counter:
 - Sequential Code: $\text{PC} \leftarrow \text{PC} + 4$
 - Branch and Jump: $\text{PC} \leftarrow \text{“something else”}$



RTL: The ADD Instruction

 

◦ **add rd, rs, rt**

• **mem[PC]**

Fetch the instruction from memory


• **$R[rd] \leftarrow R[rs] + R[rt]$**

The actual operation

• **$PC \leftarrow PC + 4$**

Calculate the next instruction's address

RTL: The Subtract Instruction

 

◦ **sub rd, rs, rt**



- **mem[PC]** **Fetch the instruction from memory**
- **R[rd] ← R[rs] - R[rt]** **The actual operation**
- **PC ← PC + 4** **Calculate the next instruction's address**

3b: Add & Subtract

◦ $R[rd] \leftarrow R[rs] \text{ op } R[rt]$

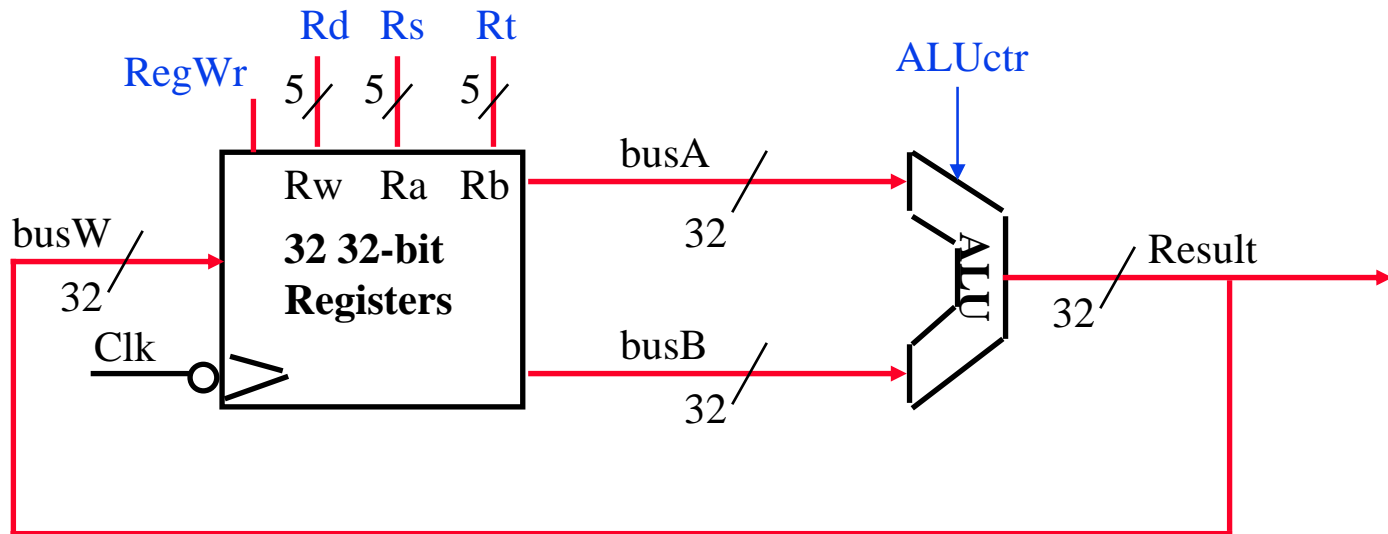 
Example: addU rd, rs, rt

- Ra, Rb, and Rw come from instruction's rs, rt, and rd fields
- ALUctr and RegWr: control logic after decoding the instruction





Datapath for Register-Register Operations (in general)

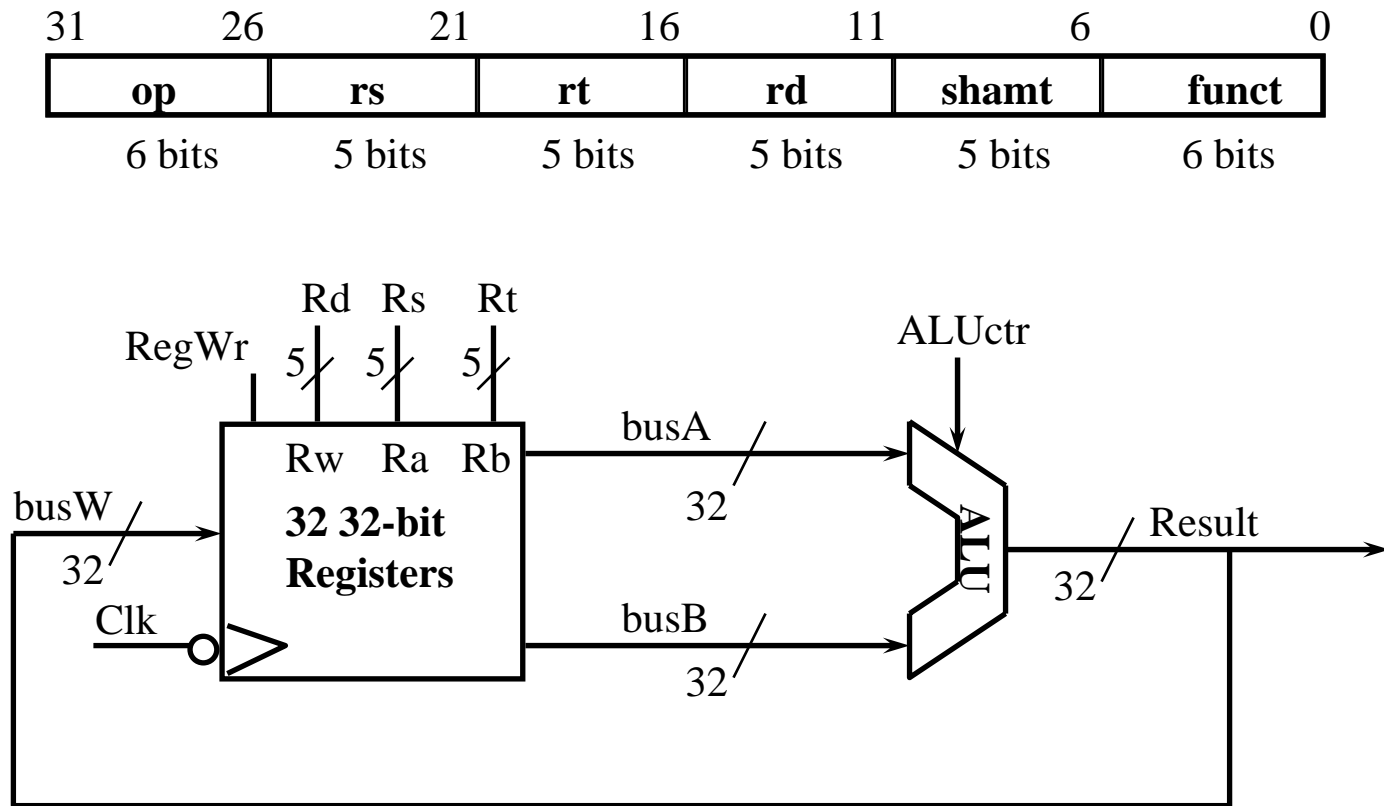
- $R[rd] \leftarrow R[rs] \text{ op } R[rt]$ Example: `add rd, rs, rt`
 - Ra, Rb, and Rw comes from instruction's rs, rt, and rd fields
 - ALUctr and RegWr: control logic after decoding the instruction



Register-Register Timing

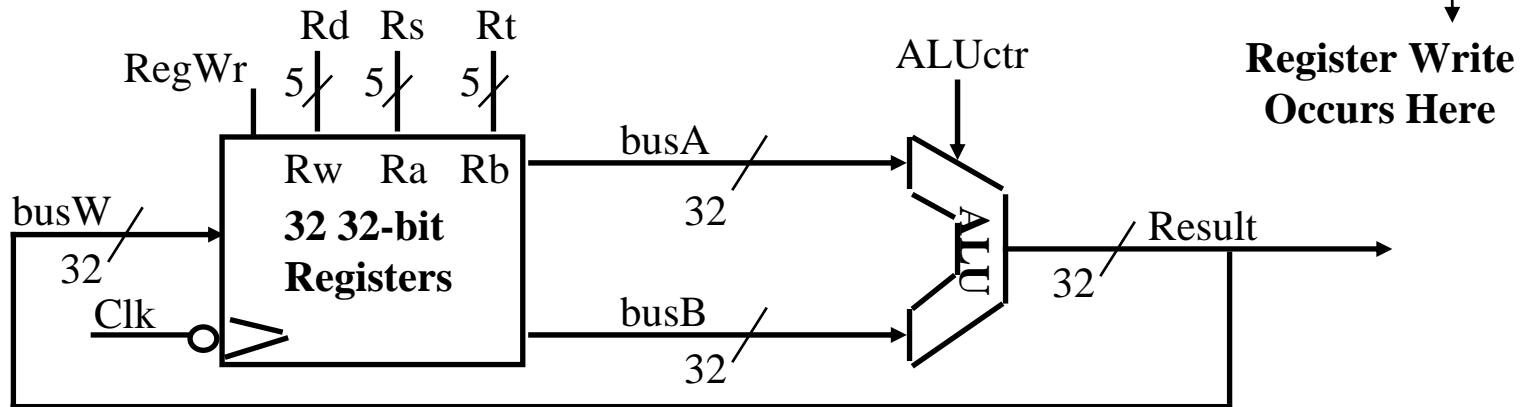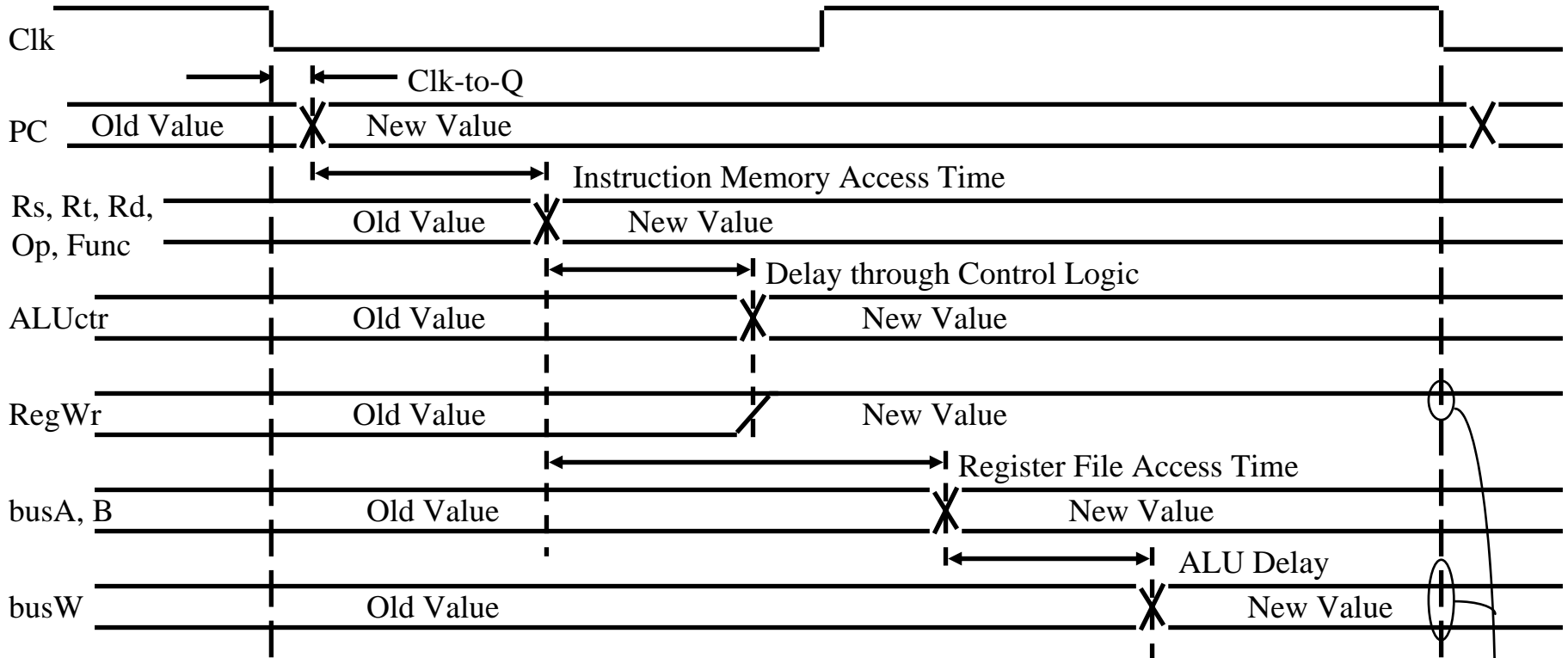


RTL: The OR Immediate Instruction

 



◦ **ori** **rt, rs, imm16**

 - **mem[PC]** **Fetch the instruction from memory**
- **R[rt] <- R[rs] or ZeroExt(imm16)**
 The OR operation
- **PC <- PC + 4** **Calculate the next instruction's address**




3c: Logical Operations with Immediate

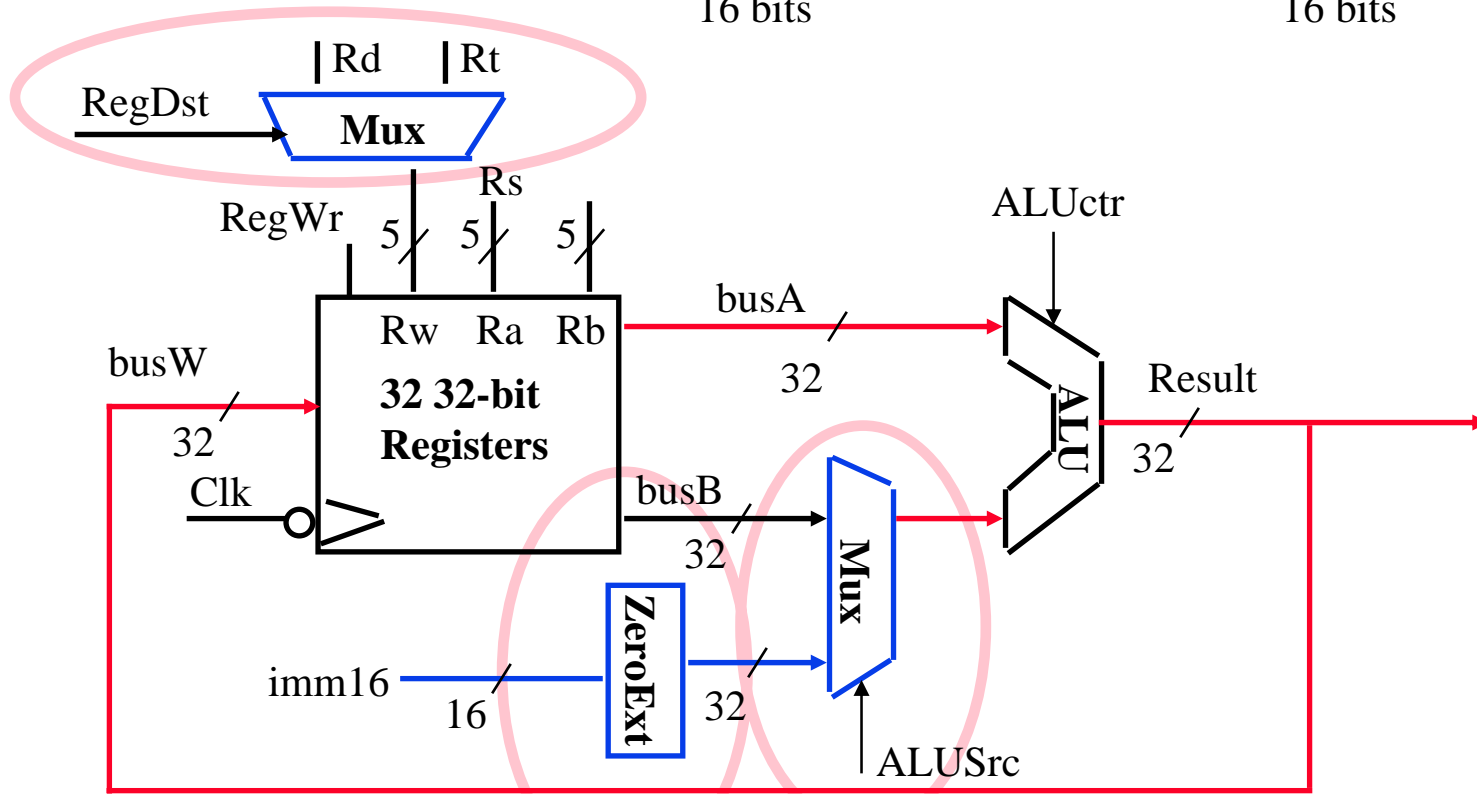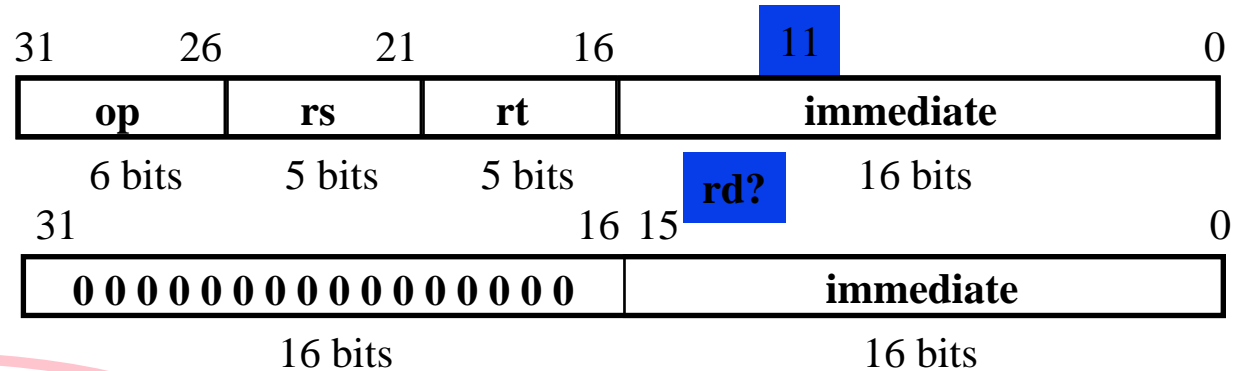◦ $R[rt] \leftarrow R[rs] \text{ op ZeroExt}[imm16]$




RTL: The Load Instruction

 

- mem[PC] **Fetch the instruction from memory**



- Addr <- R[rs] + SignExt(imm16) **Calculate the memory address**
 - R[rt] <- Mem[Addr] **Load the data into the register**

 - PC <- PC + 4 **Calculate the next instruction's address**





3d: Load Operations

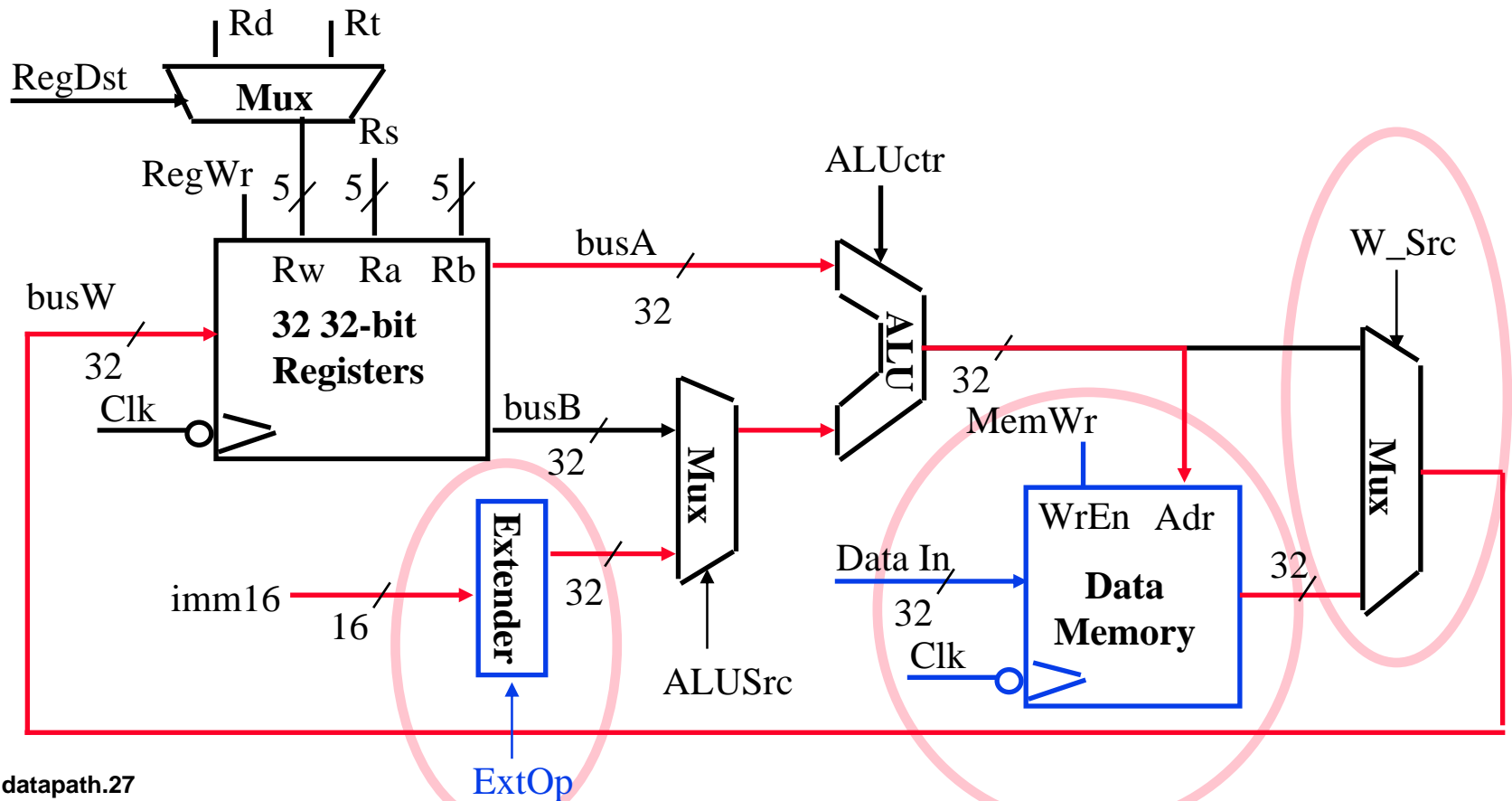 ◦ $R[rt] \leftarrow Mem[R[rs] + SignExt[imm16]]$ Example: lw rt, rs, imm16




3e: Store Operations

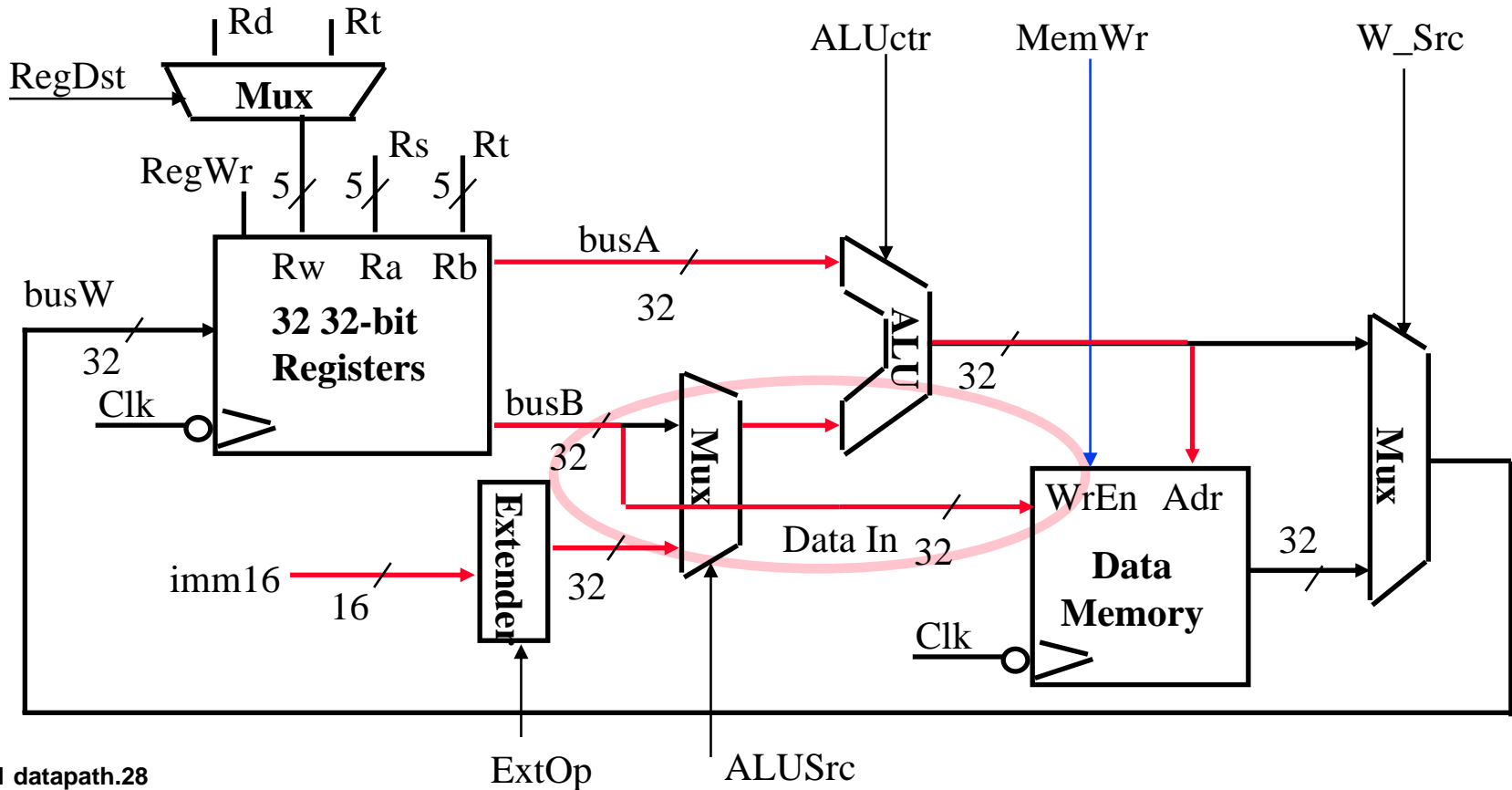 - $\text{Mem}[R[\text{rs}] + \text{SignExt}[\text{imm16}] \leftarrow R[\text{rt}]]$ Example: `sw rt, rs, imm16`



3f: The Branch Instruction

 

- **beq rs, rt, imm16**
 - **mem[PC]** **Fetch the instruction from memory**

 - **Equal <- R[rs] == R[rt]** **Calculate the branch condition**



 - **if (COND eq 0)** **Calculate the next instruction's address**
 - **PC <- PC + 4 + (SignExt(imm16) x 4)**

 - **else**
 - **PC <- PC + 4**


Datapath for Branch Operations

◦ beq rs, rt, imm16

Datapath generates condition (equal)

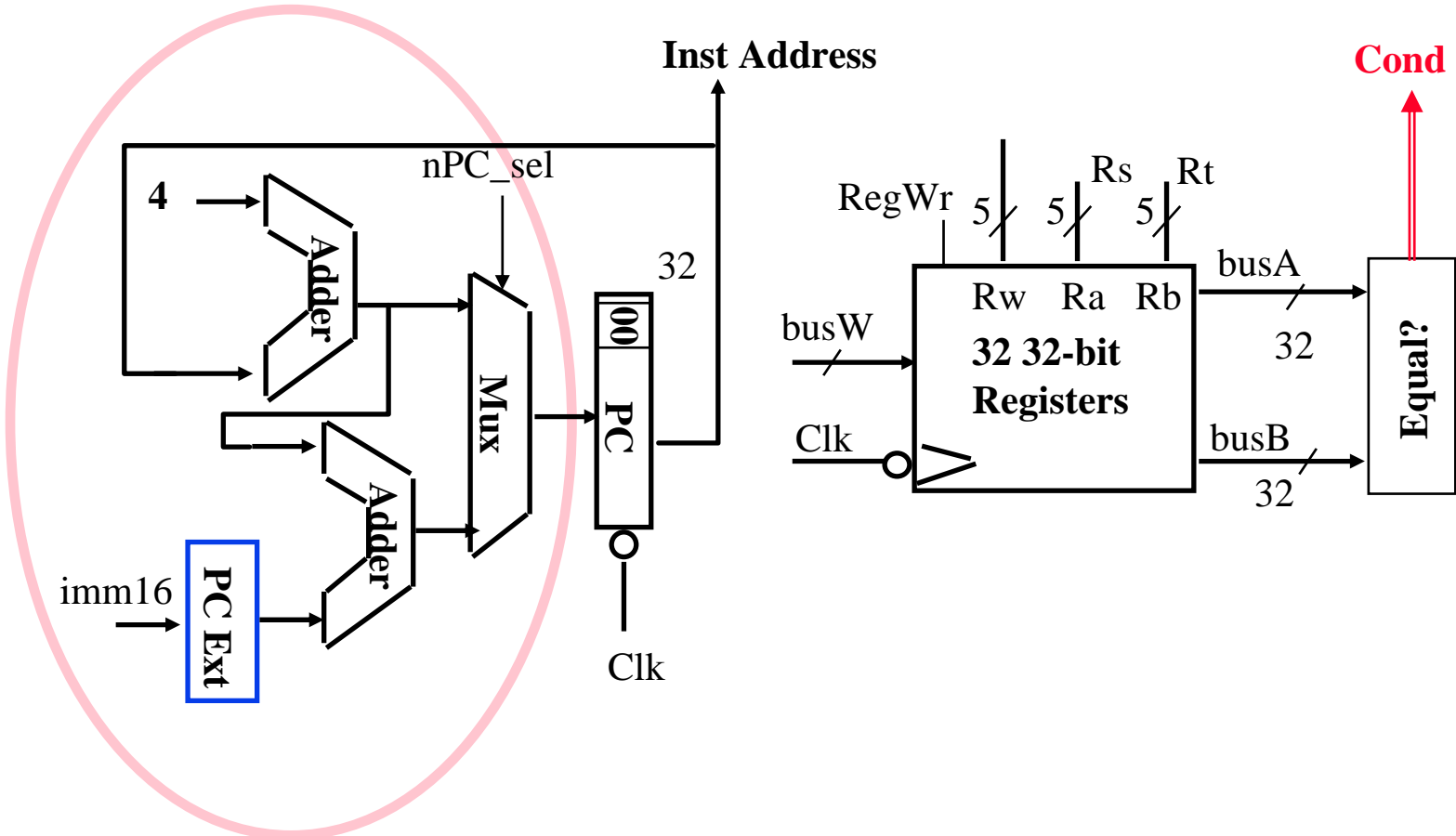 


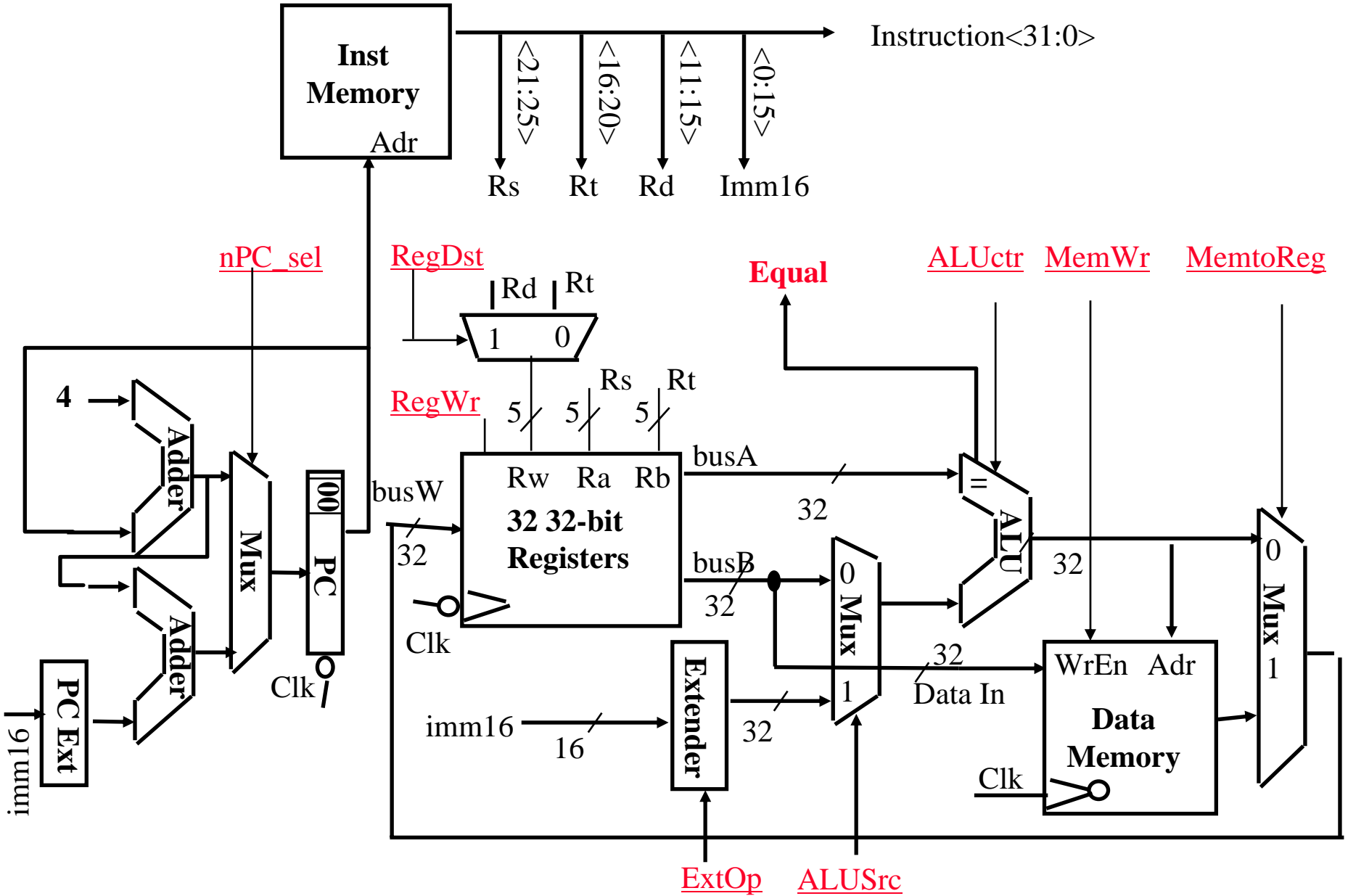Putting it All Together: A Single Cycle Datapath



An Abstract View of the Critical Path

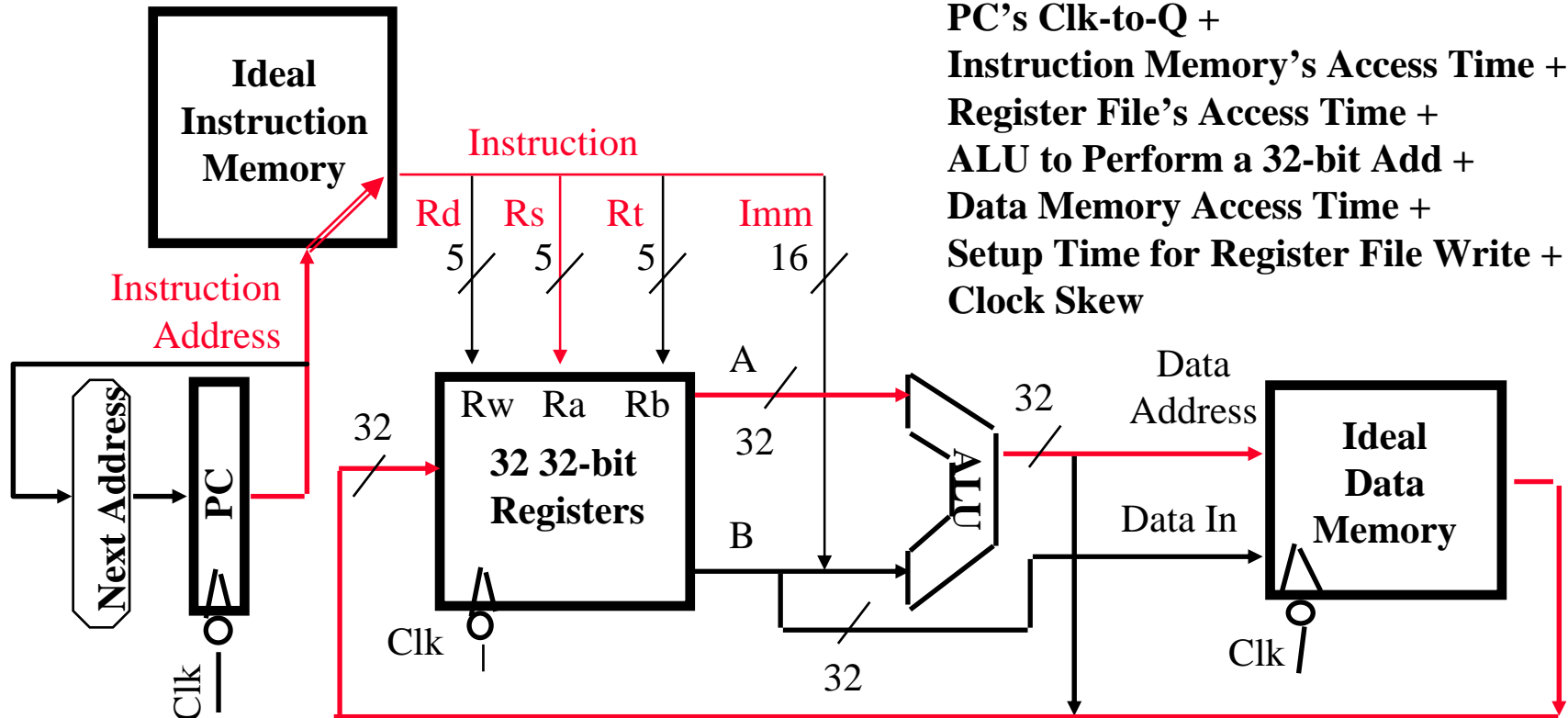- Register file and ideal memory:
 - The CLK input is a factor ONLY during write operation
 - During read operation, behave as combinational logic:
 - Address valid => Output valid after “access time.”



Critical Path (Load Operation) =
PC's Clk-to-Q +
Instruction Memory's Access Time +
Register File's Access Time +
ALU to Perform a 32-bit Add +
Data Memory Access Time +
Setup Time for Register File Write +
Clock Skew


Binary Arithmetics for the Next Address

- In theory, the PC is a 32-bit byte address into the instruction memory:
 - Sequential operation: $PC\langle 31:0 \rangle = PC\langle 31:0 \rangle + 4$
 - Branch operation: $PC\langle 31:0 \rangle = PC\langle 31:0 \rangle + 4 + \text{SignExt}[\text{Imm16}] * 4$
- The magic number “4” always comes up because:
 - The 32-bit PC is a byte address
 - And all our instructions are 4 bytes (32 bits) long
- In other words:
 - The 2 LSBs of the 32-bit PC are always zeros
 - There is no reason to have hardware to keep the 2 LSBs
- In practice, we can simplify the hardware by using a 30-bit $PC\langle 31:2 \rangle$:
 - Sequential operation: $PC\langle 31:2 \rangle = PC\langle 31:2 \rangle + 1$
 - Branch operation: $PC\langle 31:2 \rangle = PC\langle 31:2 \rangle + 1 + \text{SignExt}[\text{Imm16}]$
 - In either case: Instruction Memory Address = $PC\langle 31:2 \rangle$ concat “00”

Next Address Logic: Expensive and Fast Solution


- Using a 30-bit PC:

 - Sequential operation: $PC\langle 31:2 \rangle = PC\langle 31:2 \rangle + 1$
- Branch operation: $PC\langle 31:2 \rangle = PC\langle 31:2 \rangle + 1 + \text{SignExt}[\text{Imm16}]$
- In either case: Instruction Memory Address = $PC\langle 31:2 \rangle$ concat "00"




Next Address Logic: Cheap and Slow Solution

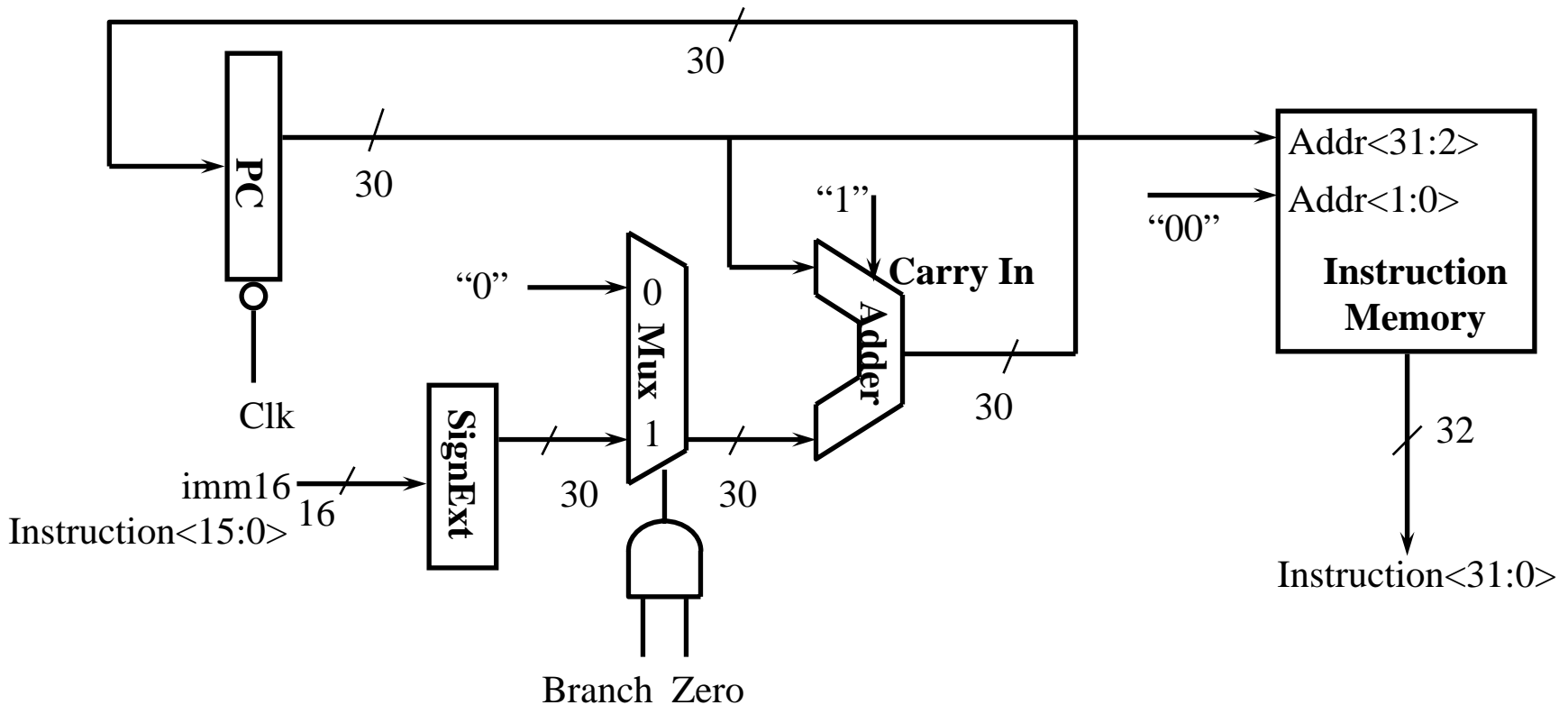- Why is this slow?
 - Cannot start the address add until Zero (output of ALU) is valid
- Does it matter that this is slow in the overall scheme of things?
 - Probably not here. Critical path is the load operation.



RTL: The Jump Instruction

 


◦ j target

- mem[PC] Fetch the instruction from memory
- $PC\langle 31:2 \rangle \leftarrow PC\langle 31:28 \rangle \text{ concat target}\langle 25:0 \rangle$
Calculate the next instruction's address


Instruction Fetch Unit

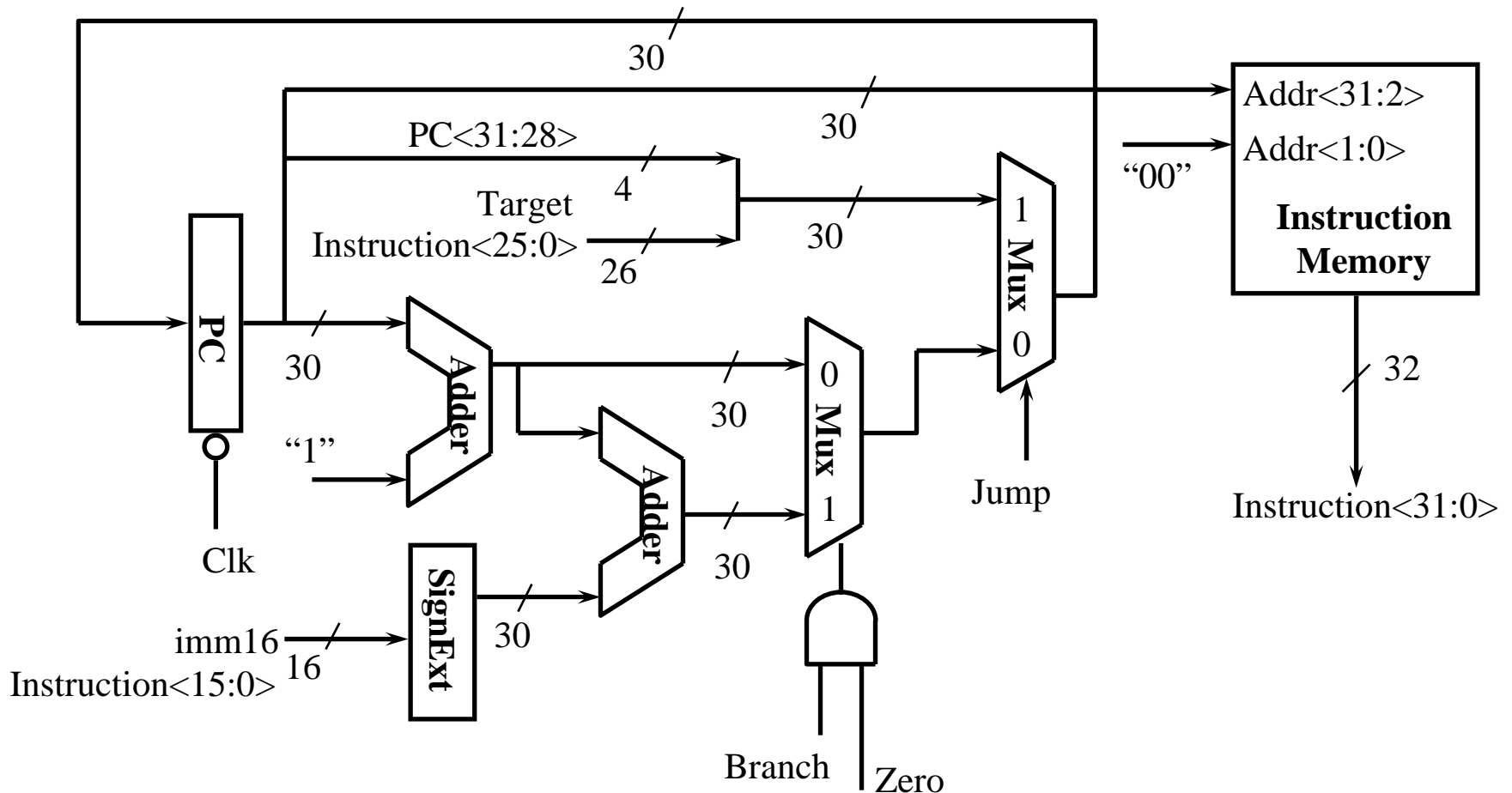- j target
 - $PC\langle 31:2 \rangle \leftarrow PC\langle 31:28 \rangle \text{ concat target}\langle 25:0 \rangle$




Putting it All Together: A Single Cycle Datapath

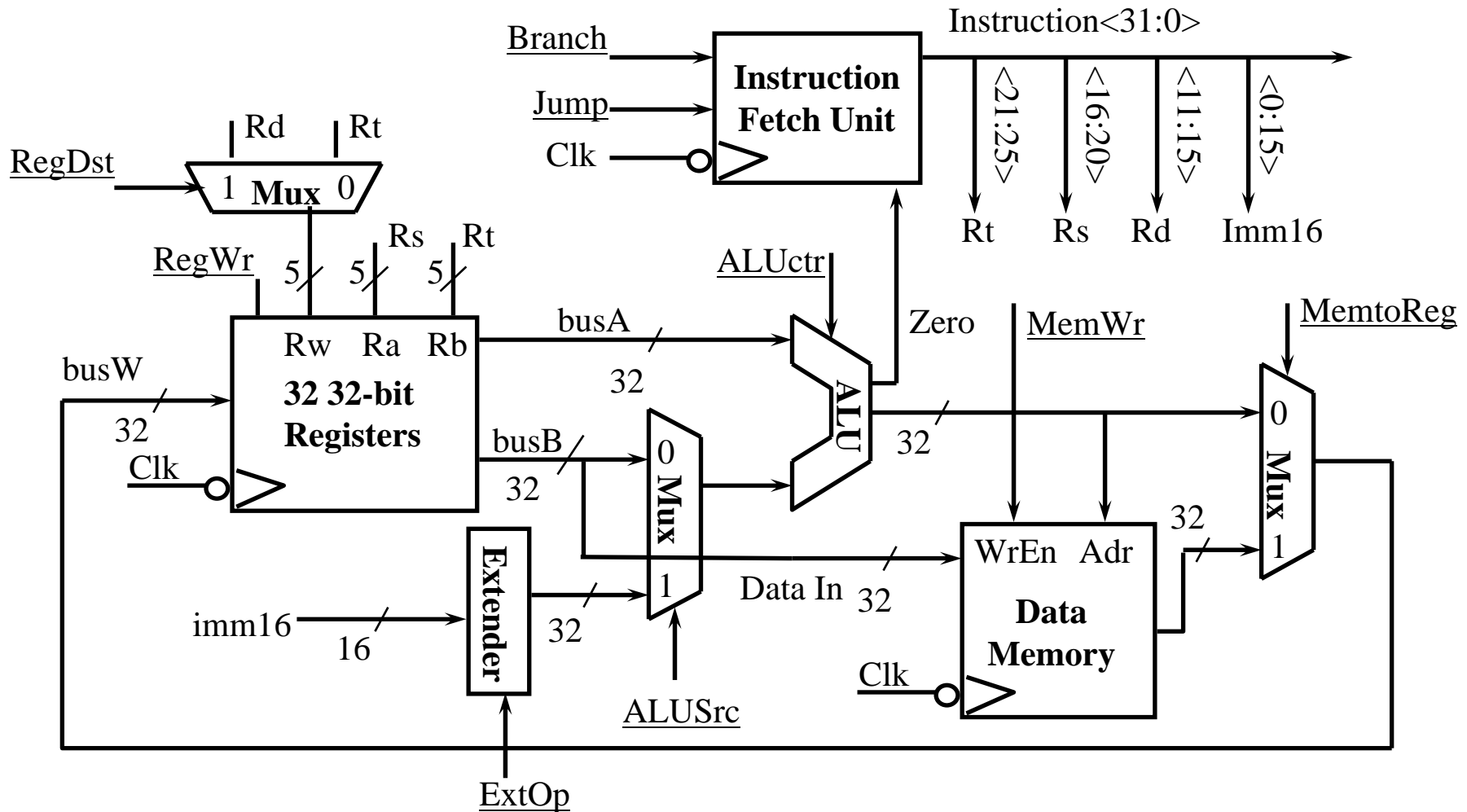- We have everything except control signals (underline)





An Abstract View of the Implementation

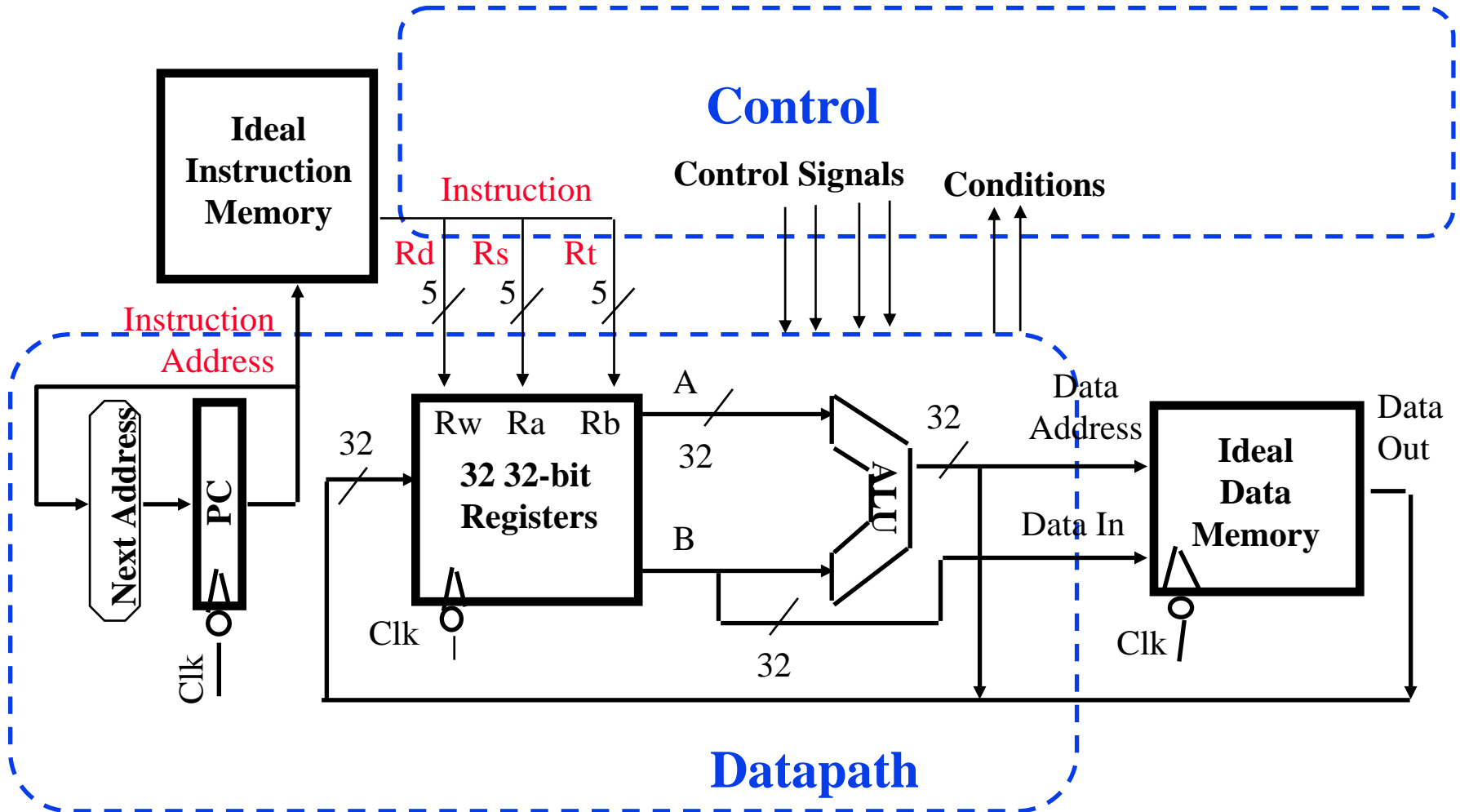

- Logical vs. Physical Structure

A Real MIPS Datapath

 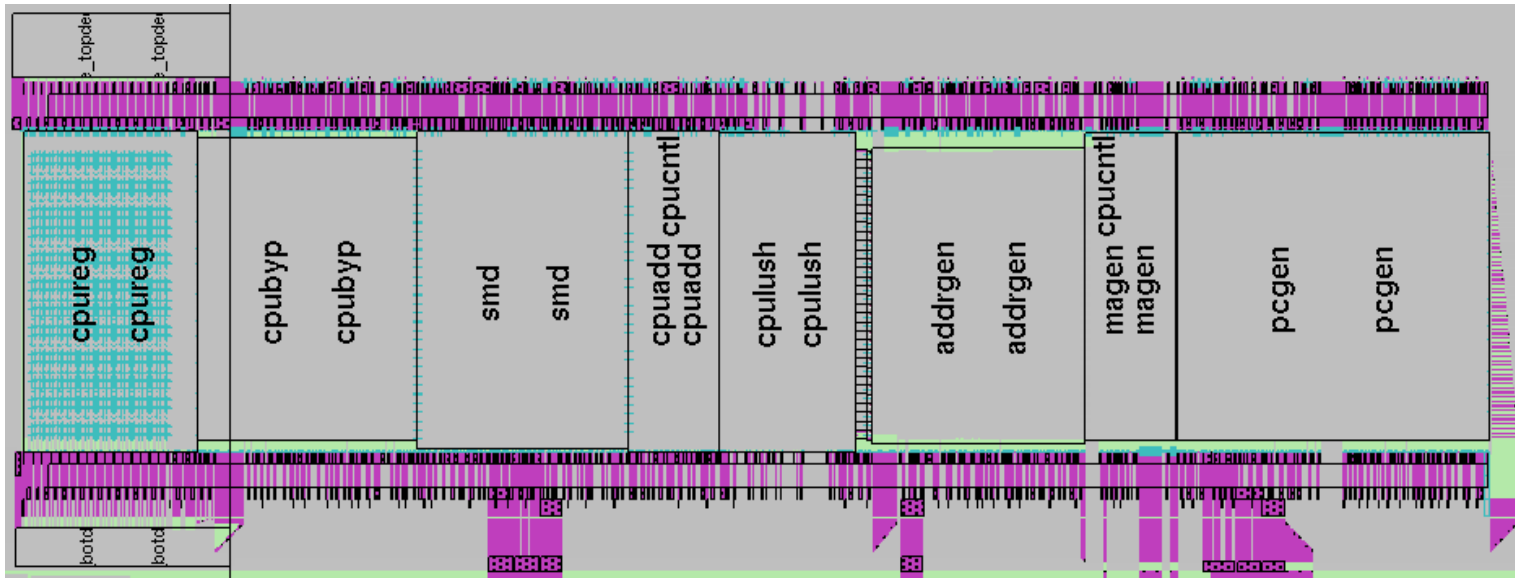

Summary

◦ 5 steps to design a processor

- 1. Analyze instruction set => datapath requirements
- 2. Select set of datapath components & establish clock methodology
- 3. Assemble datapath meeting the requirements
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- 5. Assemble the control logic

◦ MIPS makes it easier

- Instructions same size
- Source registers always in same place
- Immediates same size, location
- Operations always on registers/immediates

◦ Single cycle datapath => CPI=1, CCT => long

◦ Next time: implementing control (Steps 4 and 5)