 



EECS 361
Computer Architecture
Lecture 10: Designing a Multiple Cycle Processor

Recap: A Single Cycle Datapath

- We have everything except control signals (underline)
 - Today's lecture will show you how to generate the control signals




 Recap: PLA Implementation of the Main Control



The Big Picture: Where are We Now?

 - The Five Classic Components of a Computer




- Today's Topic: Designing the Datapath for the Multiple Clock Cycle Datapath

Outline of Today's Lecture

- **Recap and Introduction**
- **Introduction to the Concept of Multiple Cycle Processor**
- **Multiple Cycle Implementation of R-type Instructions**
- **What is a Multiple Cycle Delay Path and Why is it Bad?**
- **Multiple Cycle Implementation of Or Immediate**
- **Multiple Cycle Implementation of Load and Store**
- **Putting it all Together**

 
Abstract View of our single cycle processor



◦ looks like a FSM with PC as state

What's wrong with our CPI=1 processor?

Arithmetic & Logical

 

Load



← Critical Path →

Store



Branch



- Long Cycle Time
- All instructions take as much time as the slowest
- Real memory is not so nice as our idealized memory
 - cannot always get the job done in one (short) cycle


Drawbacks of this Single Cycle Processor

- Long cycle time:
 - Cycle time must be long enough for the load instruction:
 - PC's Clock -to-Q +
 - Instruction Memory Access Time +
 - Register File Access Time +
 - ALU Delay (address calculation) +
 - Data Memory Access Time +
 - Register File Setup Time +
 - Clock Skew
- Cycle time is much longer than needed for all other instructions.
Examples:
 - R-type instructions do not require data memory access
 - Jump does not require ALU operation nor data memory access

Overview of a Multiple Cycle Implementation

- The root of the single cycle processor's problems:
 - The cycle time has to be long enough for the slowest instruction
- Solution:
 - Break the instruction into smaller steps
 - Execute each step (instead of the entire instruction) in one cycle
 - Cycle time: time it takes to execute the longest step
 - Keep all the steps to have similar length
 - This is the essence of the multiple cycle processor
- The advantages of the multiple cycle processor:
 - Cycle time is much shorter
 - Different instructions take different number of cycles to complete
 - Load takes five cycles
 - Jump only takes three cycles
 - Allows a functional unit to be used more than once per instruction


The Five Steps of a Load Instruction

 

Register File & Memory Write Timing: Ideal vs. Reality


- In previous lectures, register file and memory are simplified:

 - Write happens at the clock tick
- Address, data, and write enable must be stable one “set-up” time before the clock tick



- In real life:

 
- Neither register file nor ideal memory has the clock input
- The write path is a combinational logic delay path:
 - Write enable goes to 1 and Din settles down
 - Memory write access delay
 - Din is written into mem[address]
- Important: Address and Data must be stable BEFORE Write Enable goes to 1



Race Condition Between Address and Write Enable


- This “real” (no clock input) register file may not work reliably in the single cycle processor because:

 - We cannot guarantee Rw will be stable BEFORE $RegWr = 1$
- There is a “race” between Rw (address) and $RegWr$ (write enable)



- The “real” (no clock input) memory may not work reliably in the single cycle processor because:

 - We cannot guarantee Address will be stable BEFORE $WrEn = 1$
- There is a race between Adr and $WrEn$




How to Avoid this Race Condition?

- **Solution for the multiple cycle implementation:**
 - **Make sure Address is stable by the end of Cycle N**
 - **Assert Write Enable signal ONE cycle later at Cycle (N + 1)**
 - **Address cannot change until Write Enable is disasserted**

Dual-Port Ideal Memory

- Dual Port Ideal Memory
 - Independent Read (RAdr, Dout) and Write (WAdr, Din) ports
 - Read and write (to different location) can occur at the same cycle
- Read Port is a combinational path:
 - Read Address Valid -->
 - Memory Read Access Delay -->
 - Data Out Valid
- Write Port is also a combinational path:
 - MemWrite = 1 -->
 - Memory Write Access Delay -->
 - Data In is written into location[WrAdr]

 

Questions and Administrative Matters


Instruction Fetch Cycle: In the Beginning

◦ Every cycle begins right AFTER the clock tick:

- $\text{mem}[\text{PC}] \quad \text{PC} < 31:0 > + 4$





You are here!

 

Instruction Fetch Cycle: The End

- Every cycle ends AT the next clock tick (storage element updates):

 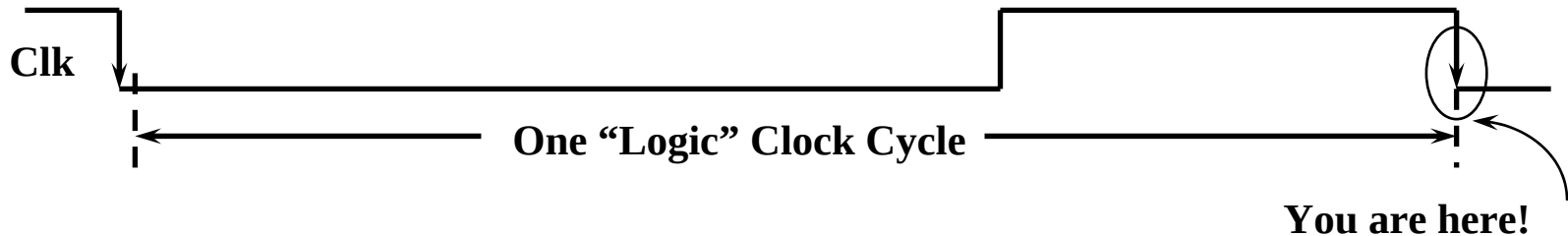
- $IR \leftarrow \text{mem}[\text{PC}] \quad \text{PC} \leftarrow \text{PC} + 4$



Instruction Fetch Cycle: Overall Picture


Ifetch

 ALUOp=Add
1: PCWr, IRWr
x: PCWrCond
RegDst, Mem2R
Others: 0s



Register Fetch / Instruction Decode

 - $\text{busA} \leftarrow \text{RegFile}[\text{rs}] ; \text{busB} \leftarrow \text{RegFile}[\text{rt}] ;$
- ALU is not being used: $\text{ALUctr} = \text{xx}$



Register Fetch / Instruction Decode (Continue)

- $\text{busA} \leftarrow \text{Reg}[\text{rs}] ; \text{busB} \leftarrow \text{Reg}[\text{rt}] ;$
- $\text{Target} \leftarrow \text{PC} + \text{SignExt}(\text{Imm16}) * 4$

Rfetch/Decode

ALUOp=Add


1: BrWr, ExtOp

ALUSelB=10

x: RegDst, PCSrc

IorD, MemtoReg

Others: 0s

 


Branch Completion

- if (busA == busB)
 - PC <- Target


BrComplete

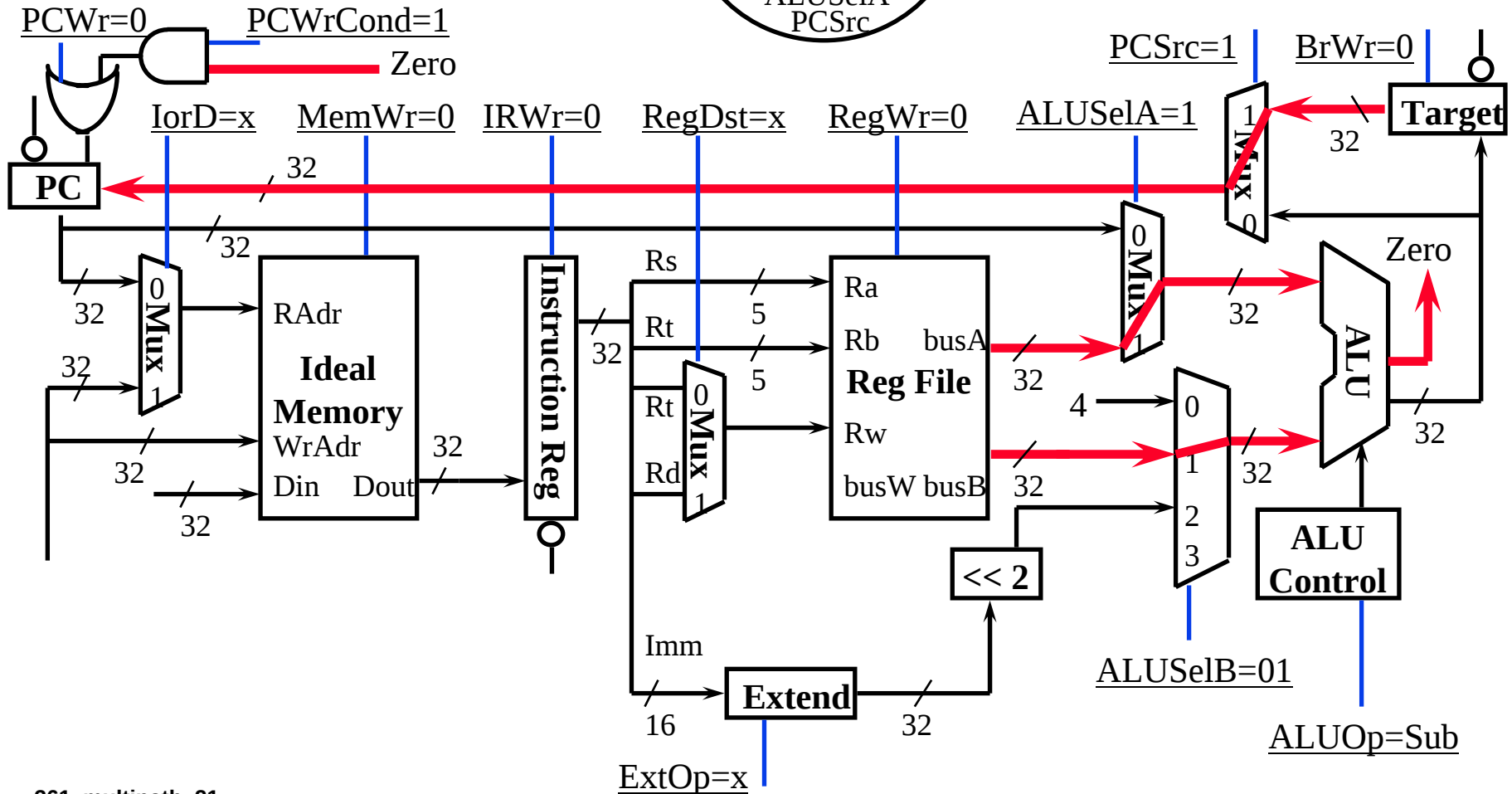ALUOp=Sub
ALUSelB=01
x: IorD, Mem2Reg
RegDst, ExtOp
1: PCWrCond
ALUSelA
PCSrc



Instruction Decode: We have a R-type!

◦ Next Cycle: R-type Execution

 


R-type Execution

° ALU Output <- busA op busB

RExec

 1: RegDst
ALUSelA
ALUSelB=01
ALUOp=Rtype
x: PCSrc, IorD
MemtoReg
ExtOp




R-type Completion

- ° $R[rd] \leftarrow \text{ALU Output}$

Rfinish

 
ALUOp=Rtype
1: RegDst, RegWr
ALUSelA
ALUSelB=01
x: IorD, PCSrc
ExtOp



A Multiple Cycle Delay Path

◦ There is no register to save the results between:

 - Register Fetch: $\text{busA} \leftarrow \text{Reg}[\text{rs}] ; \text{busB} \leftarrow \text{Reg}[\text{rt}]$ —
- R-type Execution: $\text{ALU output} \leftarrow \text{busA op busB}$ —
- R-type Completion: $\text{Reg}[\text{rd}] \leftarrow \text{ALU output}$ —




A Multiple Cycle Delay Path (Continue)

- Register is NOT needed to save the outputs of Register Fetch:
 - $IRWr = 0$: busA and busB will not change after Register Fetch
- Register is NOT needed to save the outputs of R-type Execution:
 - busA and busB will not change after Register Fetch
 - Control signals $ALUSelA$, $ALUSelB$, and $ALUOp$ will not change after R-type Execution
 - Consequently ALU output will not change after R-type Execution
- In theory (P. 316, P&H), you need a register to hold a signal value if:
 - (1) The signal is computed in one clock cycle and used in another.
 - (2) AND the inputs to the functional block that computes this signal can change before the signal is written into a state element.
- You can save a register if Cond 1 is true BUT Cond 2 is false:
 - But in practice, this will introduce a multiple cycle delay path:
 - A logic delay path that takes multiple cycles to propagate from one storage element to the next storage element

Pros and Cons of a Multiple Cycle Delay Path

 
- A 3-cycle path example:
 - IR (storage) -> Reg File Read -> ALU -> Reg File Write (storage)
- Advantages:
 - Register savings
 - We can share time among cycles:
 - If ALU takes longer than one cycle, still “a OK” as long as the entire path takes less than 3 cycles to finish



Pros and Cons of a Multiple Cycle Delay Path (Continue)


- **Disadvantage:**

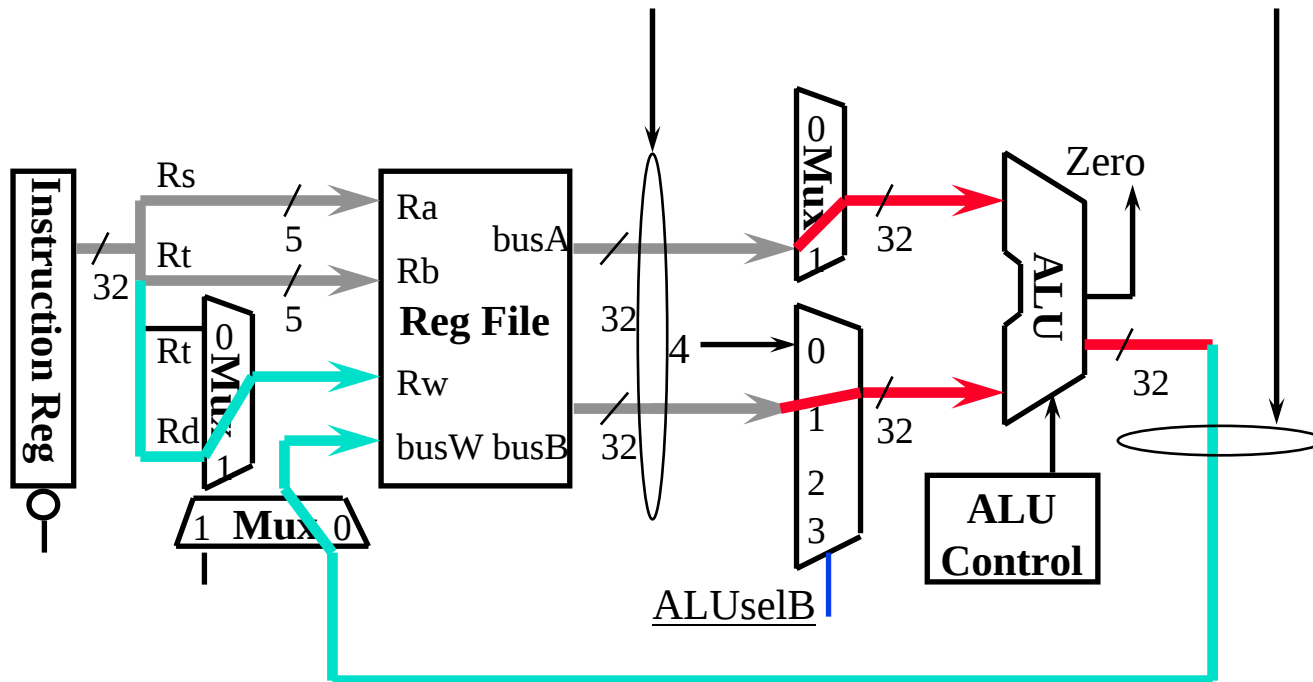- **Static timing analyzer, which ONLY looks at delay between two storage elements, will report this as a timing violation**
- **You have to ignore the static timing analyzer's warnings**



Instruction Decode: We have an Ori!

◦ Next Cycle: Ori Execution

 


Ori Execution

- ALU output $\leftarrow$ busA or ZeroExt[Imm16]

OriExec

 ALUOp=Or
 1: ALUSelA
 ALUSelB=11
 x: MemtoReg
 IorD, PCSrc



Ori Completion

◦ $\text{Reg}[rt] \leftarrow \text{ALU output}$


OriFinish

ALUOp=Or

x: IorD, PCSrc

ALUSelB=11

1: ALUSelA
RegWr

 


Memory Address Calculation

° ALU output <- busA + SignExt[Imm16]


AdrCal

 1: ExtOp
ALUSelA
ALUSelB=11
ALUOp=Add
x: MemtoReg
PCSrc



Memory Access for Store

 
◦ $\text{mem}[\text{ALU output}] \leftarrow \text{busB}$



Memory Access for Load


◦ Mem Dout <- mem[ALU output]

 1: ExtOp
ALUSelA, IorD
ALUSelB=11
ALUOp=Add
x: MemtoReg
PCSrc




Write Back for Load

 
◦ $\text{Reg}[rt] \leftarrow \text{Mem Dout}$



 Putting it all together: Multiple Cycle Datapath



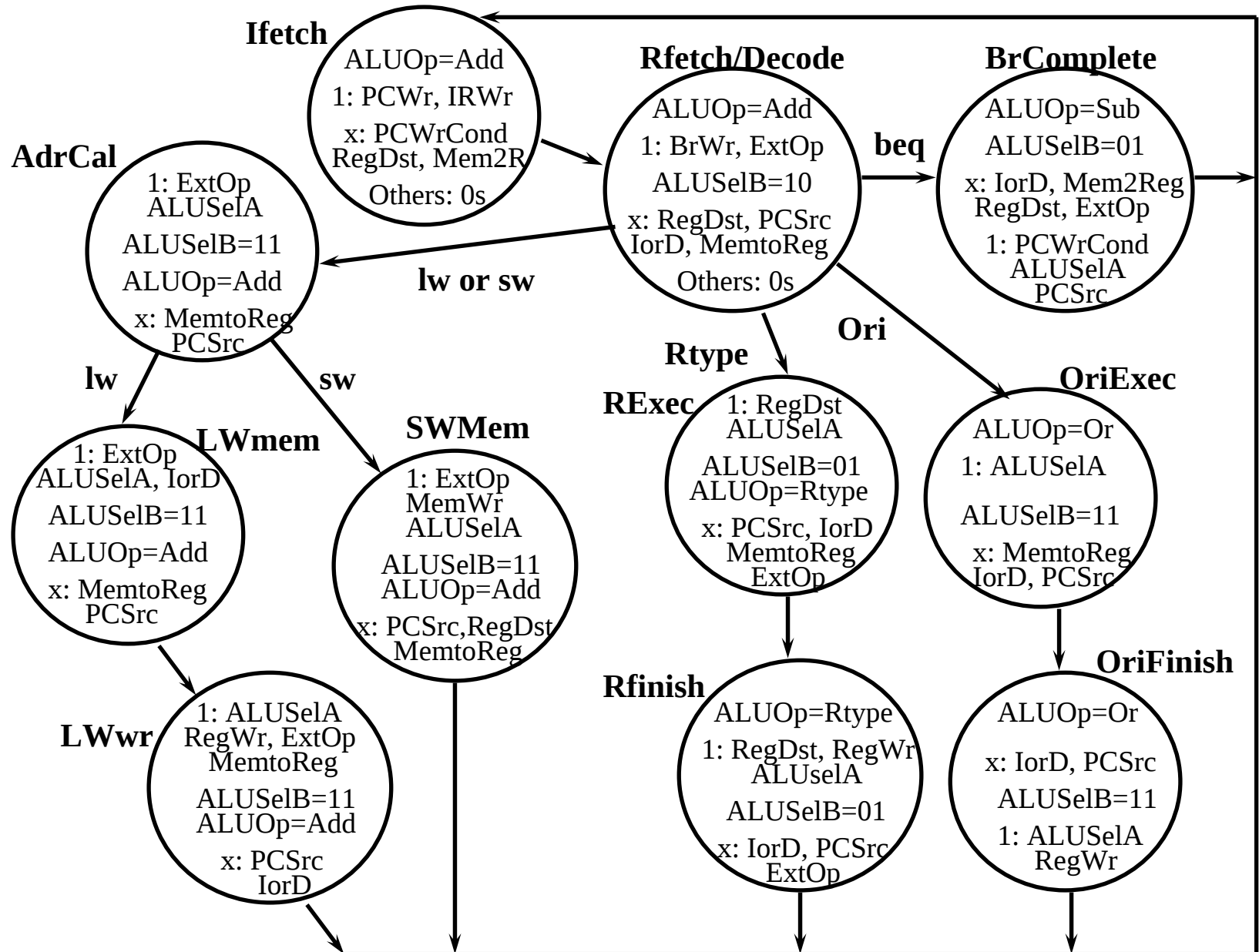Putting it all together: Control State Diagram



Summary

- **Disadvantages of the Single Cycle Processor**
 - Long cycle time
 - Cycle time is too long for all instructions except the Load
- **Multiple Cycle Processor:**
 - Divide the instructions into smaller steps
 - Execute each step (instead of the entire instruction) in one cycle
- **Do NOT confuse Multiple Cycle Processor with Multiple Cycle Delay Path**
 - Multiple Cycle Processor executes each instruction in multiple clock cycles
 - Multiple Cycle Delay Path: a combinational logic path between two storage elements that takes more than one clock cycle to complete
- **It is possible (desirable) to build a MC Processor without MCDP:**
 - Use a register to save a signal's value whenever a signal is generated in one clock cycle and used in another cycle later