


EECS 361
Computer Architecture
Lecture 12: Designing a Pipeline Processor

Overview of a Multiple Cycle Implementation

- **The root of the single cycle processor's problems:**
 - **The cycle time has to be long enough for the slowest instruction**
- **Solution:**
 - **Break the instruction into smaller steps**
 - **Execute each step (instead of the entire instruction) in one cycle**
 - **Cycle time: time it takes to execute the longest step**
 - **Keep all the steps to have similar length**
 - **This is the essence of the multiple cycle processor**
- **The advantages of the multiple cycle processor:**
 - **Cycle time is much shorter**
 - **Different instructions take different number of cycles to complete**
 - **Load takes five cycles**
 - **Jump only takes three cycles**
 - **Allows a functional unit to be used more than once per instruction**

Multiple Cycle Processor

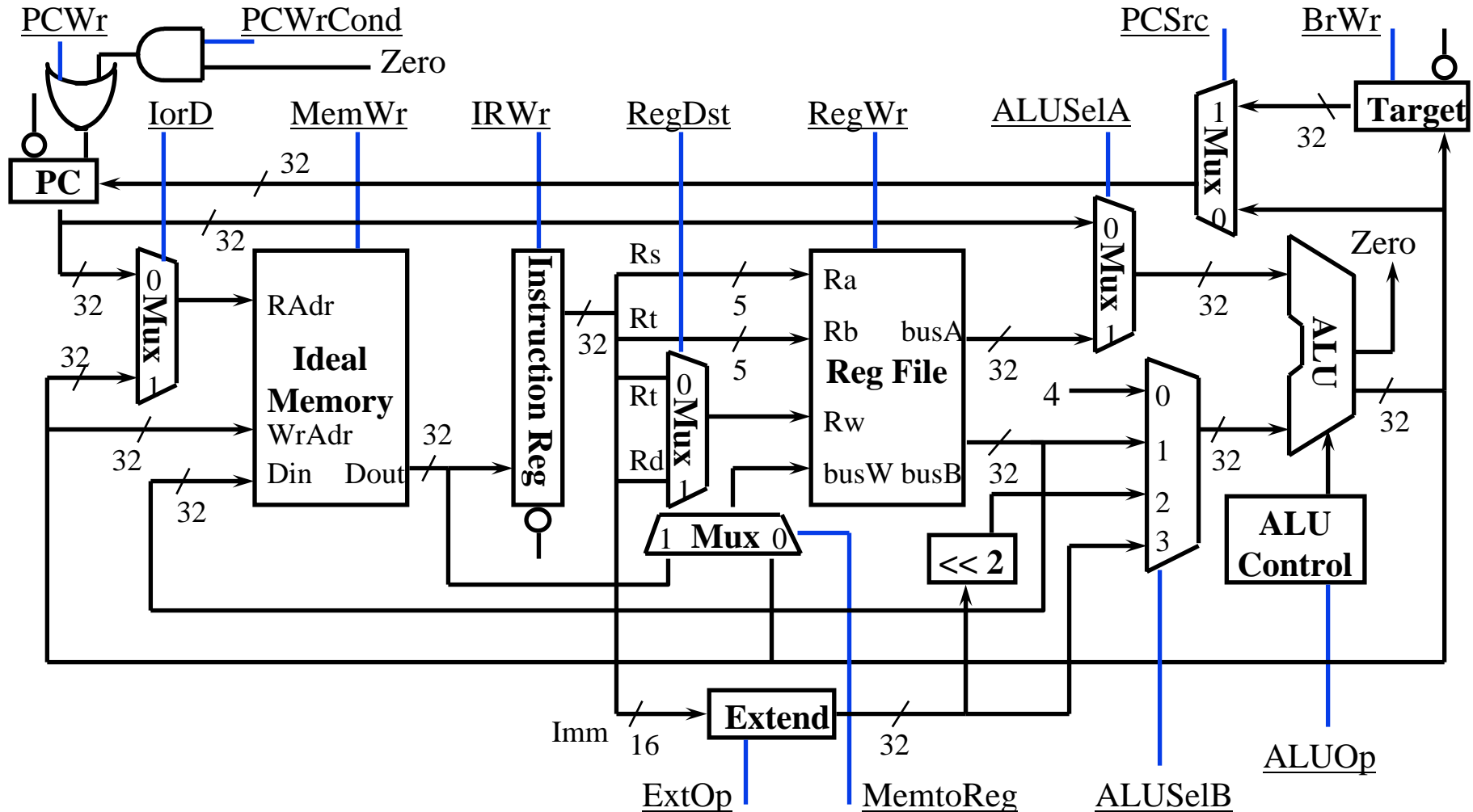- MCP: A functional unit to be used more than once per instruction






Outline of Today's Lecture


- **Recap and Introduction**
- **Introduction to the Concept of Pipelined Processor**
- **Pipelined Datapath and Pipelined Control**
- **How to Avoid Race Condition in a Pipeline Design?**
- **Pipeline Example: Instructions Interaction**
- **Summary**

Pipelining is Natural!

   - **Laundry Example**
- **Sammy, Marc, Griffy, Albert each have one load of clothes to wash, dry, and fold**
- **Washer takes 30 minutes**
- **Dryer takes 30 minutes**
- **“Folder” takes 30 minutes**
- **“Stasher” takes 30 minutes to put clothes into drawers**




Sequential Laundry

 


◦ If they learned pipelining, how long would laundry take?

Pipelined Laundry: Start work ASAP

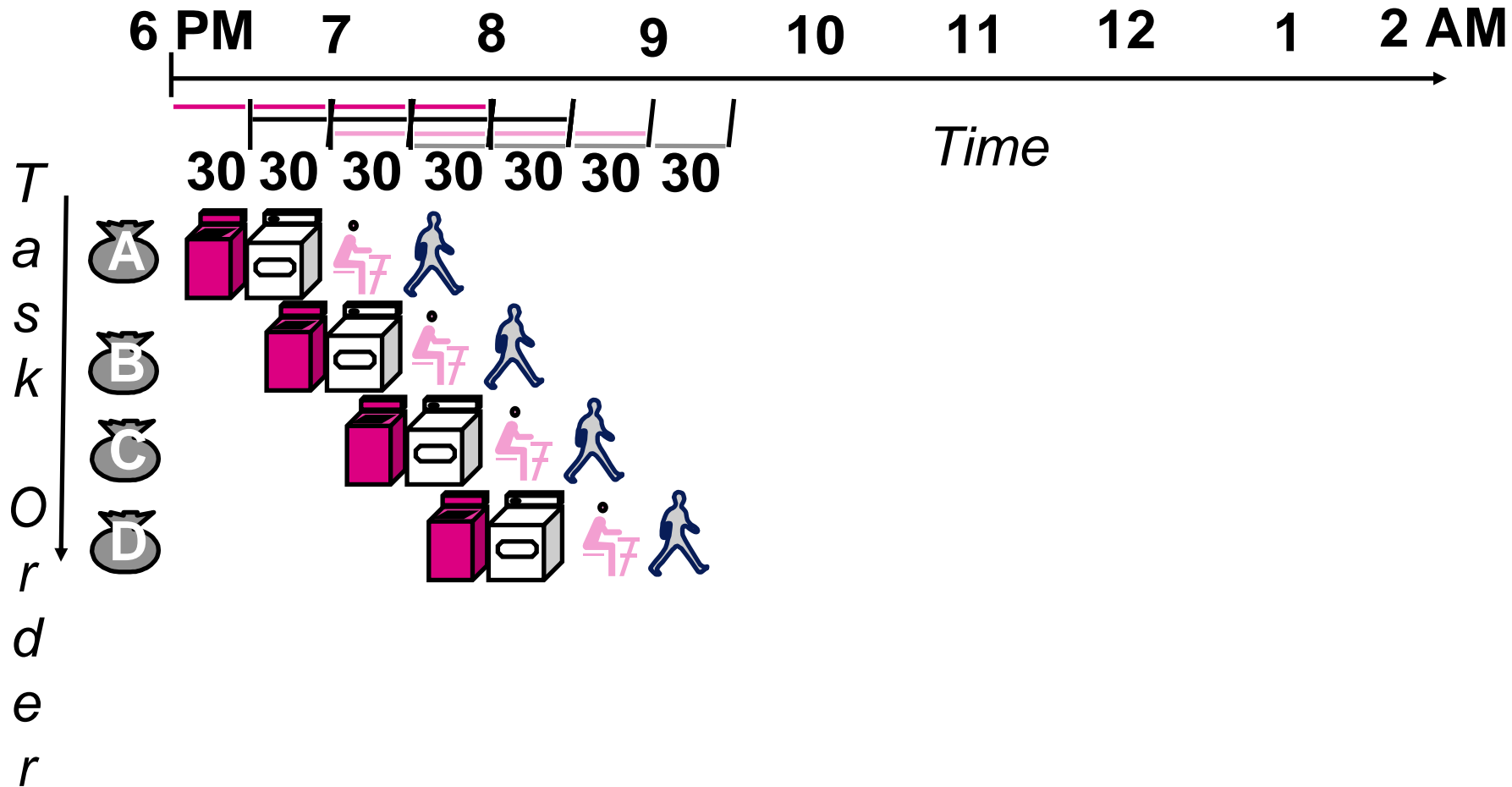

◦ **Pipelined laundry takes 3.5 hours for 4 loads!**

Pipelining Lessons

 


- Pipelining doesn't help **latency** of single task, it helps **throughput** of entire workload
- **Multiple** tasks operating simultaneously using different resources
- Potential speedup = **Number pipe stages**
- Pipeline rate limited by **slowest** pipeline stage
- Unbalanced lengths of pipe stages reduces speedup
- Time to “**fill**” pipeline and time to “**drain**” it reduces speedup
- Stall for Dependences


Why Pipeline?

- Suppose we execute 100 instructions
- Single Cycle Machine
 - $45 \text{ ns/cycle} \times 1 \text{ CPI} \times 100 \text{ inst} = 4500 \text{ ns}$
- Multicycle Machine
 - $10 \text{ ns/cycle} \times 4.6 \text{ CPI (due to inst mix)} \times 100 \text{ inst} = 4600 \text{ ns}$
- Ideal pipelined machine
 - $10 \text{ ns/cycle} \times (1 \text{ CPI} \times 100 \text{ inst} + 4 \text{ cycle drain}) = 1040 \text{ ns}$

Timing Diagram of a Load Instruction

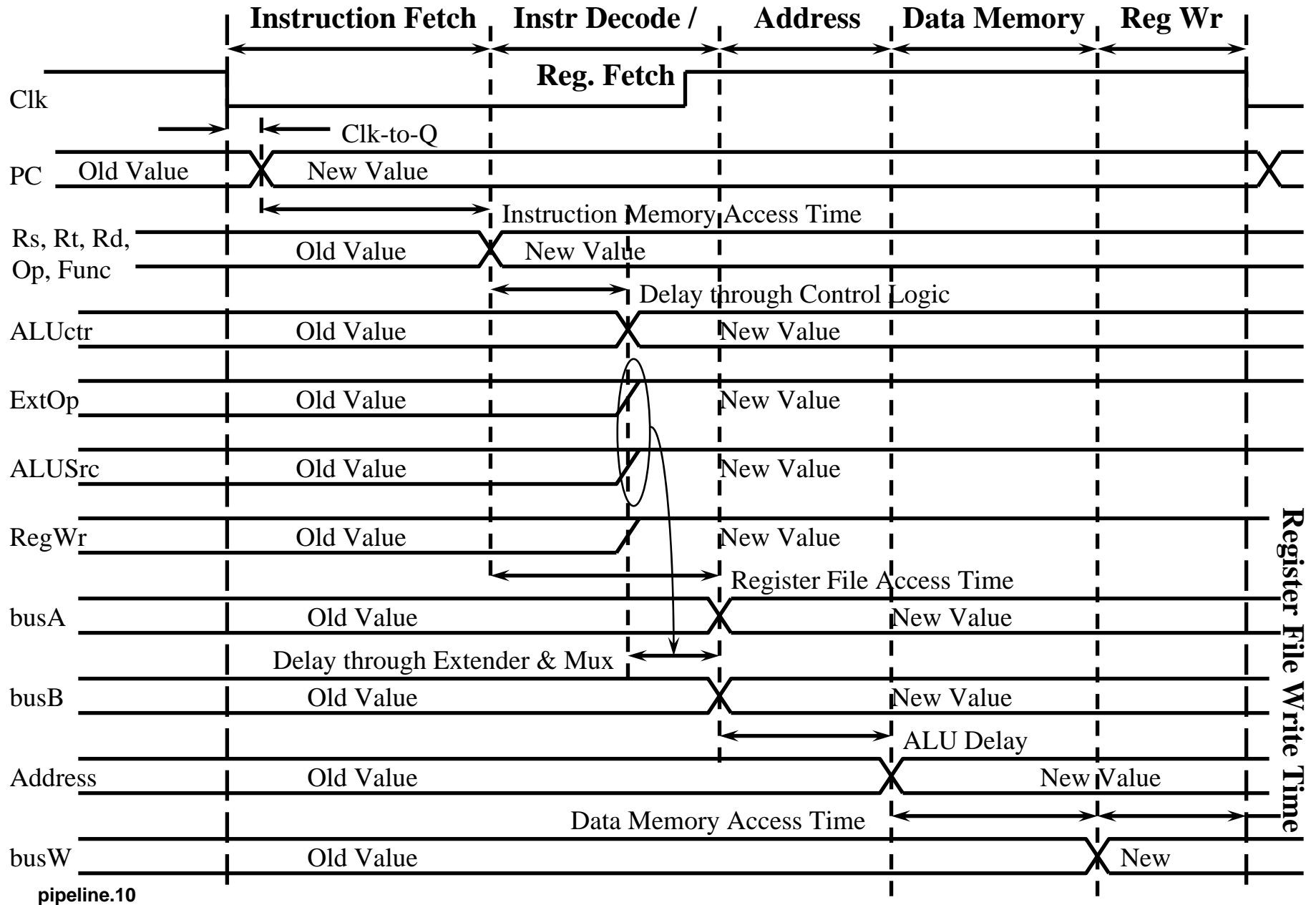


The Five **Stages** of Load

 


- **Ifetch: Instruction Fetch**
 - Fetch the instruction from the Instruction Memory
- **Reg/Dec: Registers Fetch and Instruction Decode**
- **Exec: Calculate the memory address**
- **Mem: Read the data from the Data Memory**
- **Wr: Write the data back to the register file**

Pipelining the Load Instruction

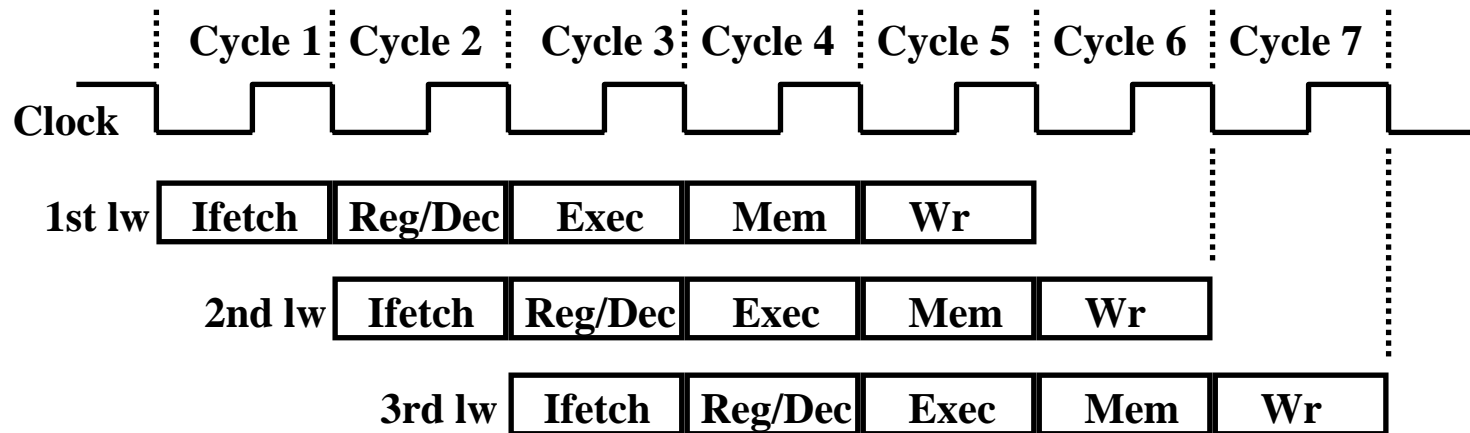


- The five independent functional units in the pipeline datapath are:
 - Instruction Memory for the Ifetch stage
 - Register File's Read ports (bus A and busB) for the Reg/Dec stage
 - ALU for the Exec stage
 - Data Memory for the Mem stage
 - Register File's Write port (bus W) for the Wr stage
- One instruction enters the pipeline every cycle
 - One instruction comes out of the pipeline (complete) every cycle
 - The "Effective" Cycles per Instruction (CPI) is 1

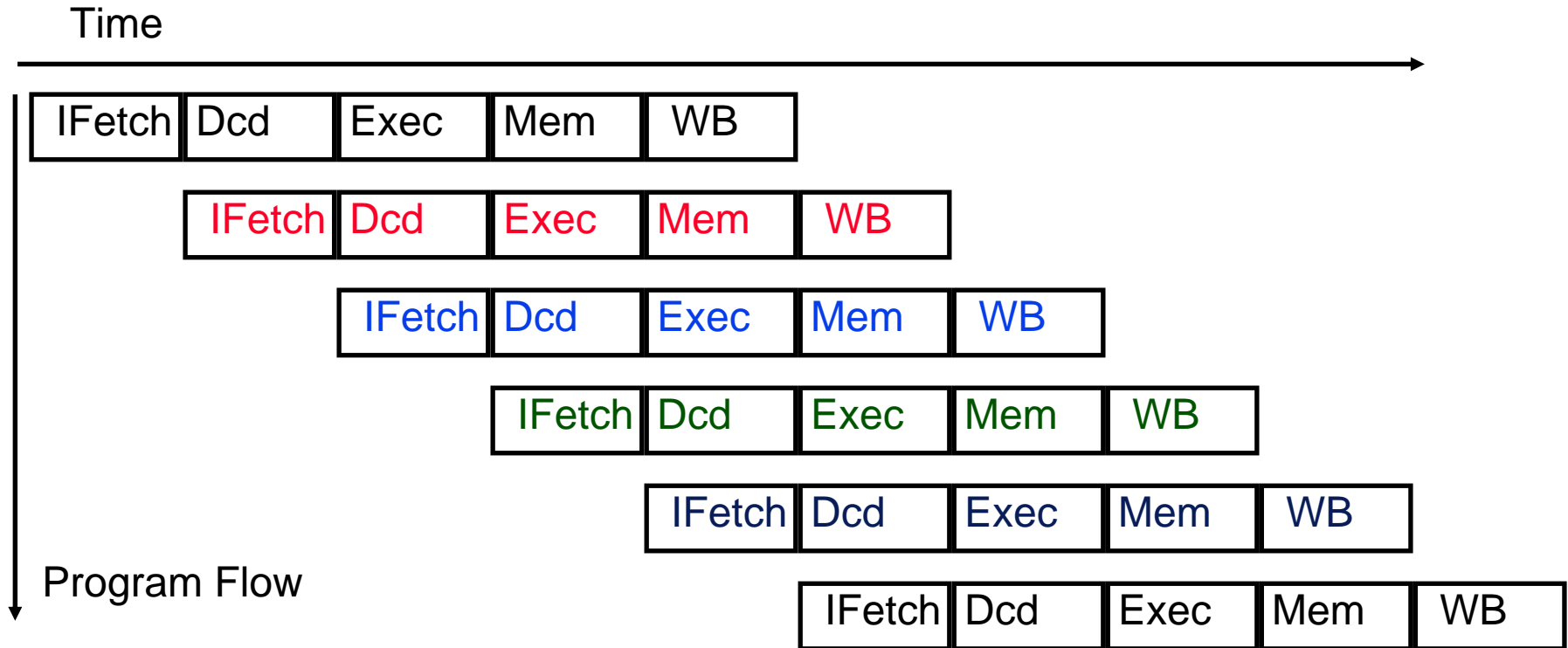
Conventional Pipelined Execution Representation



 
Single Cycle, Multiple Cycle, vs. Pipeline




Single Cycle Implementation:

 


Multiple Cycle Implementation:

 

Pipeline Implementation:

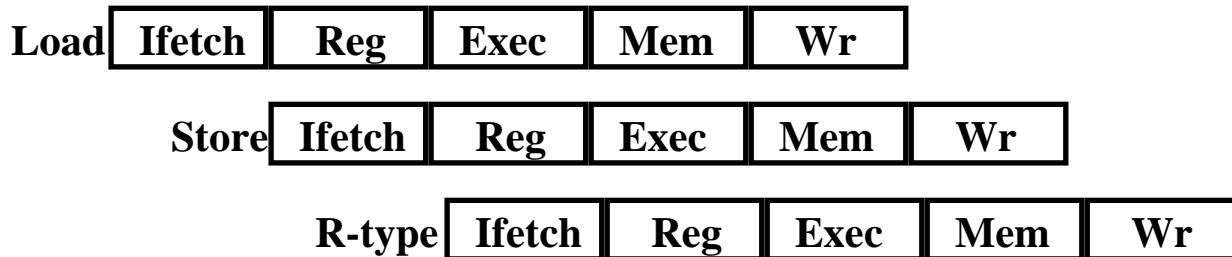

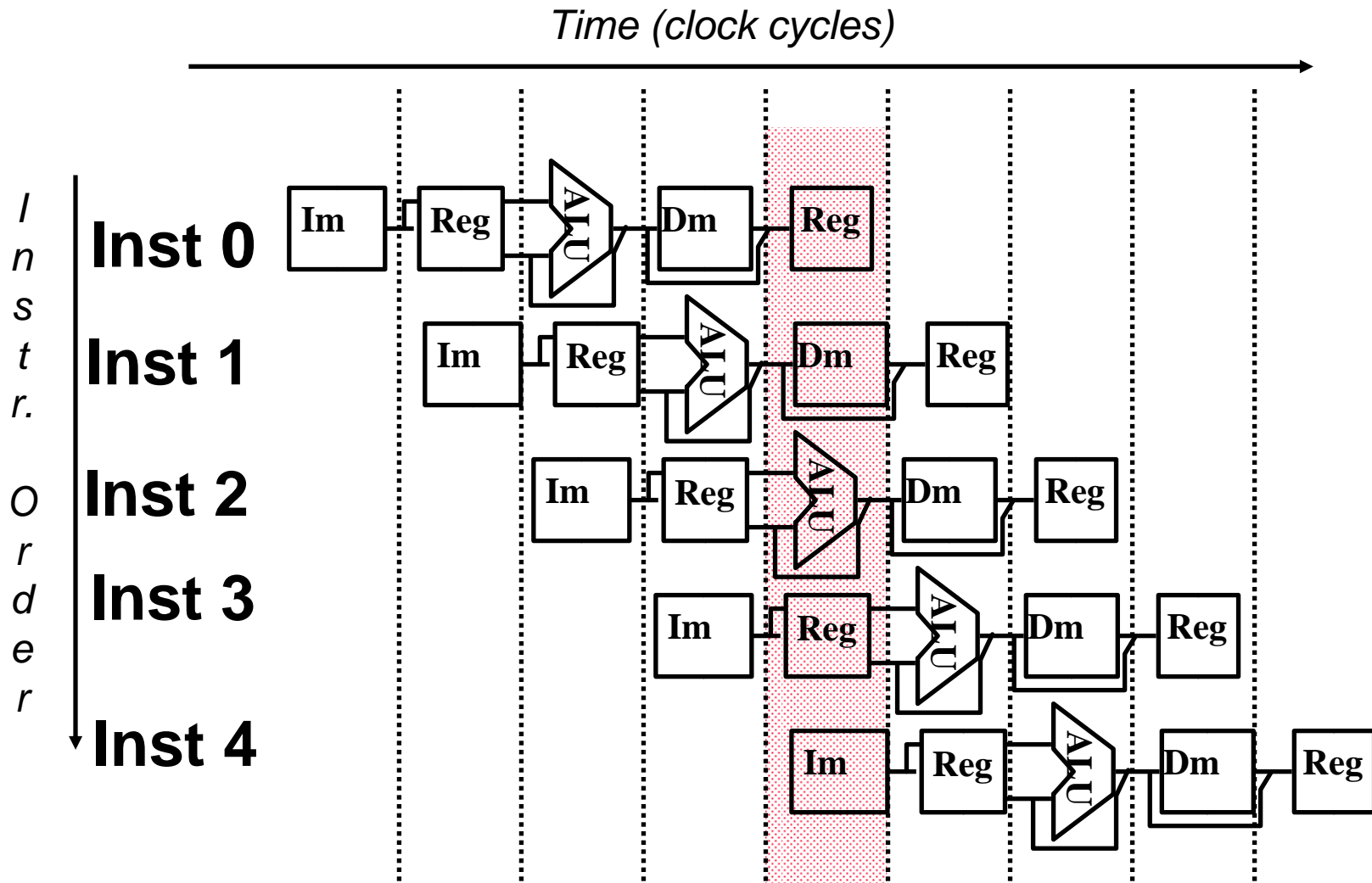Why Pipeline? Because the resources are there!



Can pipelining get us into trouble?


- Yes: **Pipeline Hazards**

- **structural hazards**: attempt to use the same resource two different ways at the same time
 - E.g., combined washer/dryer would be a structural hazard or folder busy doing something else (watching TV)
- **data hazards**: attempt to use item before it is ready
 - E.g., one sock of pair in dryer and one in washer; can't fold until get sock from washer through dryer
 - instruction depends on result of prior instruction still in the pipeline
- **control hazards**: attempt to make a decision before condition is evaluated
 - E.g., washing football uniforms and need to get proper detergent level; need to see after dryer before next load in
 - branch instructions

- Can always resolve hazards by **waiting**

- pipeline control must detect the hazard
- take action (or delay action) to resolve hazards

Single Memory is a Structural Hazard

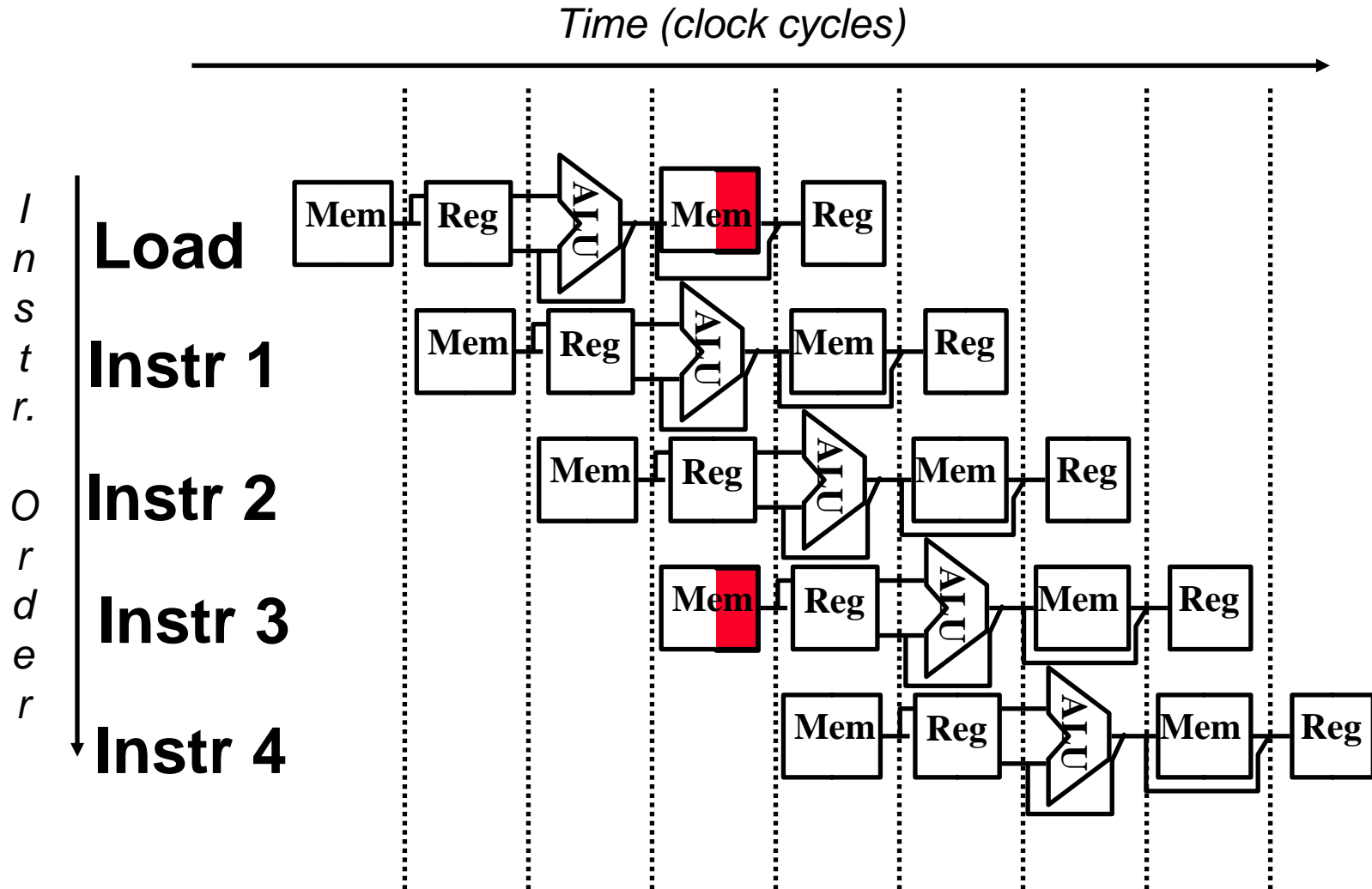


Detection is easy in this case! (right half highlight means read, left half write)

Structural Hazards limit performance

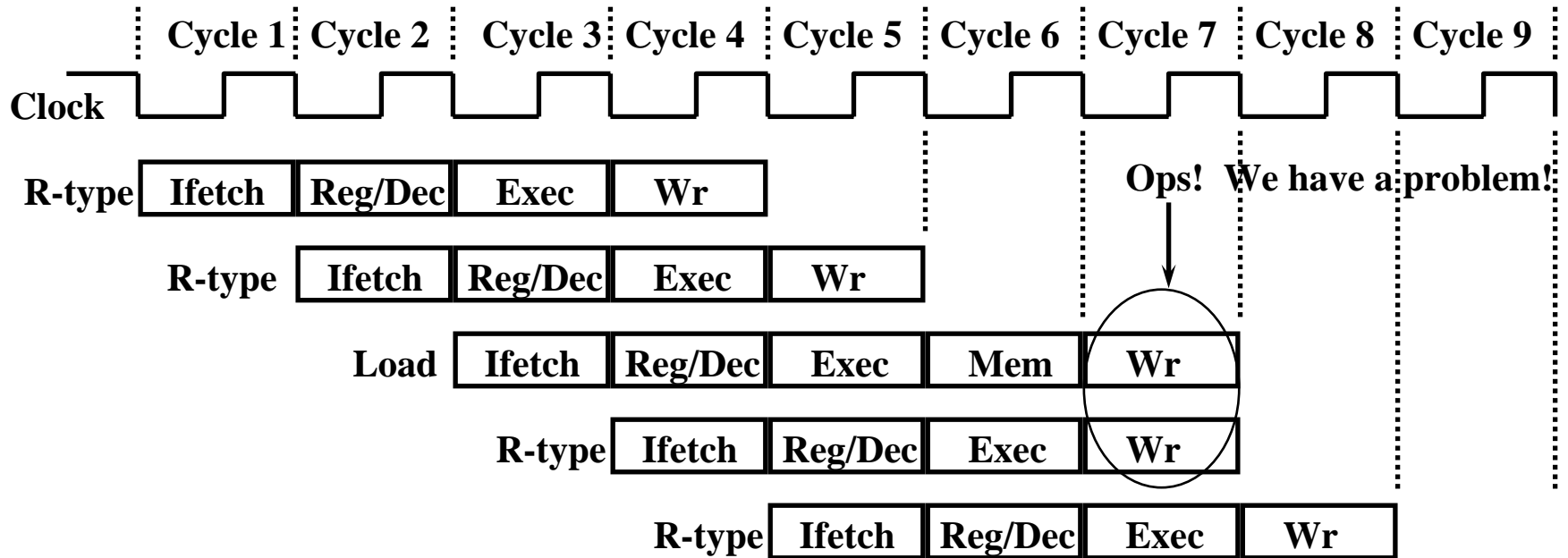
- **Example: if 1.3 memory accesses per instruction and only one memory access per cycle then**
 - **average CPI 1.3**
 - **otherwise resource is more than 100% utilized**
 - **More on Hazards later**

Pipelining the R-type and Load Instruction



- We have a problem:
 - Two instructions try to write to the register file at the same time!


The Four Stages of R-type

 


- **Ifetch: Instruction Fetch**
 - **Fetch the instruction from the Instruction Memory**
- **Reg/Dec: Registers Fetch and Instruction Decode**
- **Exec: ALU operates on the two register operands**
- **Wr: Write the ALU output back to the register file**

Important Observation

 
- Each functional unit can only be used once per instruction
- Each functional unit must be used at the same stage for all instructions:
 - Load uses Register File's Write Port during its 5th stage



- R-type uses Register File's Write Port during its 4th stage

 


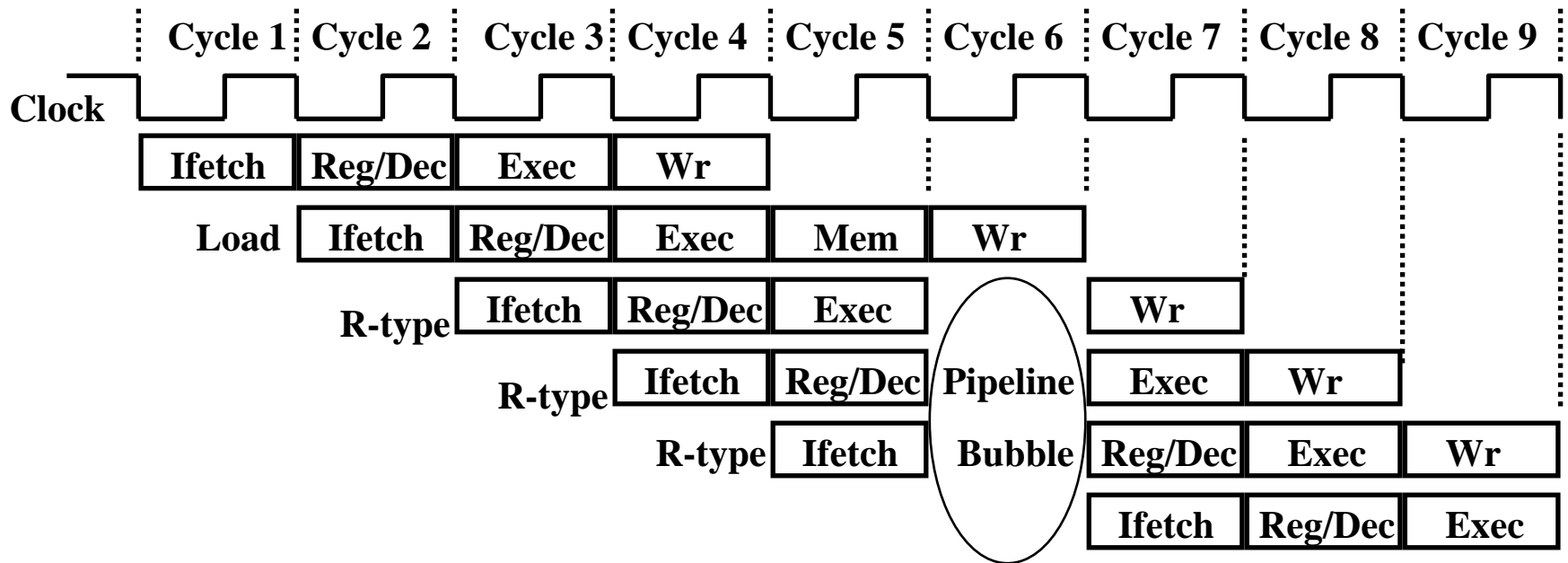
Solution 1: Insert “Bubble” into the Pipeline




- Insert a “bubble” into the pipeline to prevent 2 writes at the same cycle
 - The control logic can be complex
- No instruction is completed during Cycle 5:
 - The “Effective” CPI for load is >1

Solution 2: Delay R-type's Write by One Cycle

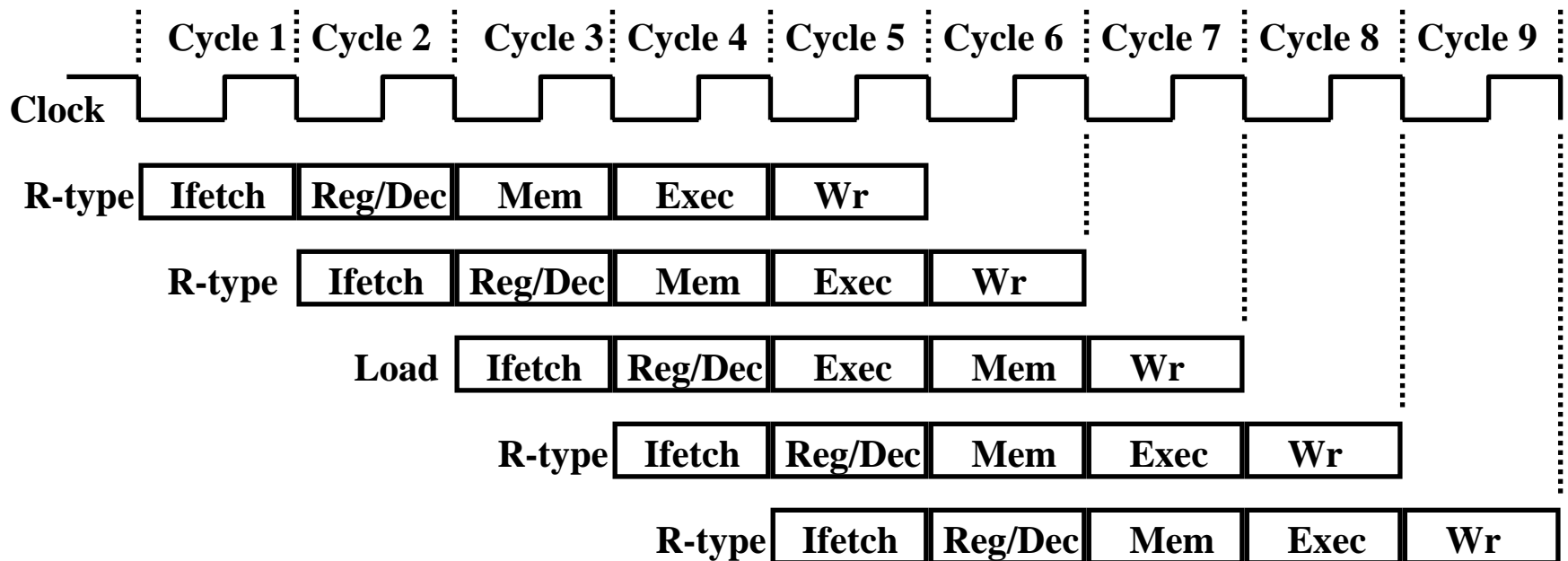 - Delay R-type's register write by one cycle:
 - Now R-type instructions also use Reg File's write port at Stage 5
 - Mem stage is a NOOP stage: nothing is being done




The Four Stages of Store

 


- **Ifetch: Instruction Fetch**
 - Fetch the instruction from the Instruction Memory
- **Reg/Dec: Registers Fetch and Instruction Decode**
- **Exec: Calculate the memory address**
- **Mem: Write the data into the Data Memory**

The Four Stages of Beq

 


- **Ifetch: Instruction Fetch**
 - Fetch the instruction from the Instruction Memory
- **Reg/Dec: Registers Fetch and Instruction Decode**
- **Exec: ALU compares the two register operands**
 - Adder calculates the branch target address
- **Mem: If the registers we compared in the Exec stage are the same,**
 - Write the branch target address into the PC

A Pipelined Datapath

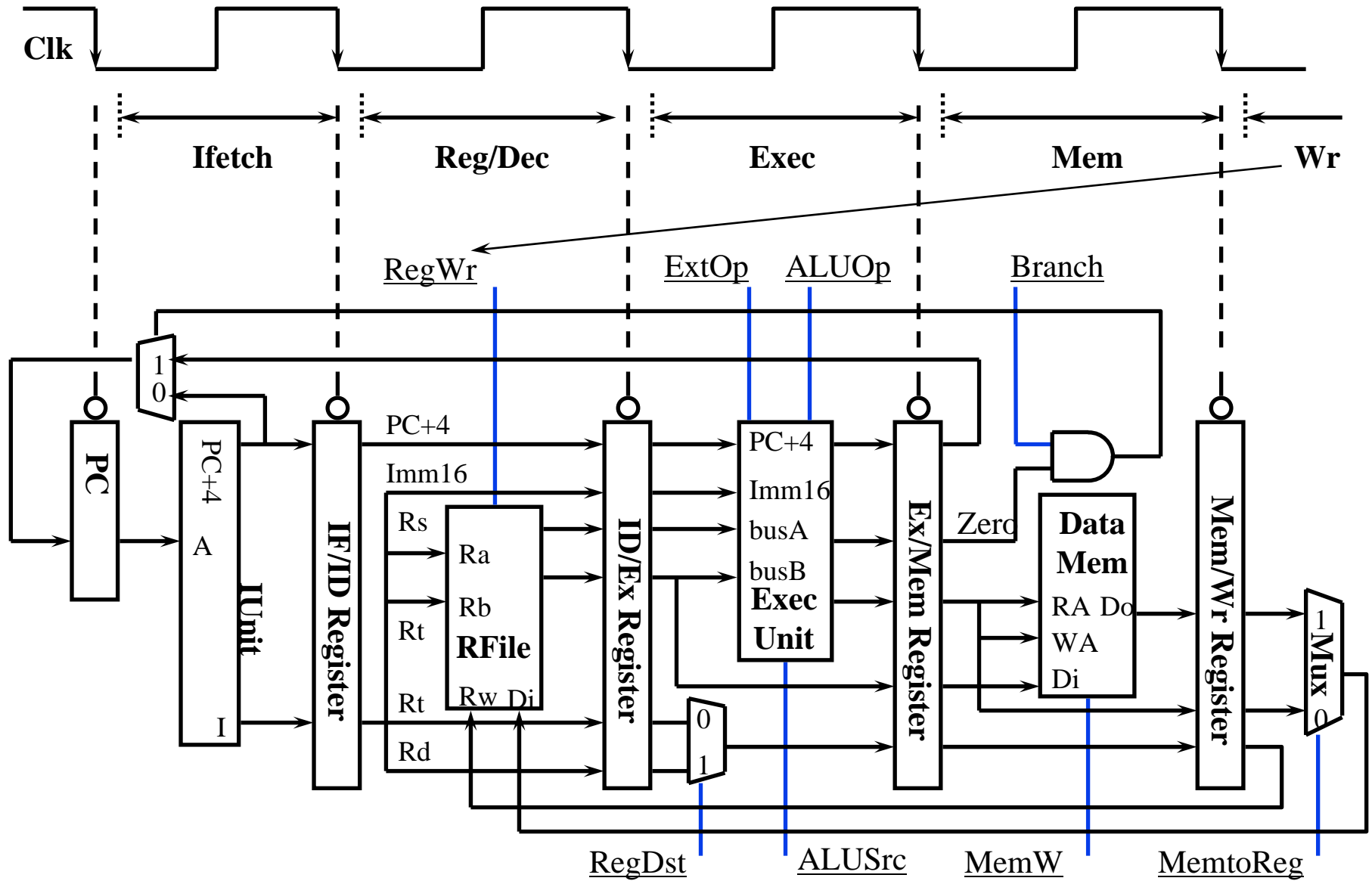


The Instruction Fetch Stage

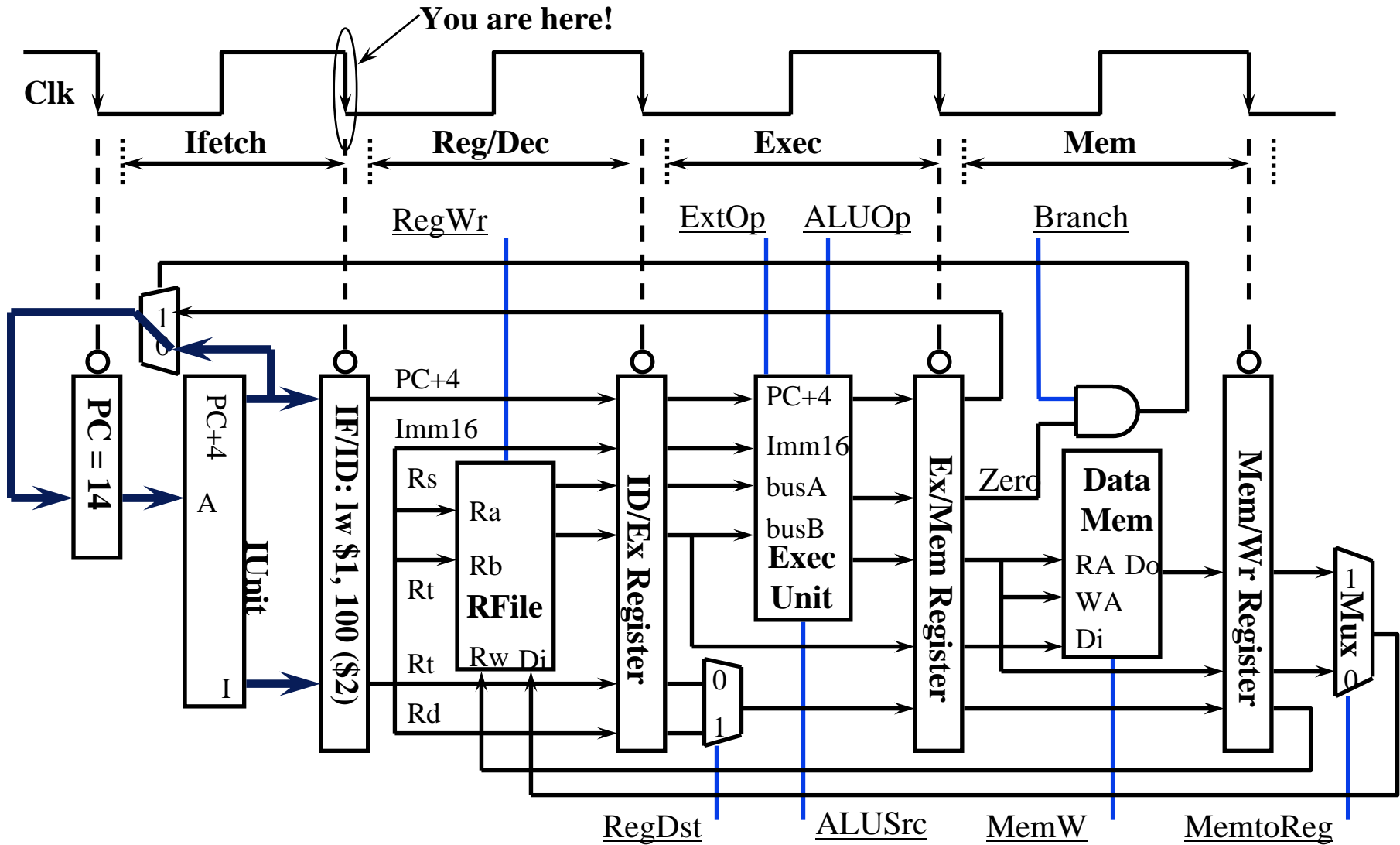◦ Location 10: lw \$1, 0x100(\$2) \$1 <- Mem[(\$2) + 0x100]




A Detail View of the Instruction Unit

- Location 10: lw \$1, 0x100(\$2)

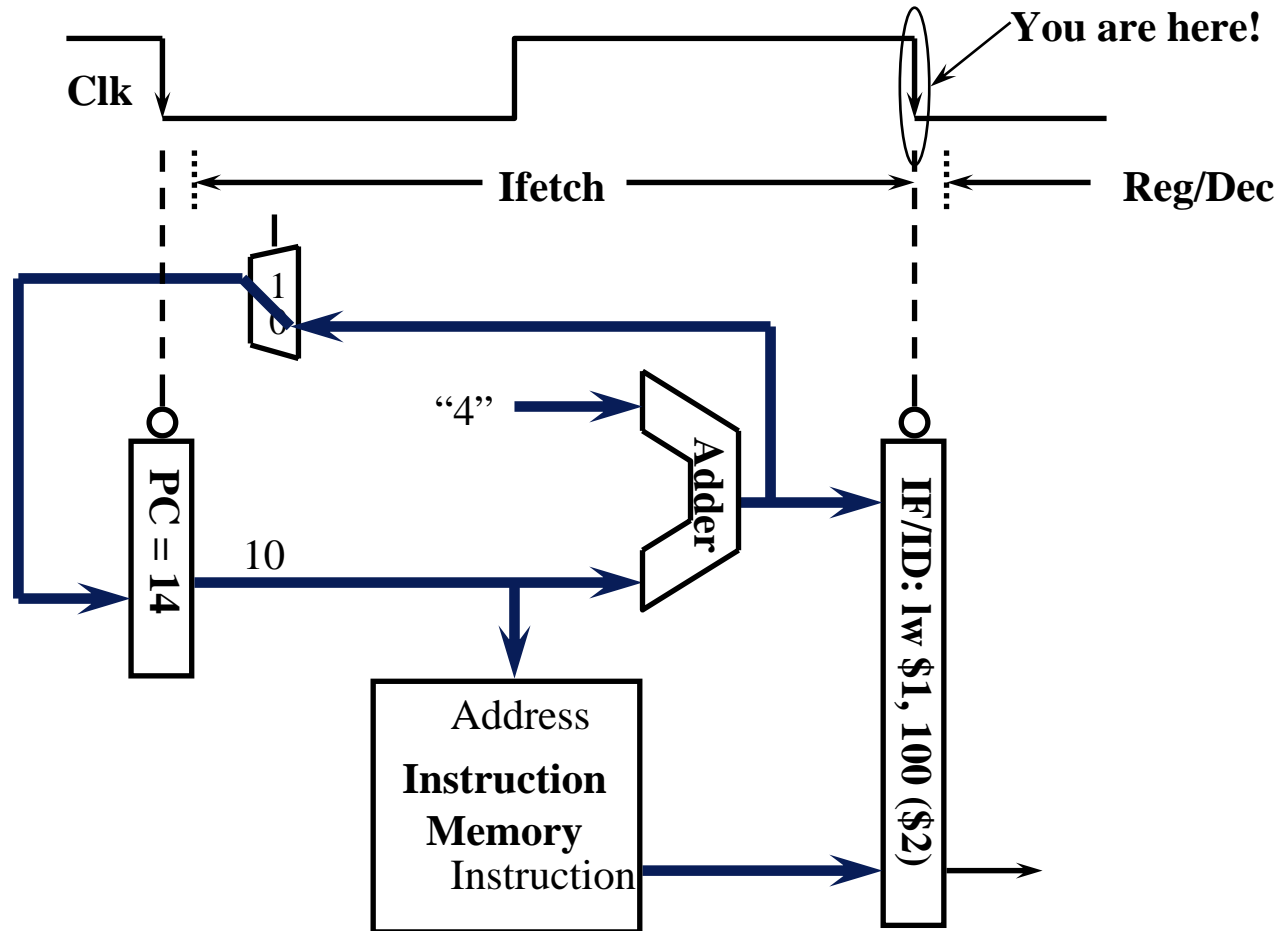


The Decode / Register Fetch Stage

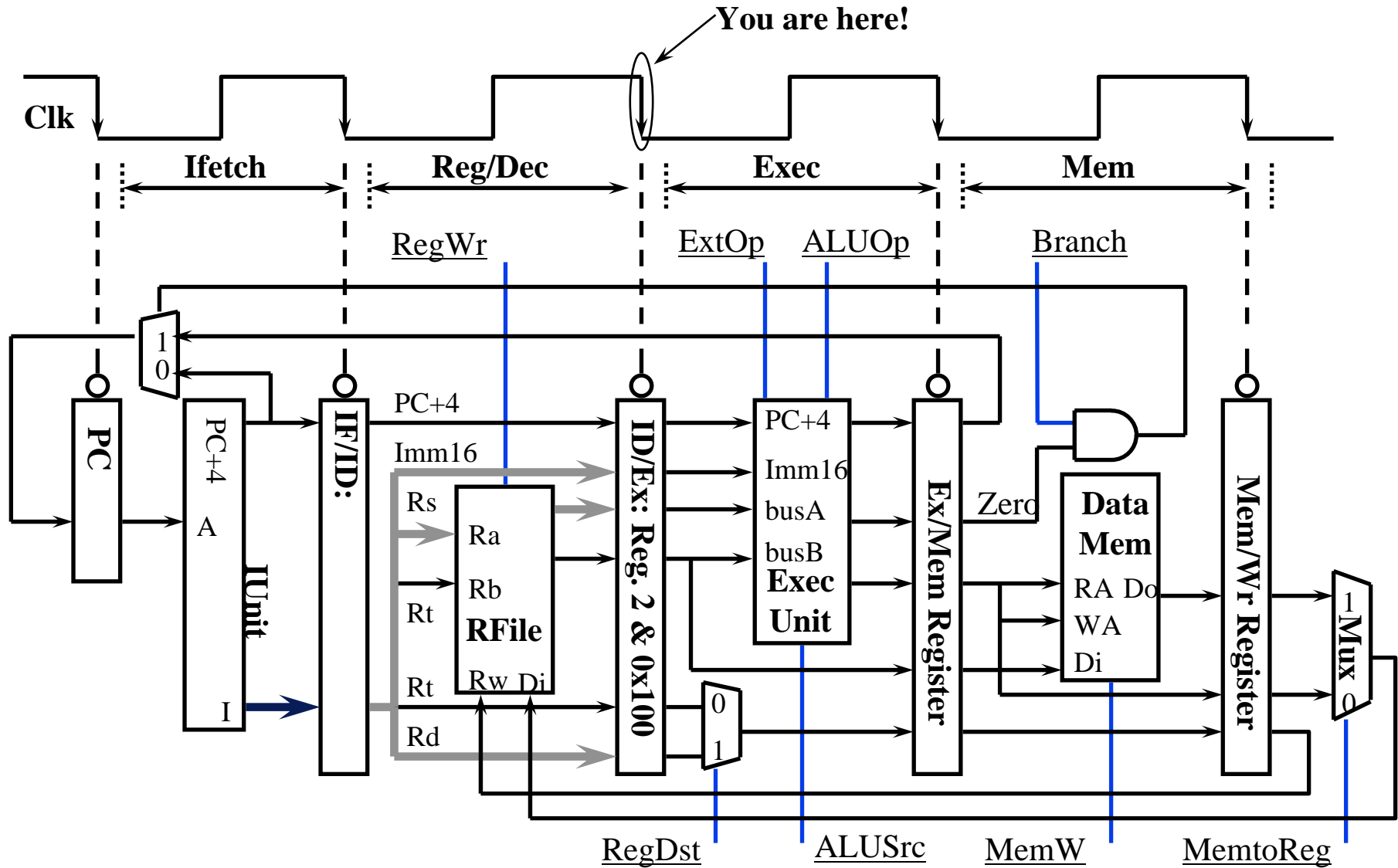◦ Location 10: lw \$1, 0x100(\$2) \$1 <- Mem[(\$2) + 0x100]




Load's Address Calculation Stage

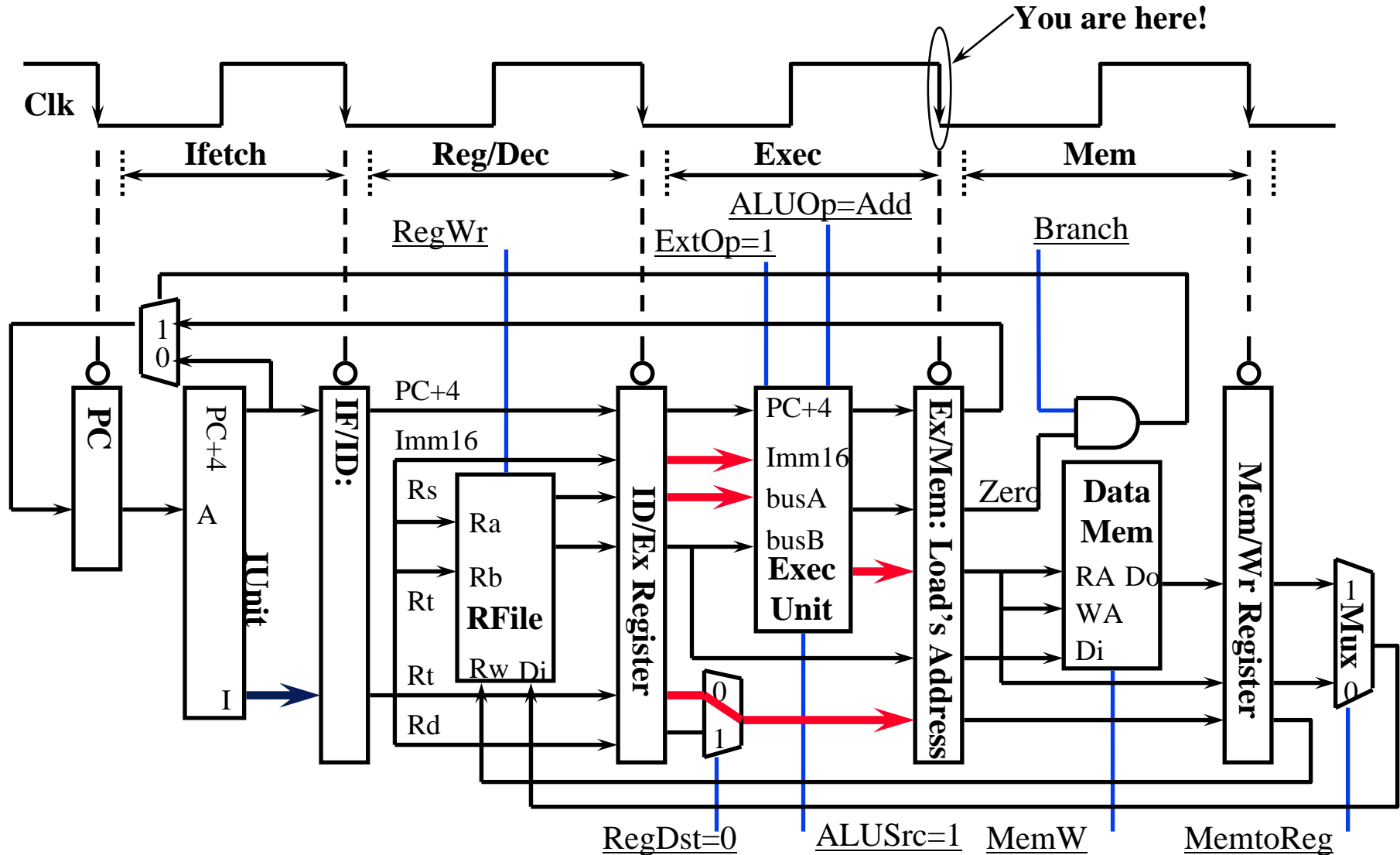◦ Location 10: lw \$1, 0x100(\$2) $\$1 \leftarrow \text{Mem}[(\$2) + 0x100]$




A Detail View of the Execution Unit

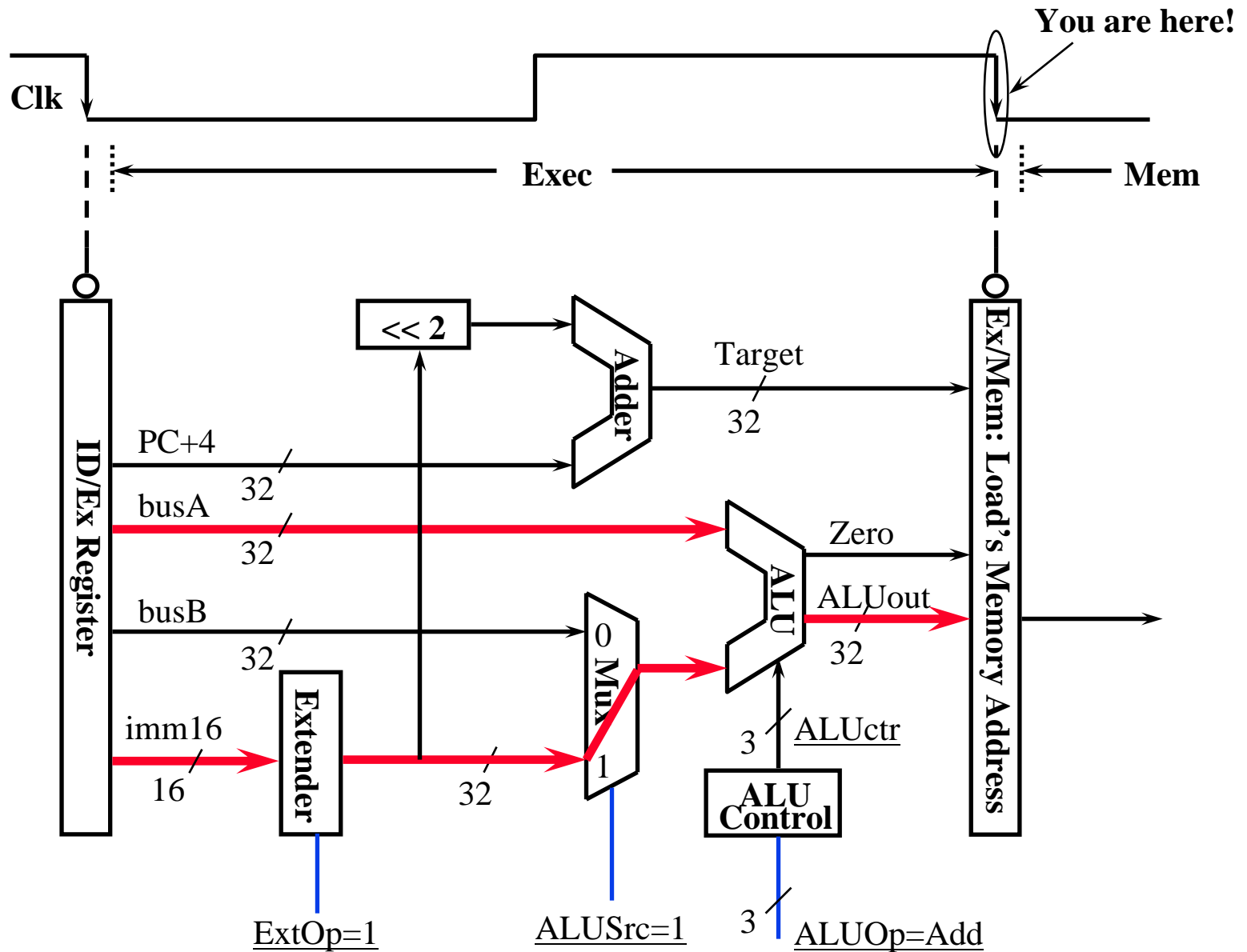

Load's Memory Access Stage


◦ Location 10: lw \$1, 0x100(\$2) \$1 <- Mem[(\$2) + 0x100]

You are here! →

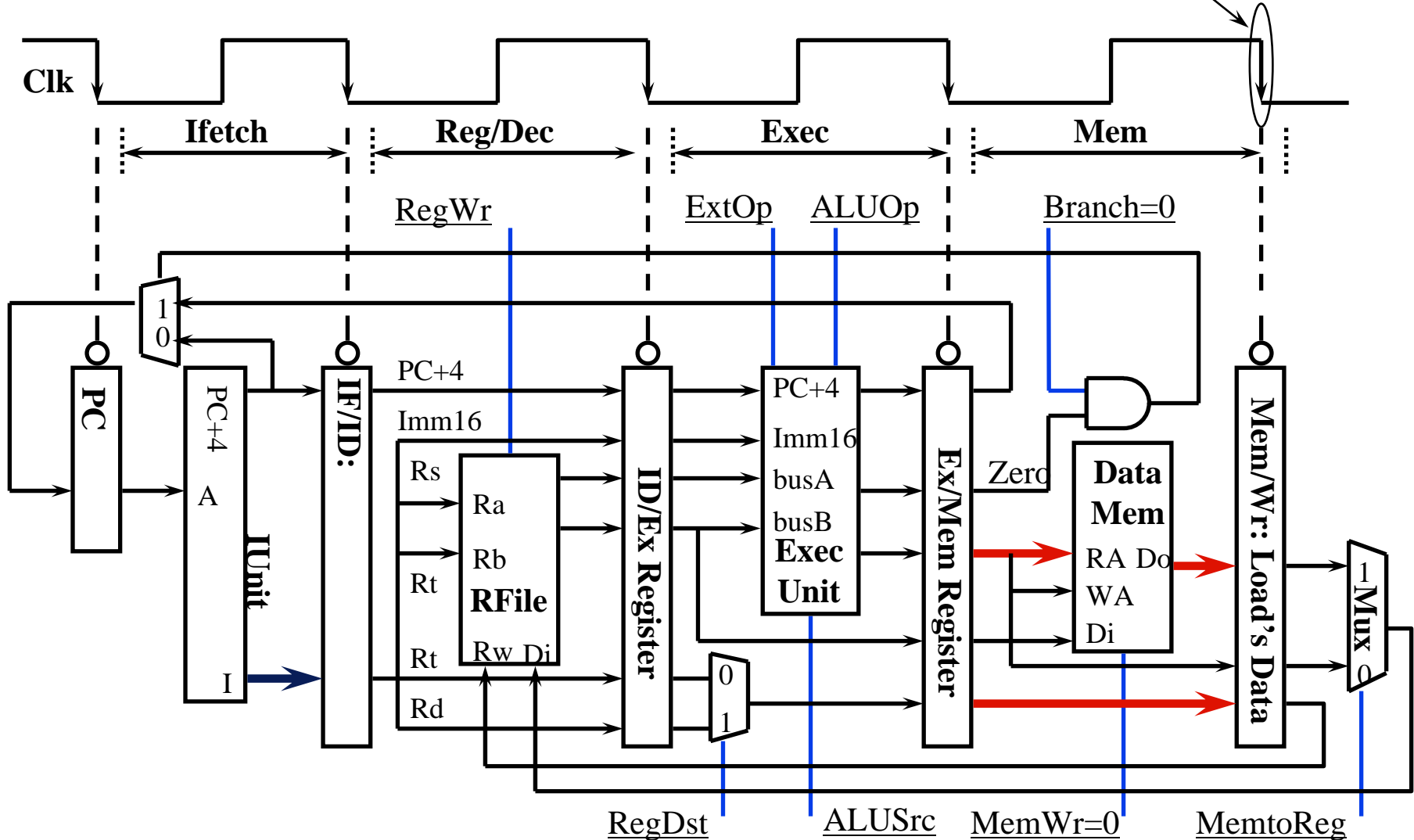


Load's Write Back Stage

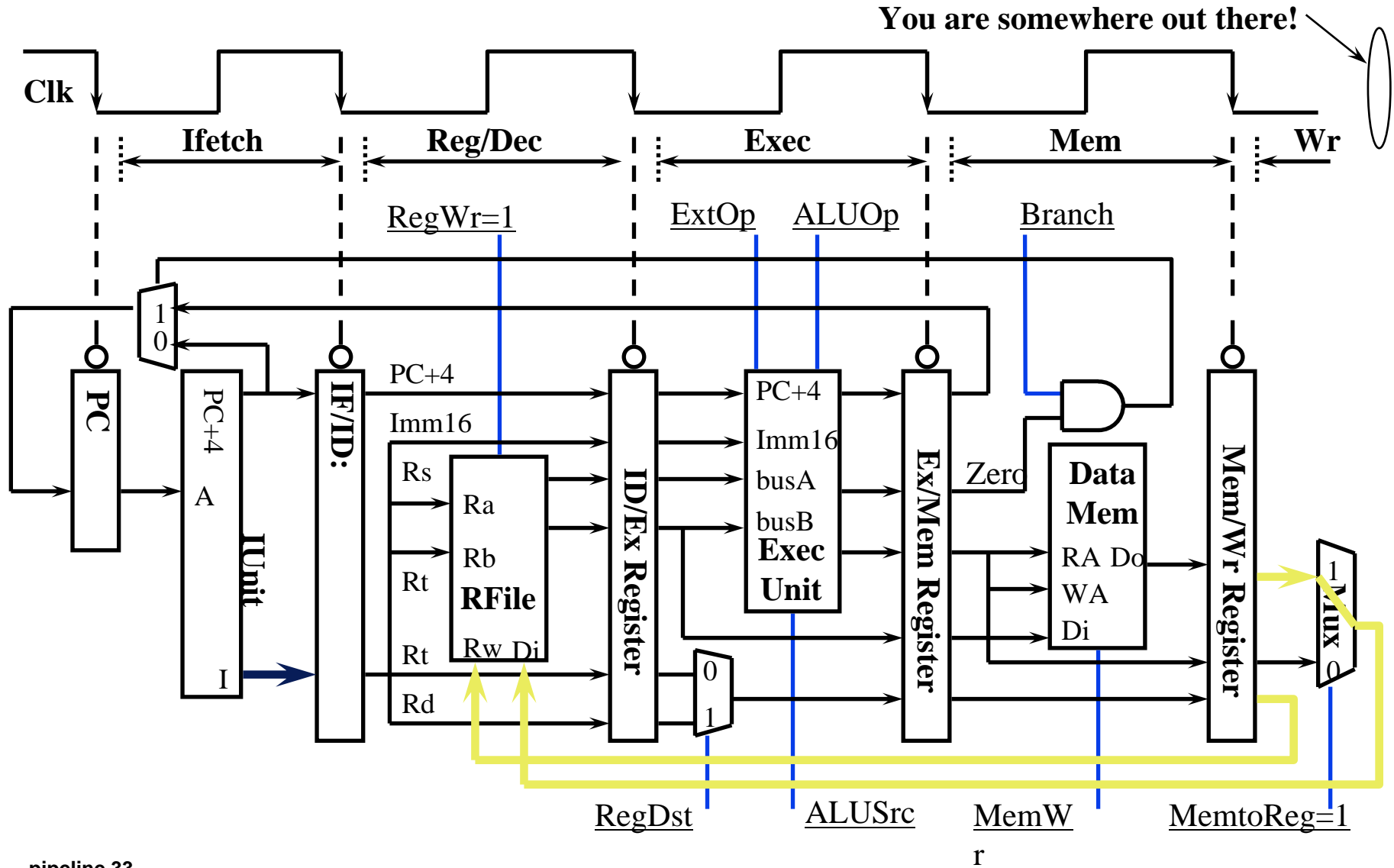◦ Location 10: `lw $1, 0x100($2)` $\$1 \leftarrow \text{Mem}[(\$2) + 0x100]$




How About Control Signals?

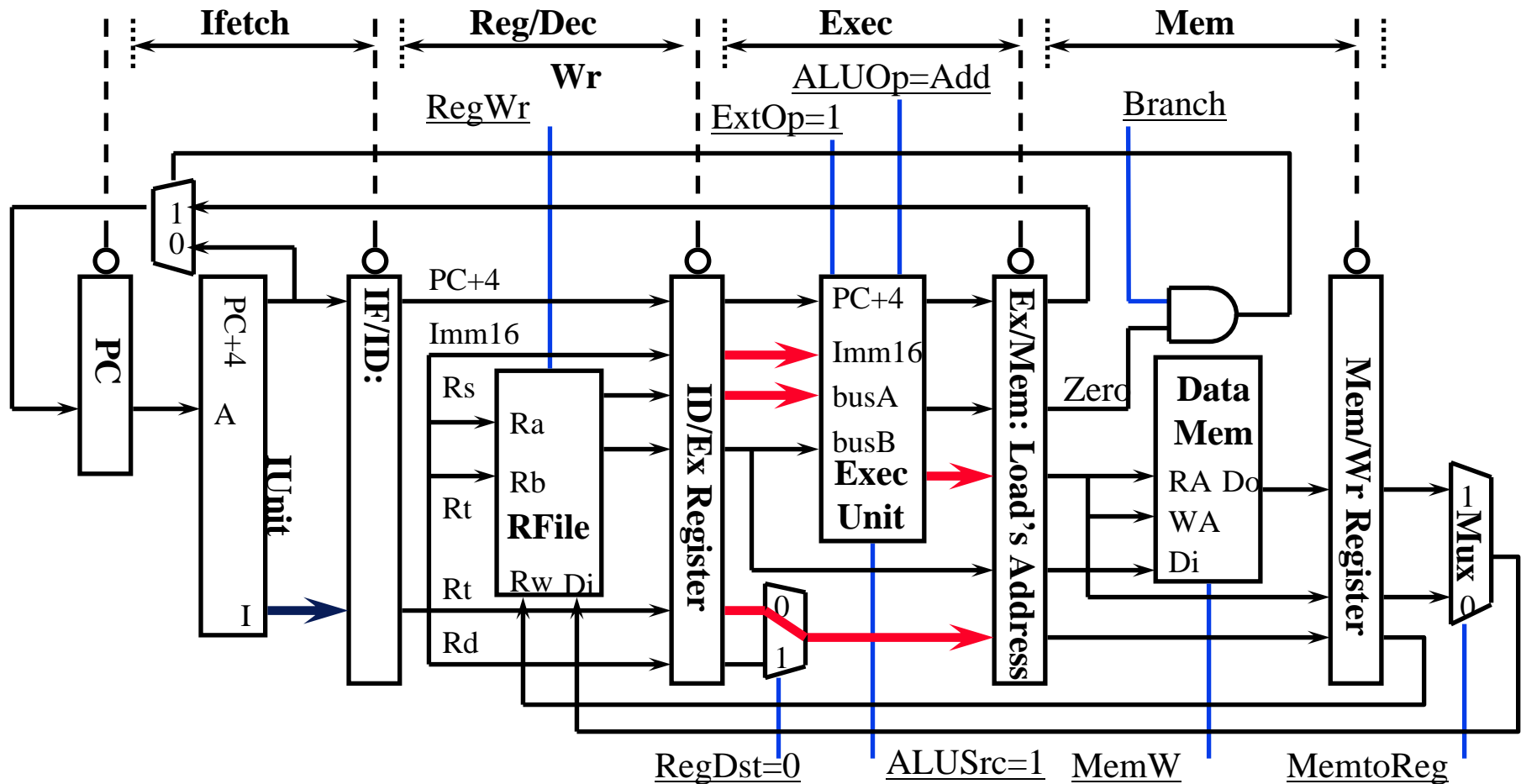- Key Observation: Control Signals at Stage N = Func (Instr. at Stage N)
 - N = Exec, Mem, or Wr
- Example: Controls Signals at Exec Stage = Func(Load's Exec)





Pipeline Control

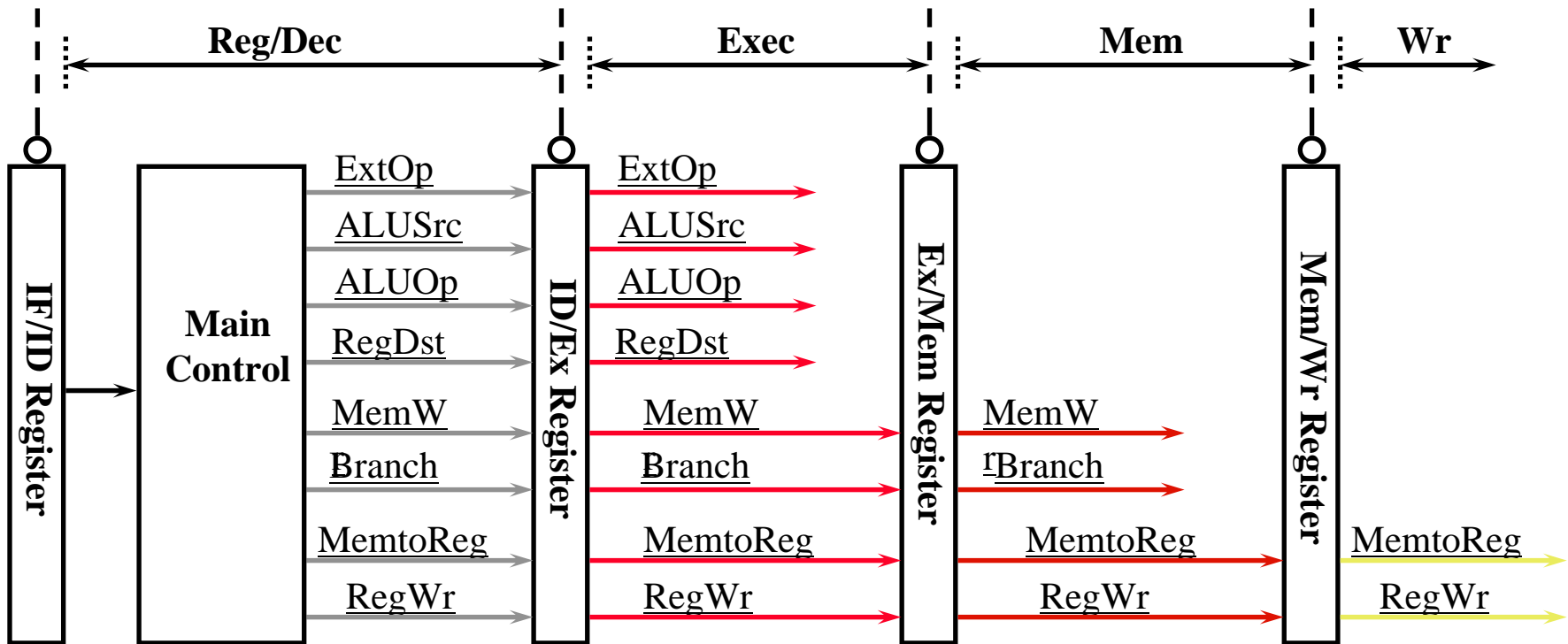- The Main Control generates the control signals during Reg/Dec
 - Control signals for Exec (ExtOp, ALUSrc, ...) are used 1 cycle later
 - Control signals for Mem (MemWr Branch) are used 2 cycles later
 - Control signals for Wr (MemtoReg MemWr) are used 3 cycles later



 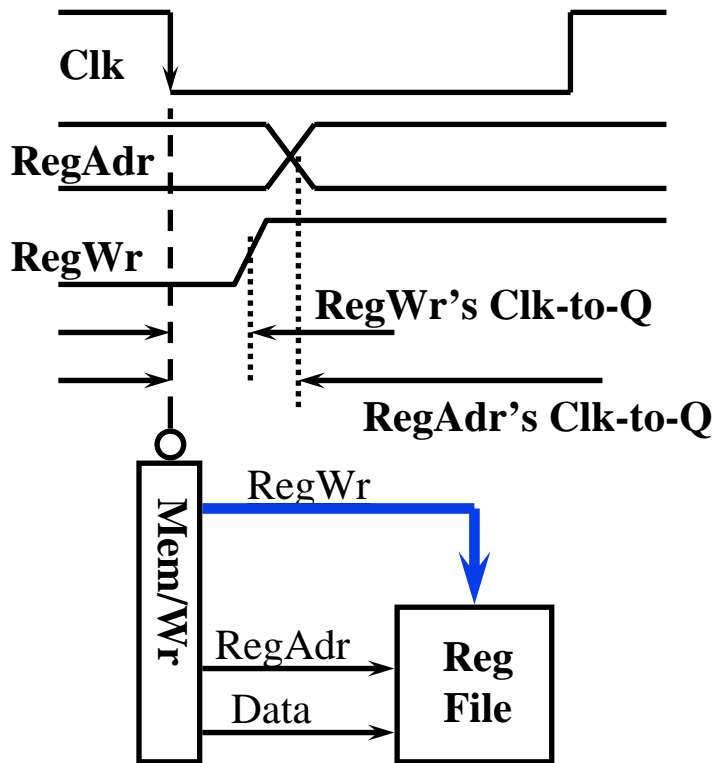
Beginning of the Wr's Stage: A Real World Problem



- At the beginning of the Wr stage, we have a problem if:
 - $\text{RegAdr's (Rd or Rt) Clk-to-Q} > \text{RegWr's Clk-to-Q}$
- Similarly, at the beginning of the Mem stage, we have a problem if:
 - $\text{WrAdr's Clk-to-Q} > \text{MemWr's Clk-to-Q}$
- **We have a race condition between Address and Write Enable!**


The Pipeline Problem

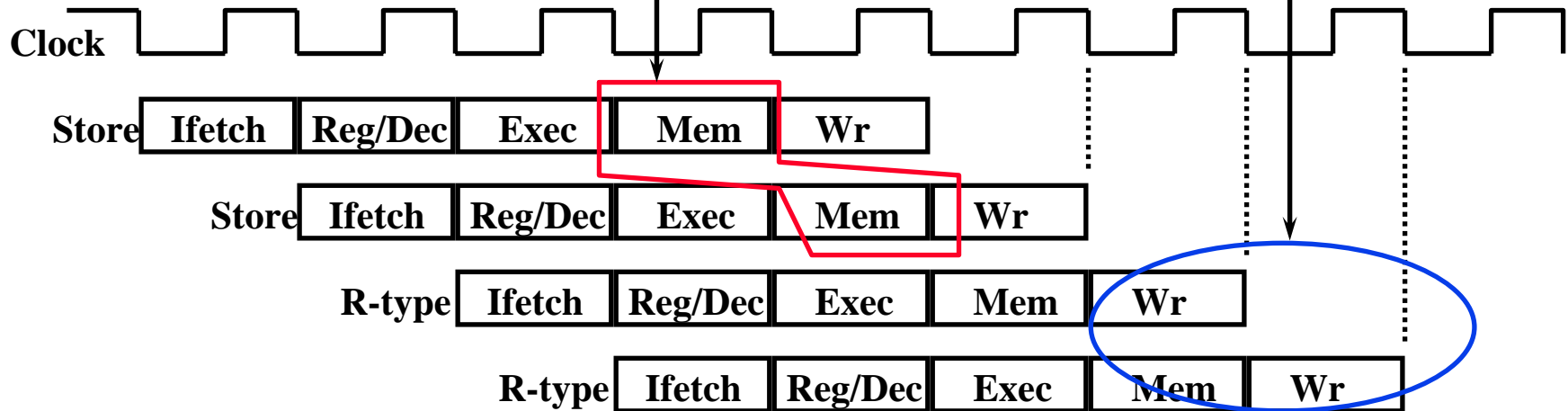- Multiple Cycle design prevents race condition between Addr and WrEn:
 - Make sure Address is stable by the end of Cycle N
 - Asserts WrEn during Cycle N + 1
- This approach can NOT be used in the pipeline design because:
 - Must be able to write the register file every cycle
 - Must be able write the data memory every cycle



Synchronize Register File & Synchronize Memory


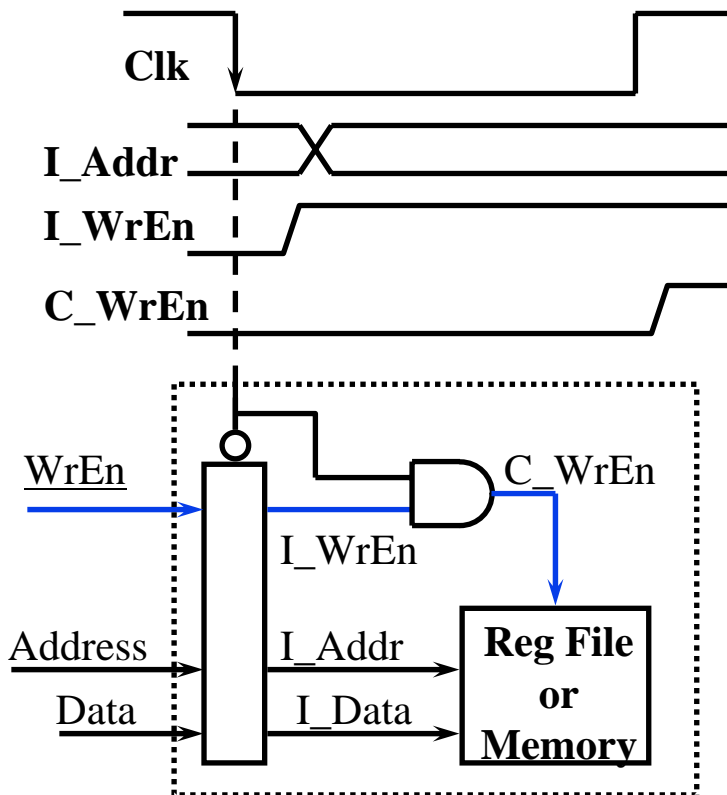
- **Solution: And the Write Enable signal with the Clock**
 - This is the **ONLY** place where gating the clock is used
 - **MUST** consult circuit expert to ensure no timing violation:
 - Example: Clock High Time > Write Access Delay




Synchronize Memory and Register File

Address, Data, and WrEn must be stable at least 1 set-up time before the Clk edge

  Write occurs at the cycle following the clock edge that captures the signals




A More Extensive Pipelining Example

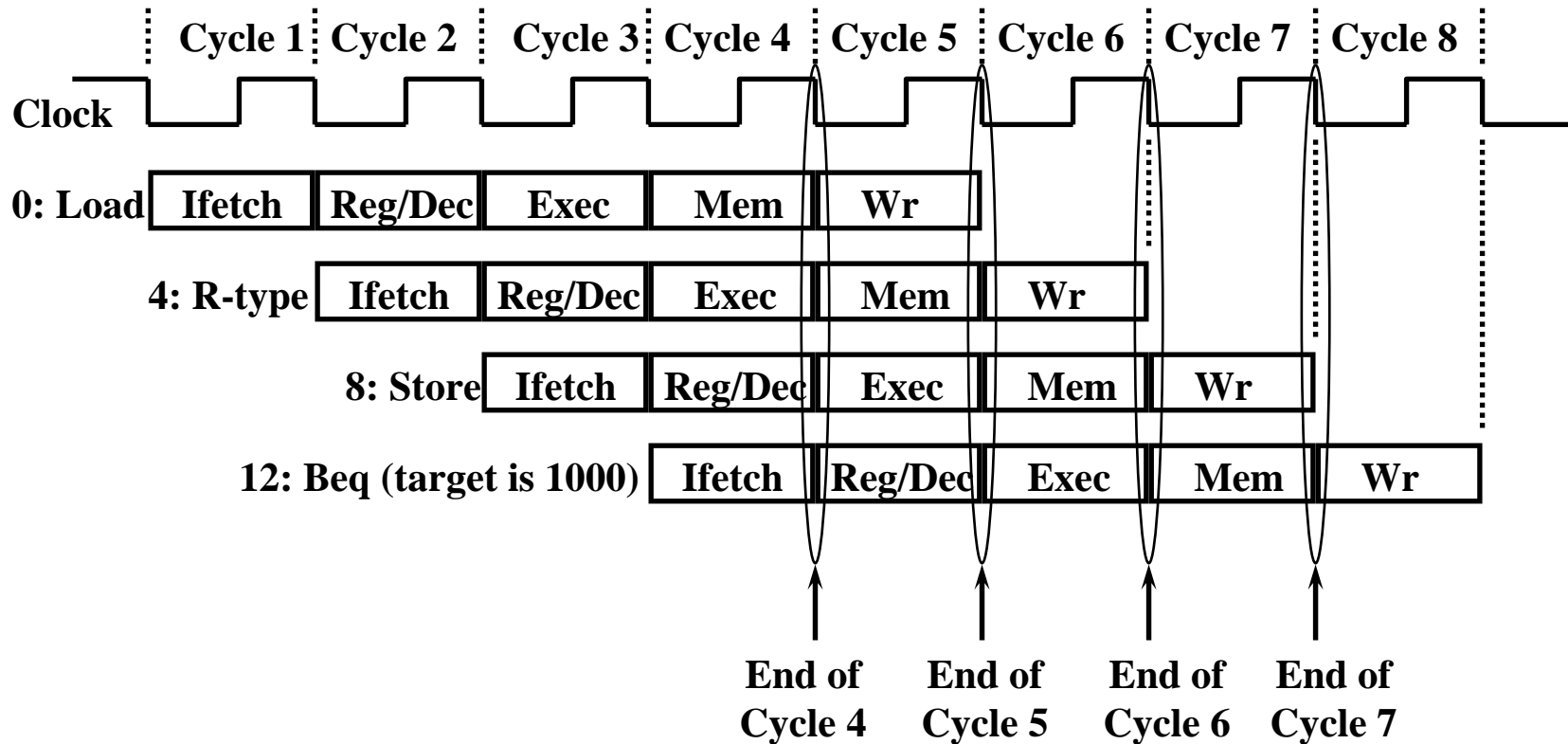

- End of Cycle 4: Load's Mem, R-type's Exec, Store's Reg, Beq's Ifetch
- End of Cycle 5: Load's Wr, R-type's Mem, Store's Exec, Beq's Reg
- End of Cycle 6: R-type's Wr, Store's Mem, Beq's Exec
- End of Cycle 7: Store's Wr, Beq's Mem


Pipelining Example: End of Cycle 4

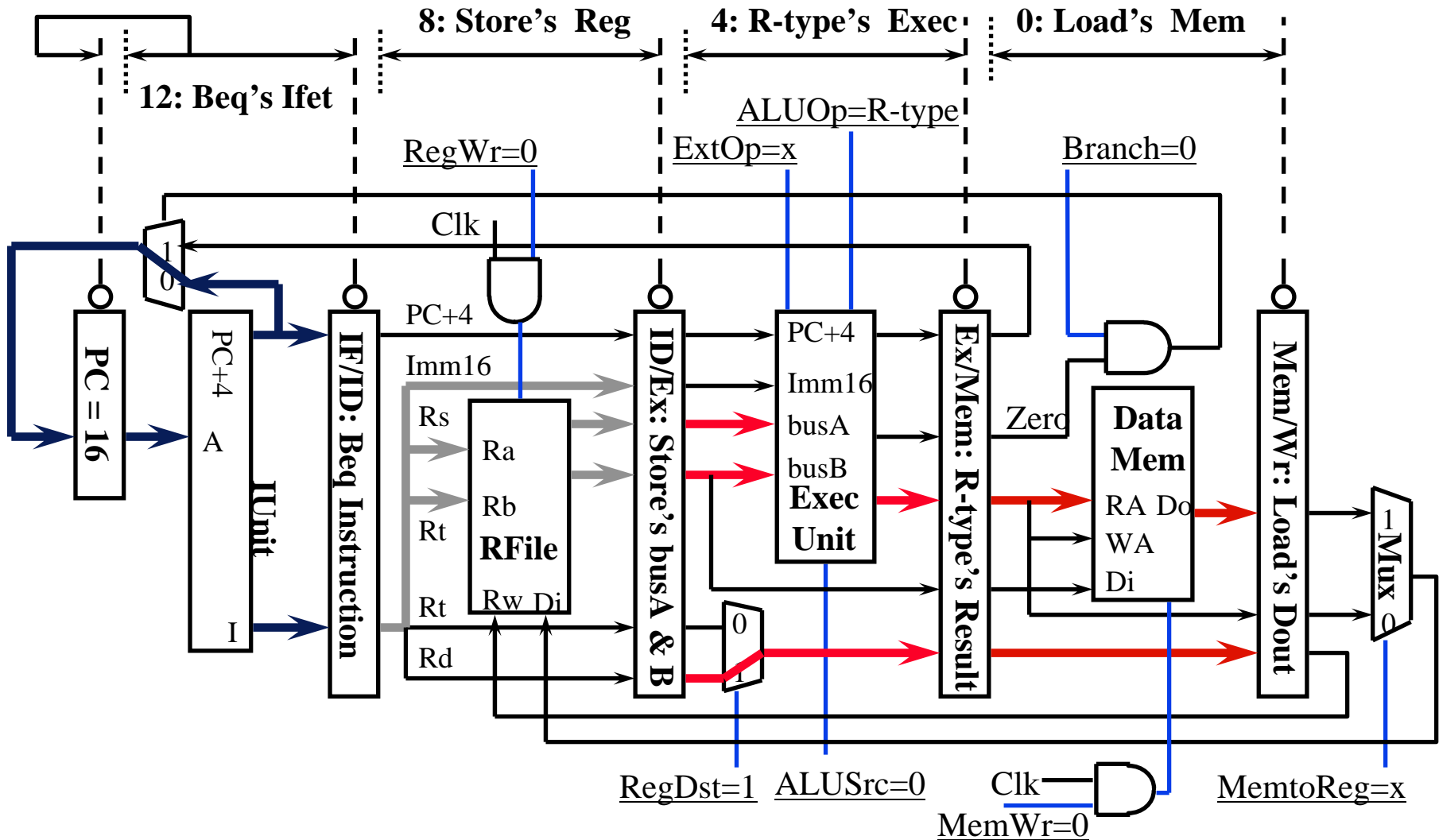° 0: Load's Mem 4: R-type's Exec 8: Store's Reg 12: Beq's Ifetch




Pipelining Example: End of Cycle 5

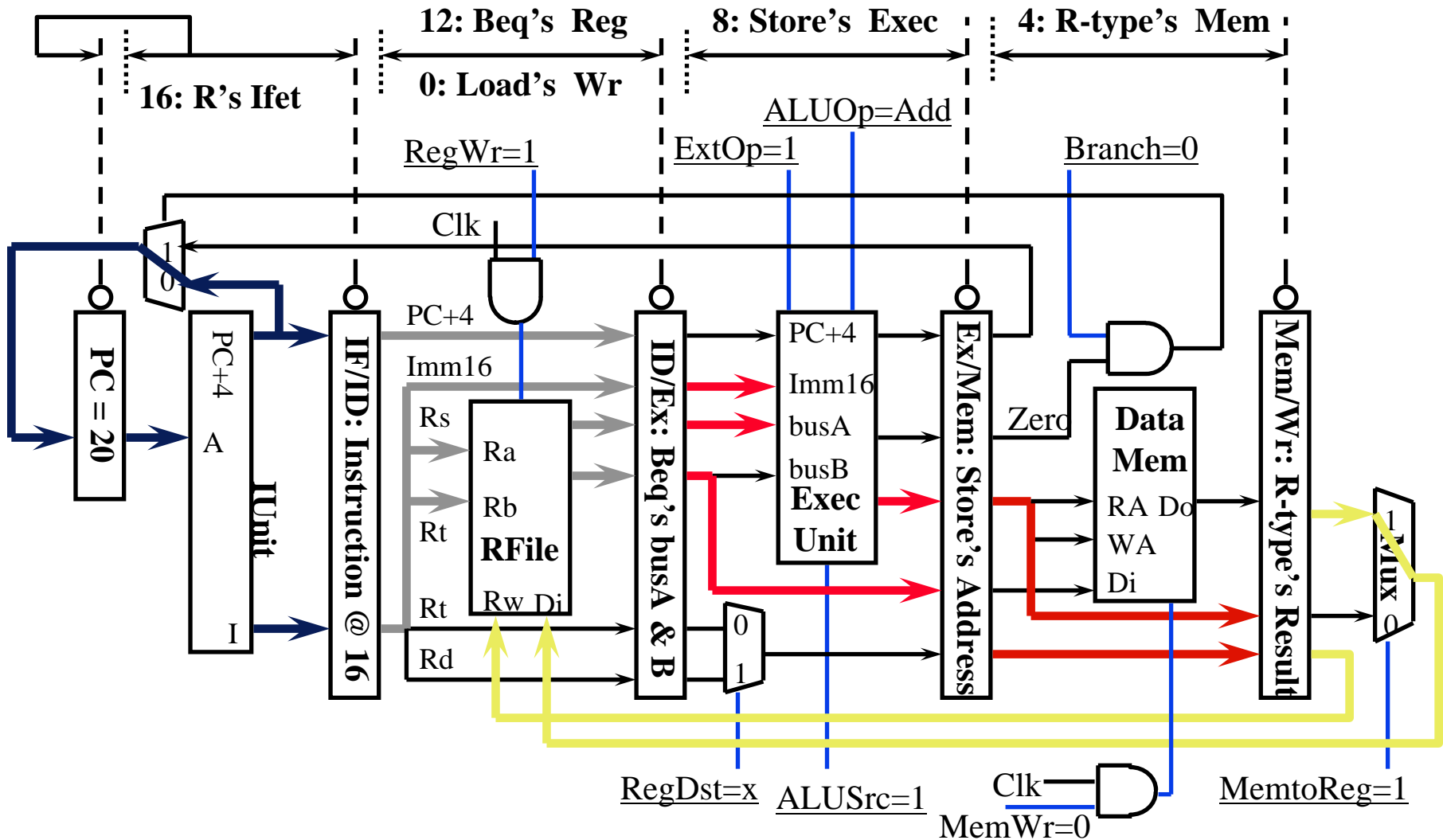° 0: Lw's Wr 4: R's Mem 8: Store's Exec 12: Beq's Reg 16: R's Ifetch




Pipelining Example: End of Cycle 6

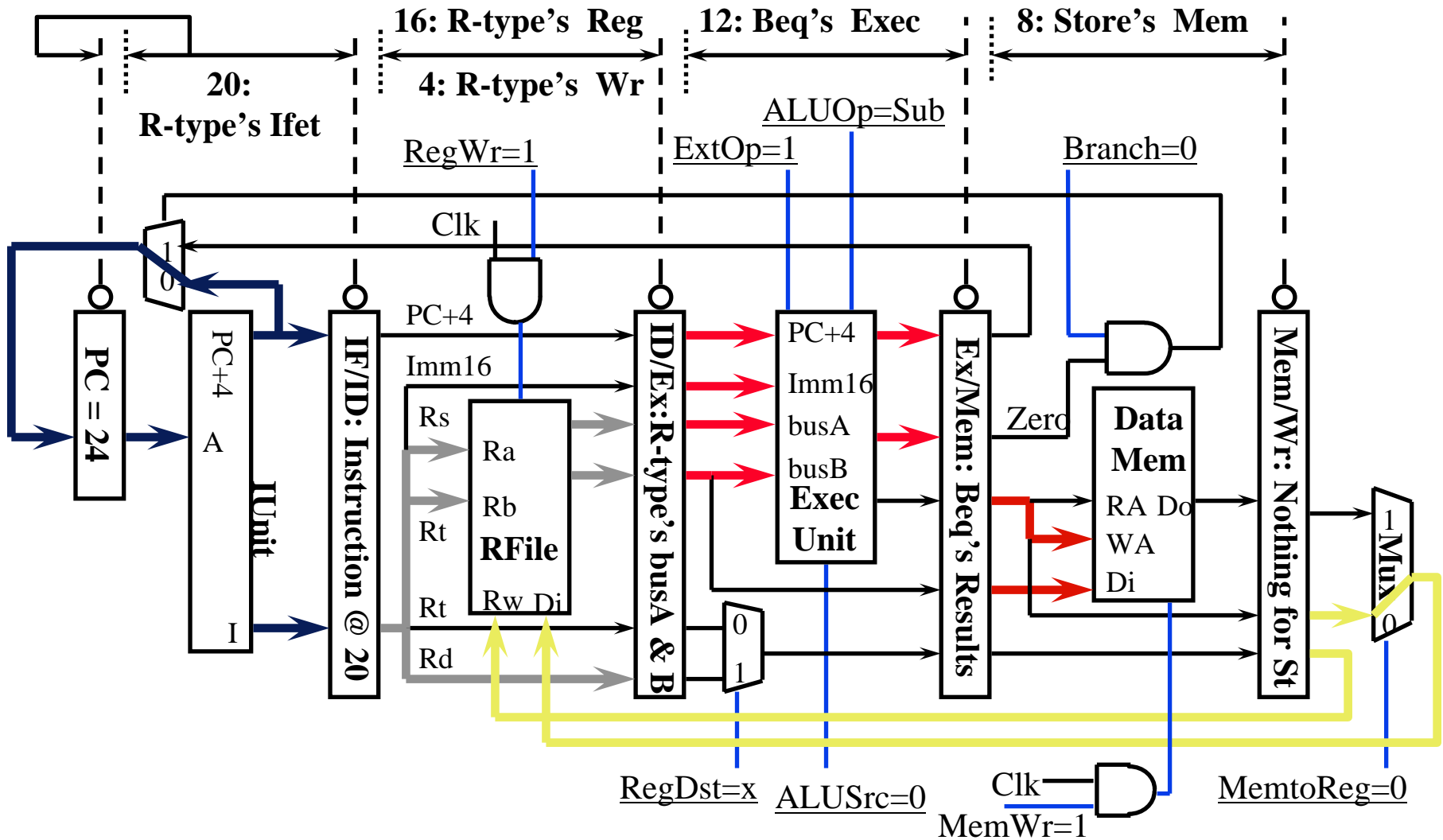◦ 4: R's Wr 8: Store's Mem 12: Beq's Exec 16: R's Reg 20: R's Ifet




Pipelining Example: End of Cycle 7

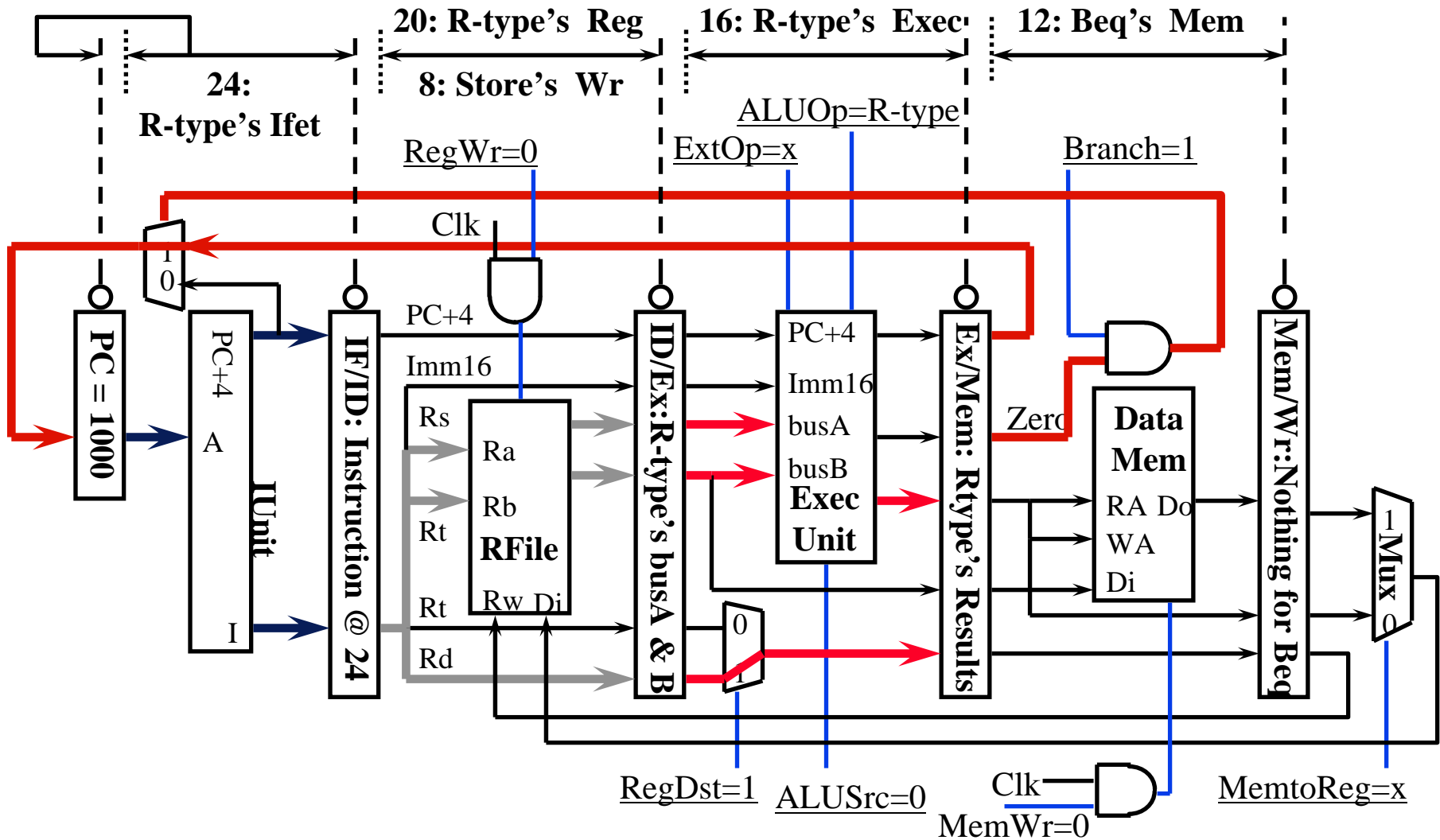◦ 8: Store's Wr 12: Beq's Mem 16: R's Exec 20: R's Reg 24: R's Ifet




The Delay Branch Phenomenon

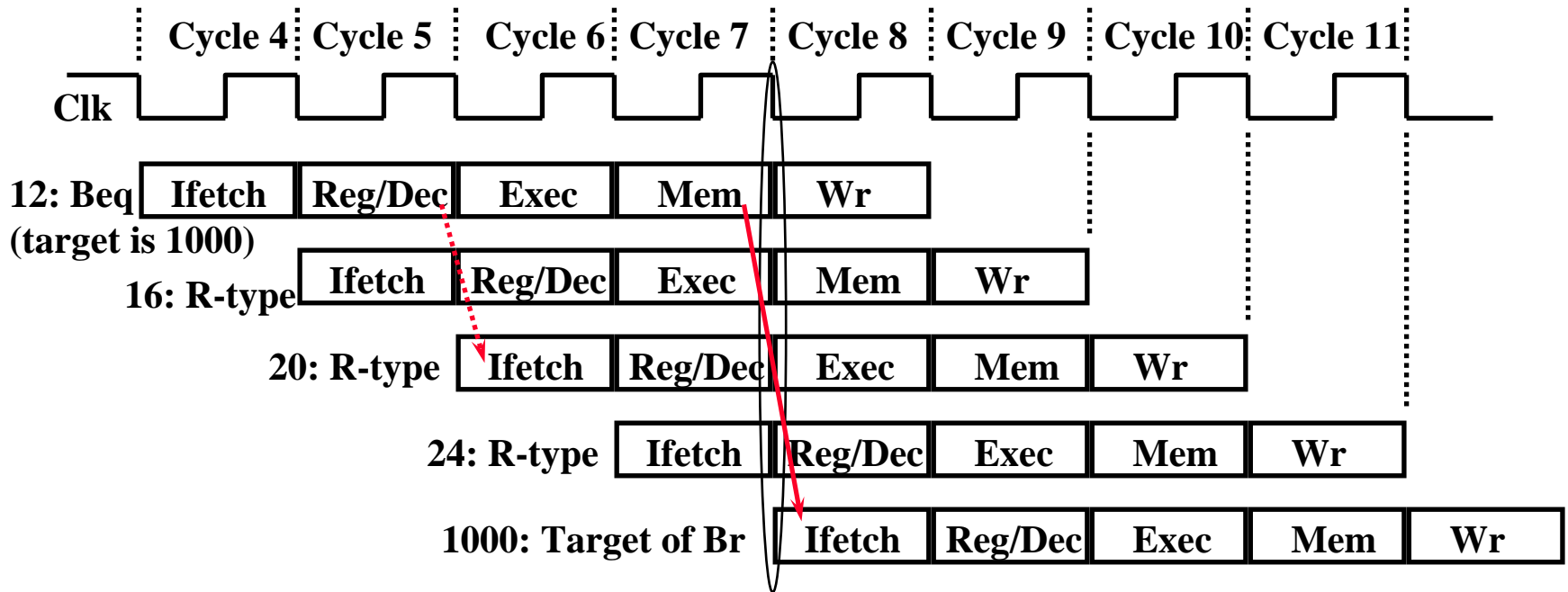

- Although Beq is fetched during Cycle 4:
 - Target address is NOT written into the PC until the end of Cycle 7
 - Branch's target is NOT fetched until Cycle 8
 - 3-instruction delay before the branch take effect
- This is referred to as Branch Hazard:
 - Clever design techniques can reduce the delay to ONE instruction

The Delay Load Phenomenon

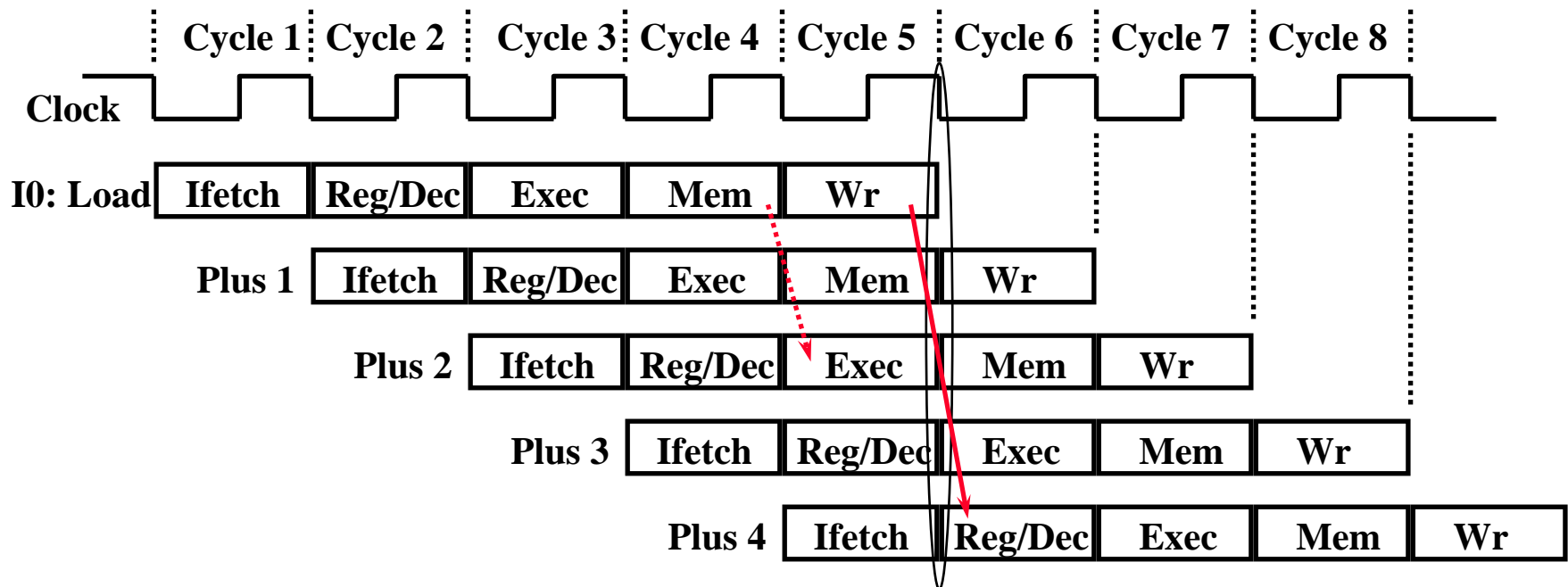

- Although Load is fetched during Cycle 1:
 - The data is NOT written into the Reg File until the end of Cycle 5
 - We cannot read this value from the Reg File until Cycle 6
 - 3-instruction delay before the load take effect
- This is referred to as Data Hazard:
 - Clever design techniques can reduce the delay to ONE instruction

Summary

- **Disadvantages of the Single Cycle Processor**
 - Long cycle time
 - Cycle time is too long for all instructions except the Load
- **Multiple Clock Cycle Processor:**
 - Divide the instructions into smaller steps
 - Execute each step (instead of the entire instruction) in one cycle
- **Pipeline Processor:**
 - Natural enhancement of the multiple clock cycle processor
 - Each functional unit can only be used once per instruction
 - If a instruction is going to use a functional unit:
 - it must use it at the same stage as all other instructions
 - Pipeline Control:
 - Each stage's control signal depends **ONLY** on the instruction that is currently in that stage