

361
Computer Architecture
Lecture 12: Designing a Pipeline Processor

pipeline.1

Overview of a Multiple Cycle Implementation

- The root of the single cycle processor's problems:
 - The cycle time has to be long enough for the slowest instruction
- Solution:
 - Break the instruction into smaller steps
 - Execute each step (instead of the entire instruction) in one cycle
 - Cycle time: time it takes to execute the longest step
 - Keep all the steps to have similar length
 - This is the essence of the multiple cycle processor
- The advantages of the multiple cycle processor:
 - Cycle time is much shorter
 - Different instructions take different number of cycles to complete
 - Load takes five cycles
 - Jump only takes three cycles
 - Allows a functional unit to be used more than once per instruction

pipeline.2

[illegible]

Outline of Today's Lecture

- **Recap and Introduction**
- **Introduction to the Concept of Pipelined Processor**
- **Pipelined Datapath and Pipelined Control**
- **How to Avoid Race Condition in a Pipeline Design?**
- **Pipeline Example: Instructions Interaction**
- **Summary**

pipeline.4


Pipelining is Natural!

- Laundry Example
- Sammy, Marc, Griffy, Albert each have one load of clothes to wash, dry, and fold
- Washer takes 30 minutes
- Dryer takes 30 minutes
- “Folder” takes 30 minutes
- “Stasher” takes 30 minutes to put clothes into drawers





pipeline.5

Sequential Laundry

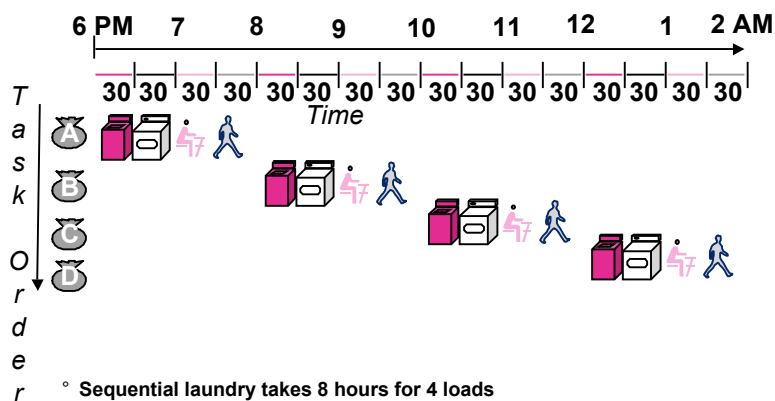

- If they learned pipelining, how long would laundry take?

pipeline.6

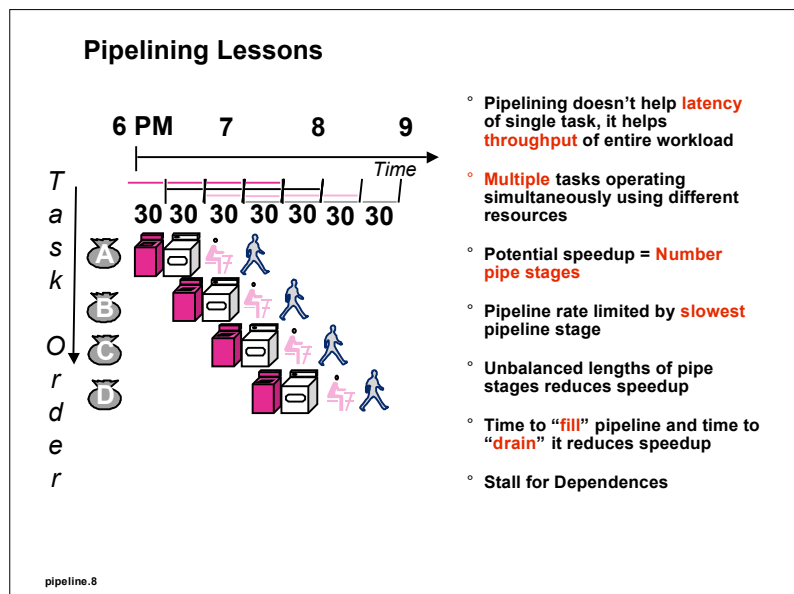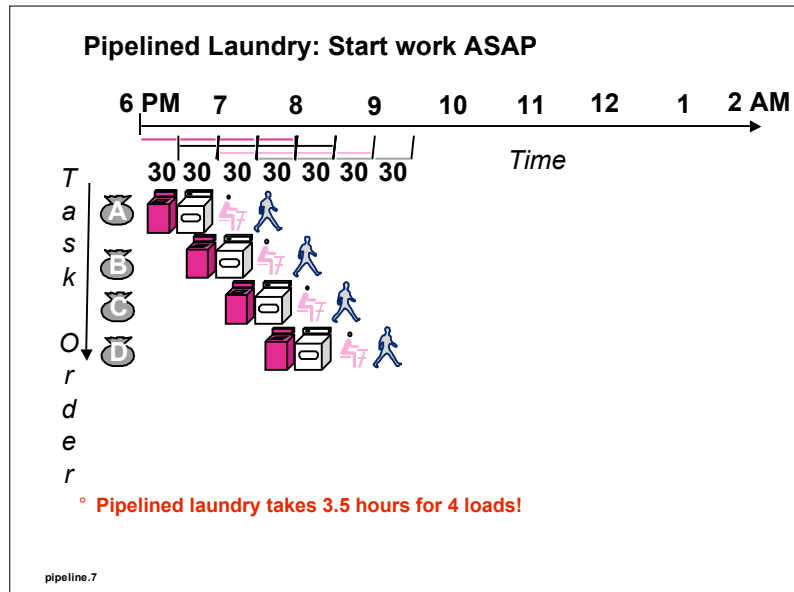


Why Pipeline?

- Suppose we execute 100 instructions
- Single Cycle Machine
 - $45 \text{ ns/cycle} \times 1 \text{ CPI} \times 100 \text{ inst} = 4500 \text{ ns}$
- Multicycle Machine
 - $10 \text{ ns/cycle} \times 4.6 \text{ CPI (due to inst mix)} \times 100 \text{ inst} = 4600 \text{ ns}$
- Ideal pipelined machine
 - $10 \text{ ns/cycle} \times (1 \text{ CPI} \times 100 \text{ inst} + 4 \text{ cycle drain}) = 1040 \text{ ns}$


pipeline.9

Timing Diagram of a Load Instruction

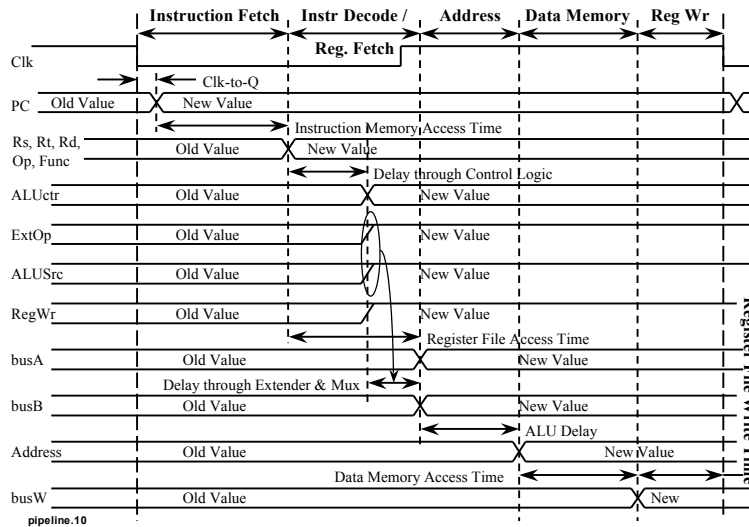

pipeline.10


The Five Stages of Load

 

- **Ifetch: Instruction Fetch**
 - Fetch the instruction from the Instruction Memory
- **Reg/Dec: Registers Fetch and Instruction Decode**
- **Exec: Calculate the memory address**
- **Mem: Read the data from the Data Memory**
- **Wr: Write the data back to the register file**

pipeline.11


Pipelining the Load Instruction

 

- The five independent functional units in the pipeline datapath are:
 - Instruction Memory for the Ifetch stage
 - Register File's Read ports (bus A and busB) for the Reg/Dec stage
 - ALU for the Exec stage
 - Data Memory for the Mem stage
 - Register File's Write port (bus W) for the Wr stage
- One instruction enters the pipeline every cycle
 - One instruction comes out of the pipeline (complete) every cycle
 - The "Effective" Cycles per Instruction (CPI) is 1


pipeline.12

Conventional Pipelined Execution Representation

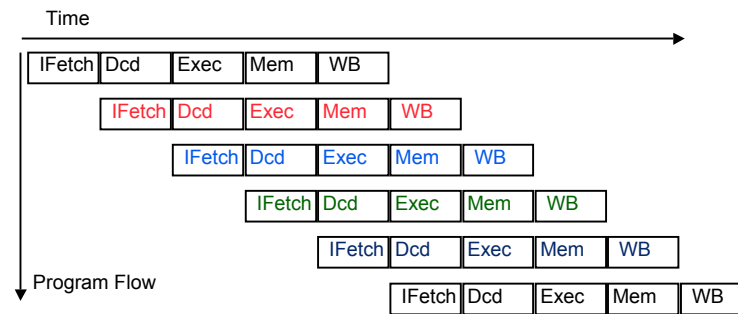


pipeline.13

Single Cycle, Multiple Cycle, vs. Pipeline

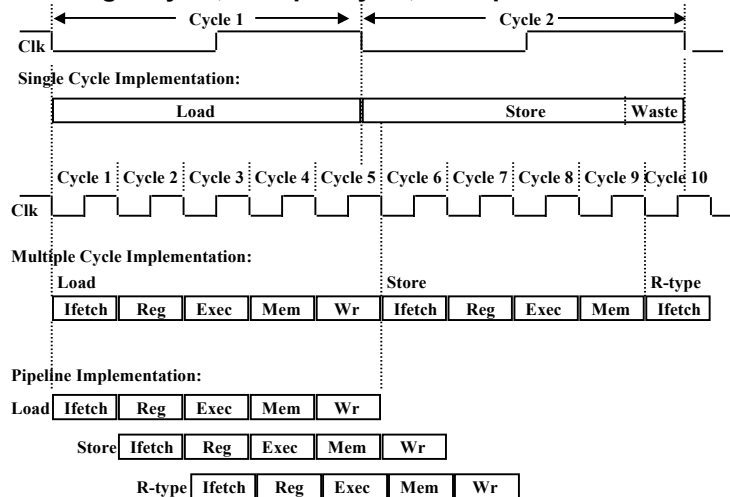

pipeline.14

Why Pipeline? Because the resources are there!

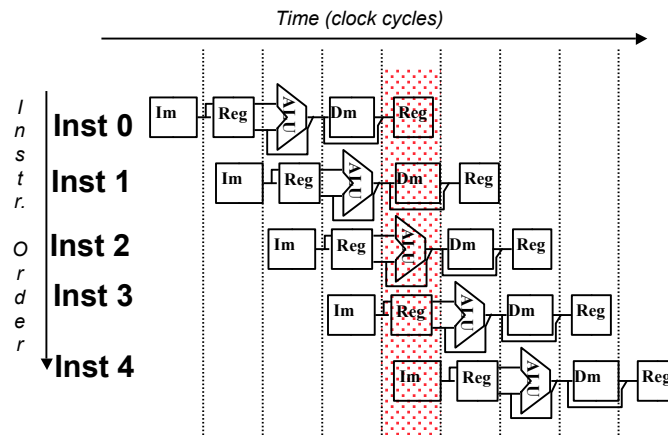

pipeline.15

Can pipelining get us into trouble?

° Yes: Pipeline Hazards


- **structural hazards:** attempt to use the same resource two different ways at the same time
 - E.g., combined washer/dryer would be a structural hazard or folder busy doing something else (watching TV)
- **data hazards:** attempt to use item before it is ready
 - E.g., one sock of pair in dryer and one in washer; can't fold until get sock from washer through dryer
 - instruction depends on result of prior instruction still in the pipeline
- **control hazards:** attempt to make a decision before condition is evaluated
 - E.g., washing football uniforms and need to get proper detergent level; need to see after dryer before next load in
 - branch instructions

° Can always resolve hazards by waiting

- pipeline control must detect the hazard
- take action (or delay action) to resolve hazards

pipeline.16

Single Memory is a Structural Hazard

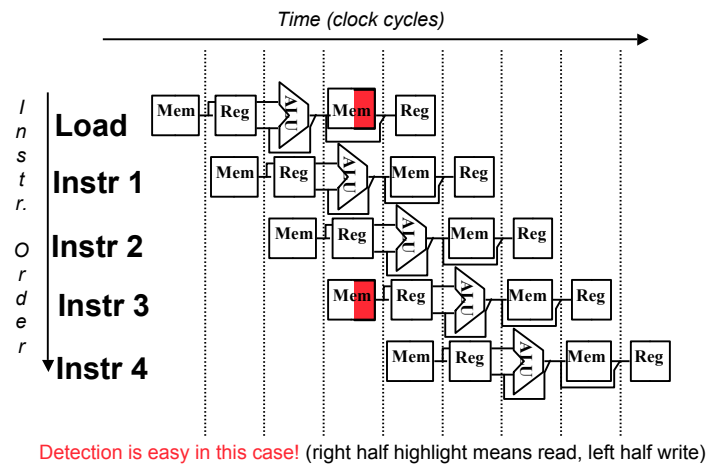


pipeline.17

Structural Hazards limit performance

- ° Example: if 1.3 memory accesses per instruction and only one memory access per cycle then
 - average CPI 1.3
 - otherwise resource is more than 100% utilized
 - More on Hazards later

pipeline.18

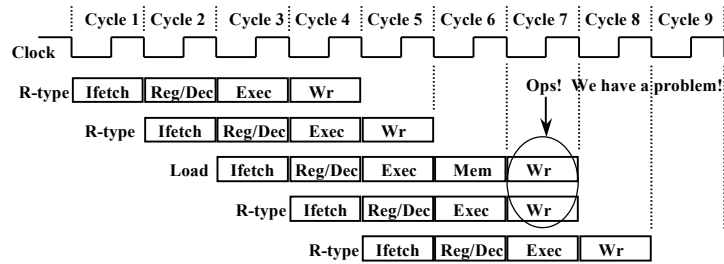
Pipelining the R-type and Load Instruction



- We have a problem:
 - Two instructions try to write to the register file at the same time!

pipeline.19

The Four Stages of R-type

 


- **Ifetch: Instruction Fetch**
 - Fetch the instruction from the Instruction Memory
- **Reg/Dec: Registers Fetch and Instruction Decode**
- **Exec: ALU operates on the two register operands**
- **Wr: Write the ALU output back to the register file**


pipeline.20

Important Observation

 - Each functional unit can only be used once per instruction
- Each functional unit must be used at the same stage for all instructions:
 - Load uses Register File's Write Port during its 5th stage




- R-type uses Register File's Write Port during its 4th stage

 

pipeline.21

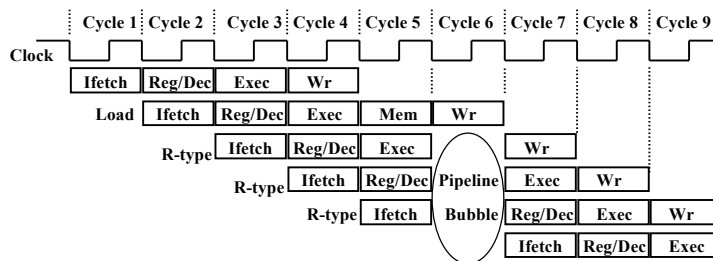Solution 1: Insert "Bubble" into the Pipeline




- Insert a "bubble" into the pipeline to prevent 2 writes at the same cycle
 - The control logic can be complex
- No instruction is completed during Cycle 5:
 - The "Effective" CPI for load is >1

pipeline.22


Solution 2: Delay R-type's Write by One Cycle

- Delay R-type's register write by one cycle:
 - Now R-type instructions also use Reg File's write port at Stage 5
 - Mem stage is a NOOP stage: nothing is being done

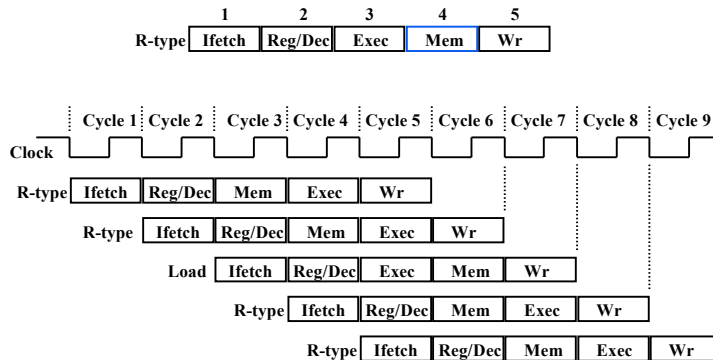

pipeline.23


The Four Stages of Store

 

- Ifetch: Instruction Fetch
 - Fetch the instruction from the Instruction Memory
- Reg/Dec: Registers Fetch and Instruction Decode
- Exec: Calculate the memory address
- Mem: Write the data into the Data Memory

pipeline.24


The Four Stages of Beq

 



- **Ifetch: Instruction Fetch**
 - Fetch the instruction from the Instruction Memory
- **Reg/Dec: Registers Fetch and Instruction Decode**
- **Exec: ALU compares the two register operands**
 - Adder calculates the branch target address
- **Mem: If the registers we compared in the Exec stage are the same,**
 - Write the branch target address into the PC

pipeline.25


A Pipelined Datapath

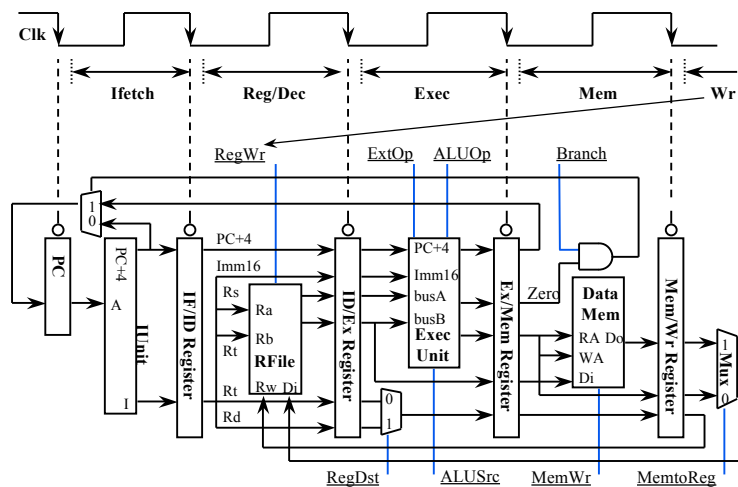

pipeline.26

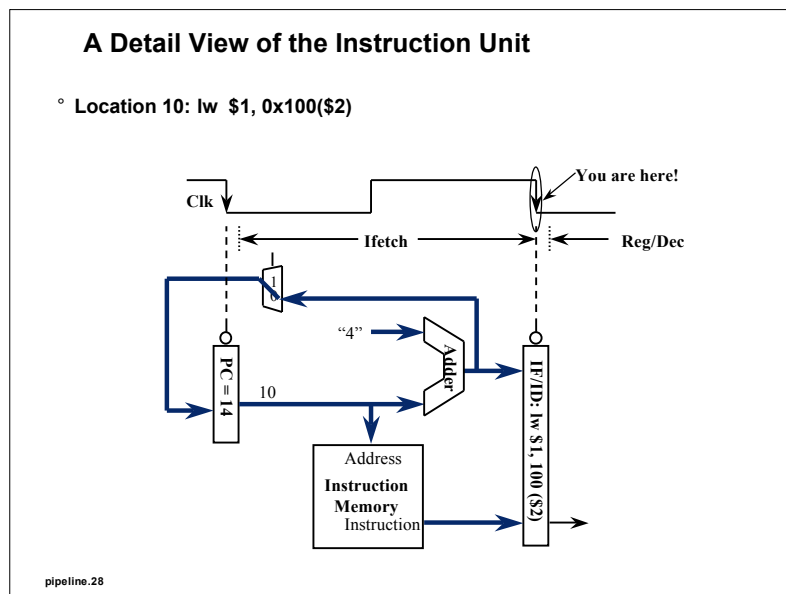 




A Detail View of the Execution Unit

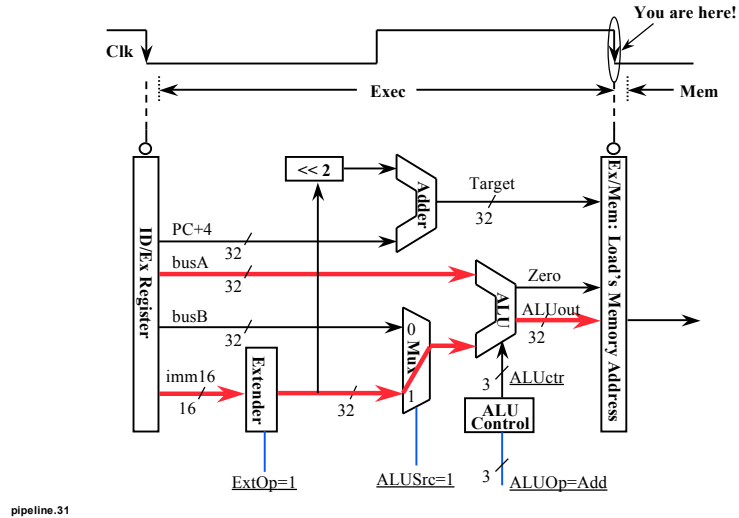

Load's Memory Access Stage

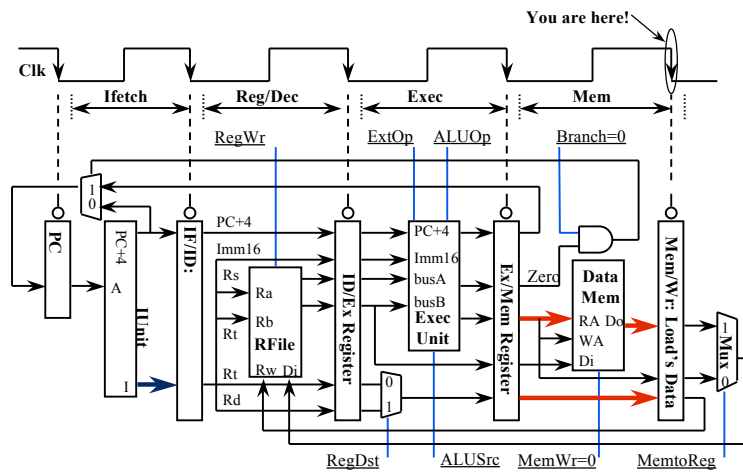
° Location 10: lw \$1, 0x100(\$2) \$1 <- Mem[(\$2) + 0x100]



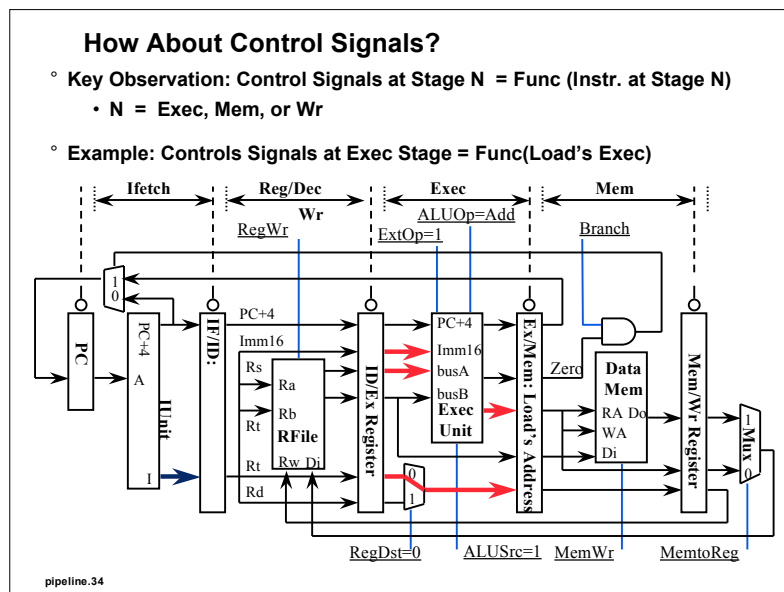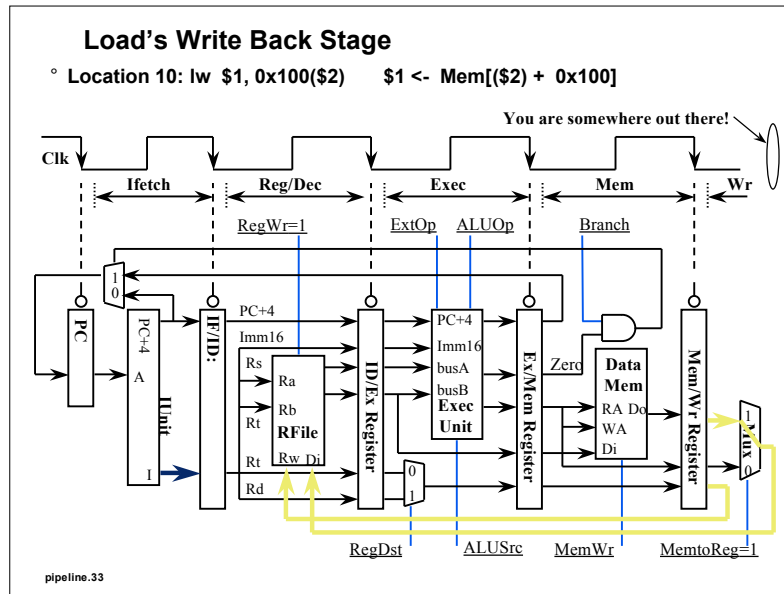


Pipeline Control

- The Main Control generates the control signals during Reg/Dec
 - Control signals for Exec (ExtOp, ALUSrc, ...) are used 1 cycle later
 - Control signals for Mem (MemWr Branch) are used 2 cycles later
 - Control signals for Wr (MemtoReg MemWr) are used 3 cycles later

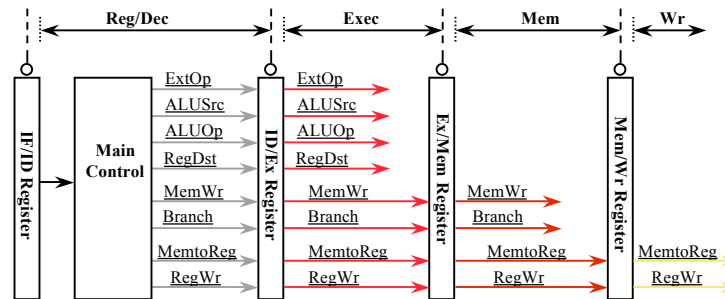

pipeline.35

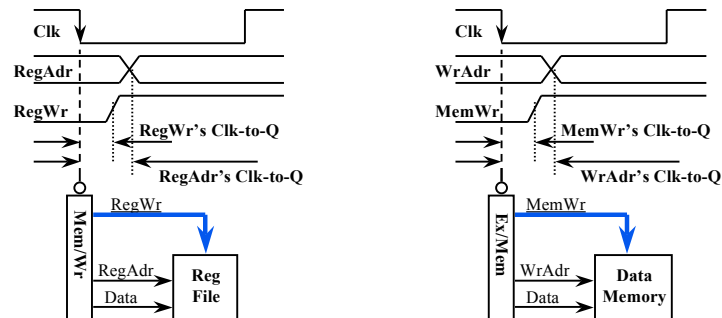Beginning of the Wr's Stage: A Real World Problem




- At the beginning of the Wr stage, we have a problem if:
 - RegAdr's (Rd or Rt) Clk-to-Q > RegWr's Clk-to-Q
- Similarly, at the beginning of the Mem stage, we have a problem if:
 - WrAdr's Clk-to-Q > MemWr's Clk-to-Q

◦ We have a race condition between Address and Write Enable!

pipeline.36

The Pipeline Problem


- Multiple Cycle design prevents race condition between Addr and WrEn:
 - Make sure Address is stable by the end of Cycle N
 - Asserts WrEn during Cycle N + 1
- This approach can NOT be used in the pipeline design because:
 - Must be able to write the register file every cycle
 - Must be able write the data memory every cycle

 

pipeline.37


Synchronize Register File & Synchronize Memory

- Solution: And the Write Enable signal with the Clock
 - This is the ONLY place where gating the clock is used
 - MUST consult circuit expert to ensure no timing violation:
 - Example: Clock High Time > Write Access Delay

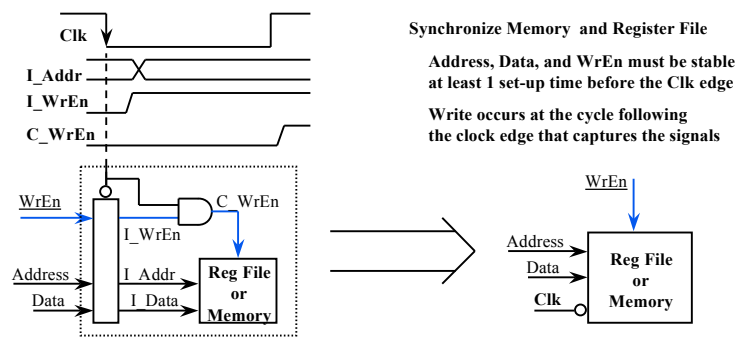

pipeline.38

A More Extensive Pipelining Example

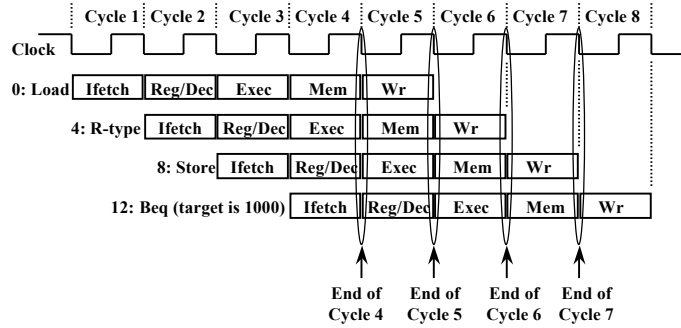


- ° End of Cycle 4: Load's Mem, R-type's Exec, Store's Reg, Beq's Ifetch
- ° End of Cycle 5: Load's Wr, R-type's Mem, Store's Exec, Beq's Reg
- ° End of Cycle 6: R-type's Wr, Store's Mem, Beq's Exec
- ° End of Cycle 7: Store's Wr, Beq's Mem



pipeline.39

Pipelining Example: End of Cycle 4

- ° 0: Load's Mem 4: R-type's Exec 8: Store's Reg 12: Beq's Ifetch

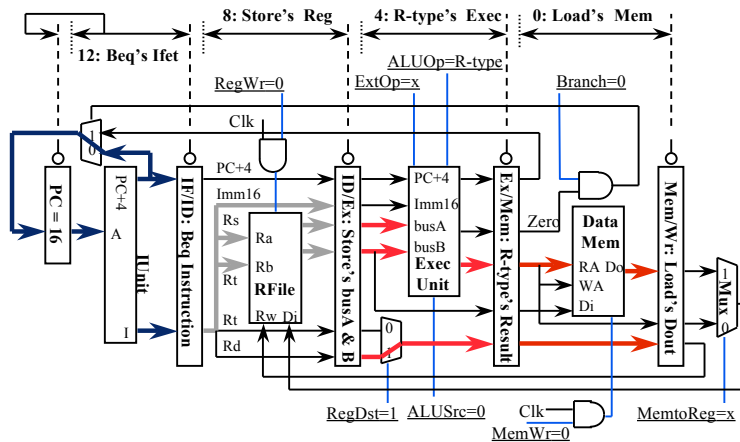


pipeline.40

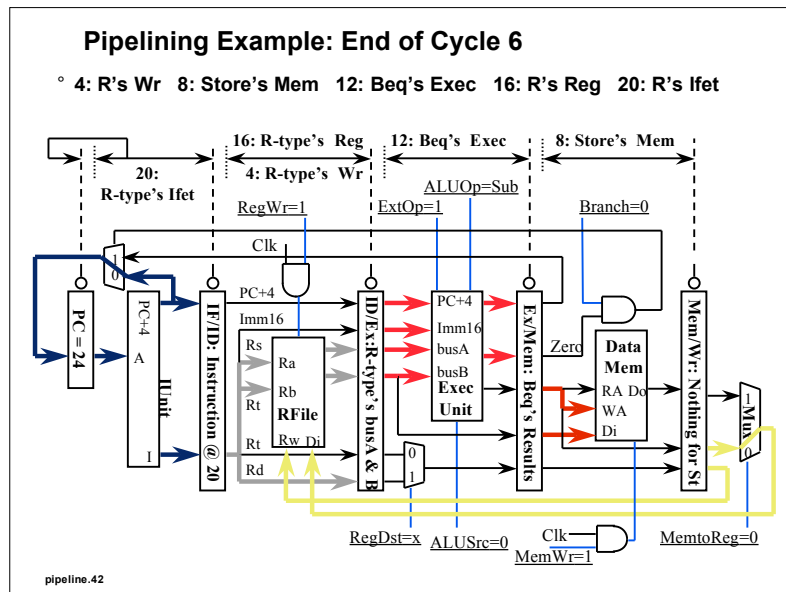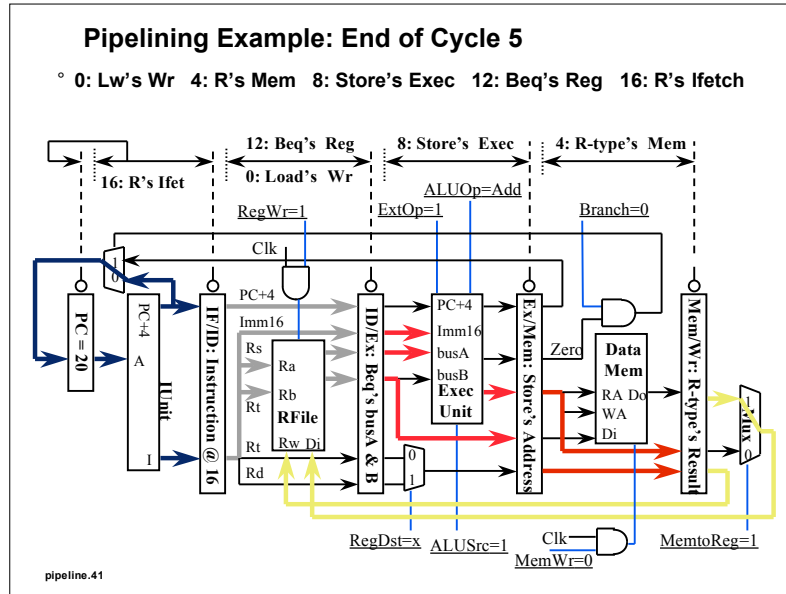


Pipelining Example: End of Cycle 7

° 8: Store's Wr 12: Beq's Mem 16: R's Exec 20: R's Reg 24: R's Ifet

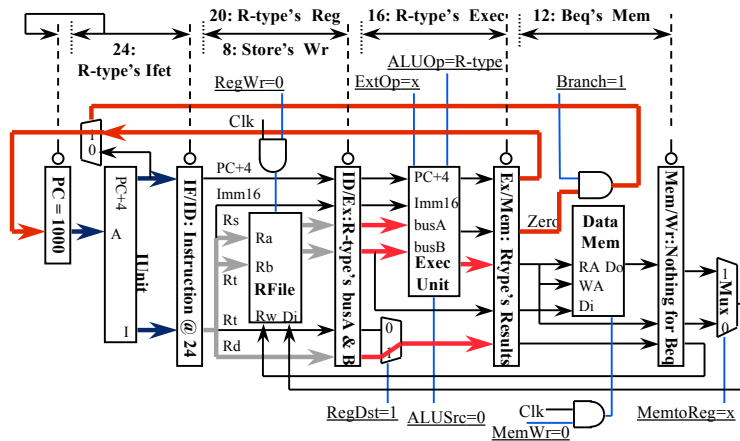

pipeline.43


The Delay Branch Phenomenon

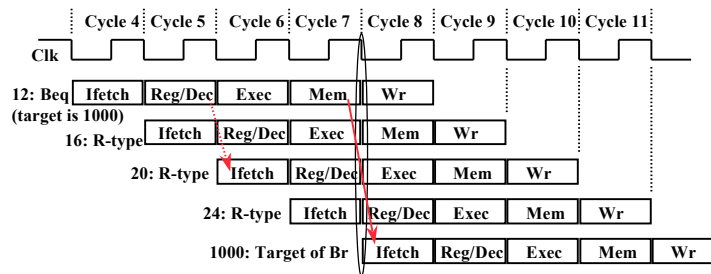

- ° Although Beq is fetched during Cycle 4:
 - Target address is NOT written into the PC until the end of Cycle 7
 - Branch's target is NOT fetched until Cycle 8
 - 3-instruction delay before the branch take effect
- ° This is referred to as Branch Hazard:
 - Clever design techniques can reduce the delay to ONE instruction

pipeline.44

The Delay Load Phenomenon

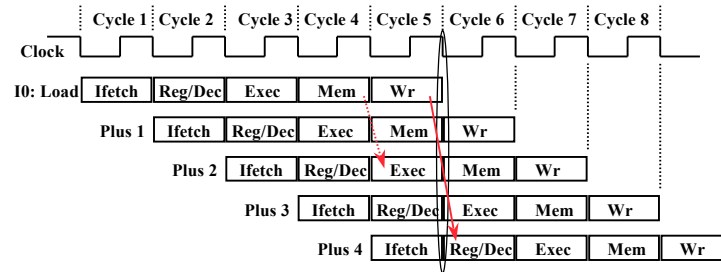

- ° Although Load is fetched during Cycle 1:
 - The data is NOT written into the Reg File until the end of Cycle 5
 - We cannot read this value from the Reg File until Cycle 6
 - 3-instruction delay before the load take effect
- ° This is referred to as Data Hazard:
 - Clever design techniques can reduce the delay to ONE instruction

pipeline.45

Summary

- ° Disadvantages of the Single Cycle Processor
 - Long cycle time
 - Cycle time is too long for all instructions except the Load
- ° Multiple Clock Cycle Processor:
 - Divide the instructions into smaller steps
 - Execute each step (instead of the entire instruction) in one cycle
- ° Pipeline Processor:
 - Natural enhancement of the multiple clock cycle processor
 - Each functional unit can only be used once per instruction
 - If a instruction is going to use a functional unit:
 - it must use it at the same stage as all other instructions
 - Pipeline Control:
 - Each stage's control signal depends ONLY on the instruction that is currently in that stage

pipeline.46